


EE3034
12/08/15



BT mir: PMOS & NMOS equivalent circuits
inverters CMOS

current mirrors BJT & CMOS

amplifiers; grounded source & source emitter followers
1, 1 emitter


$$V_{GS} = V_{GS} + V_{gs}$$

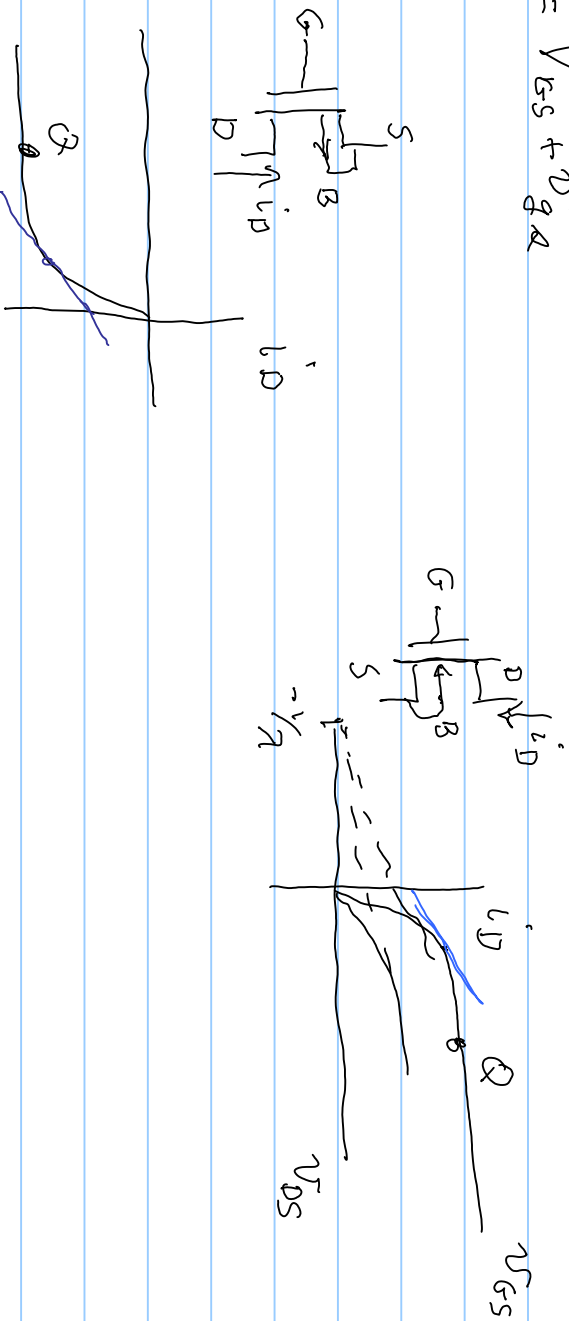

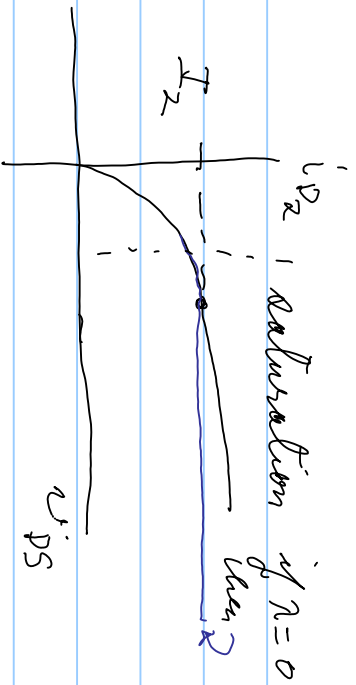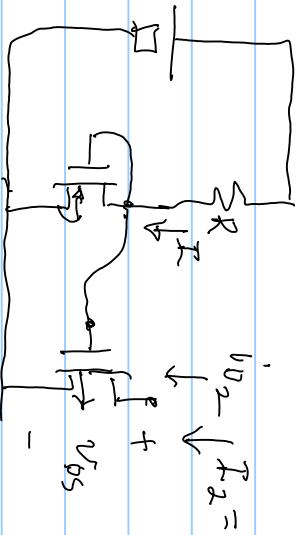


if $\lambda = 0$
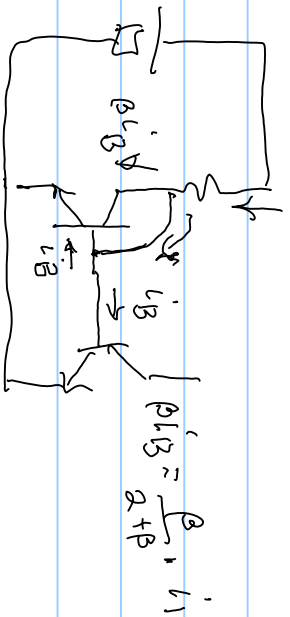
$$I_1 = \beta I_B + 2 I_B \Rightarrow I_B = I_1 / [2 + \beta]$$




$$I_C = \frac{\beta}{\beta + 1} I_1$$

Emitter follower.

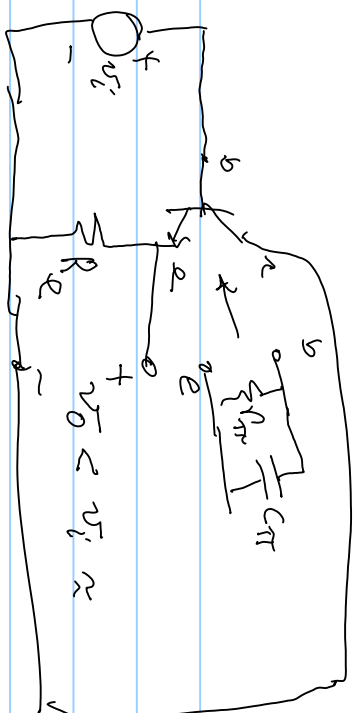

approx

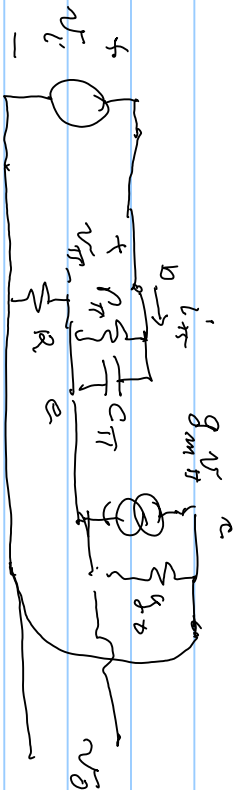

$$v_o = v_i - v_{TE} \Rightarrow g_m v_{TE} \approx i_b = i_b = (g_{\pi} + \alpha C_{\pi}) v_{TE}$$

$$KCL @ R_E : i_b + i_c = i_e = (g_{\pi} + \alpha C_{\pi}) v_{TE} + g_m v_{TE} - g_o v_o \geq G v_o$$

$$(g_{\pi} + \alpha) v_o = [g_m + g_{\pi} + \alpha C_{\pi}] v_{TE}$$

$$v_o = v_i \frac{g_{\pi} + \alpha}{g_m + g_{\pi} + \alpha C_{\pi}} \Rightarrow \left[\frac{1 + \frac{g_{\pi} + \alpha}{g_m + g_{\pi} + \alpha C_{\pi}}}{g_m + g_{\pi} + \alpha C_{\pi}} \right] v_o = v_i$$

$$\frac{v_0}{v_i} = \text{voltage gain} = \frac{1}{1 + \frac{g_0 + G}{g_m + g_{\pi} + R C_{\pi}}} \approx 1$$

$$\approx \frac{g_m + g_{\pi} + R}{C_{\pi} \left[R + \frac{1}{C_{\pi}} \left[g_0 + G + g_m + g_{\pi} \right] \right]} \approx \frac{R - R_0}{R - R_0}$$

$$A_0 \approx - \frac{(g_m + g_{\pi})}{C_{\pi}} = g_{\text{eff}}$$

$$R_p = - \frac{(g_0 + G + g_m + g_{\pi})}{C_{\pi}}$$

