

610 Fall 2015 – Homework 4 Due Tu 10/06/15

1. (50 points, degree one state-variable design)
For the driving point admittance
$$y(s) = [as+b]/[cs+d]$$
 - a) Set up state-variable equations. Interpret the state as voltage on capacitors and from that give a synthesis using a constant coupling admittance matrix, Y_c , loaded with a capacitor..
 - b) Show that $y(s)$ is PR for all real non-negative a, b, c, d . Then determine if the Y_c found in part a) is positive semi-definite to see if it can be made with only passive elements. {note: a sufficient condition for a matrix to be positive semi-definite is that all principle minors are non-negative; the condition for a matrix to be positive-definite is that all of the nested set of principle minors be positive}.
 - c) For $a=1, b=1, \text{ and } c=-1$ $y(s)$ is not PR. Prove that and discuss how this shows up in Y_c .

2. (20 points, V_2/V_1 design from state variables)
Given a voltage transfer function $A_v(s)=V_1/V_2=N(s)/D(s)$ where $N(s)$ and $D(s)$ are polynomials with real coefficients and with $A_v(s)$ having no pole at infinity, discuss design via state-variable equations using the fact that $N(s)$ and $D(s)$ can be factored into products of degree two or one polynomials with real coefficients. Will this work if $D(s)$ has zeros in the right half plane (meaning that $A_v(s)$ is unstable)

3. (30 points, Sensitivity via adjoint)
For the gyrator-capacitor circuit of Problem 1 of Homework set 3 use the adjoint method to find the sensitivity of V_o/V_i with respect to the capacitance C_1 and again to the gyrator conductance g .