
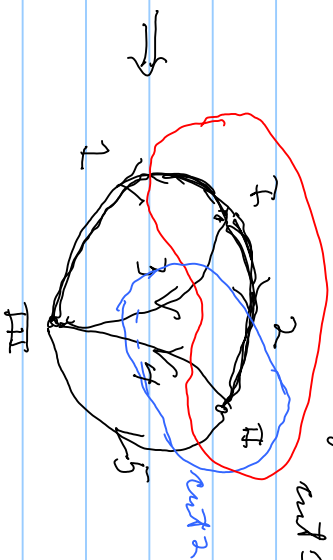


EE 610  
09/01/15

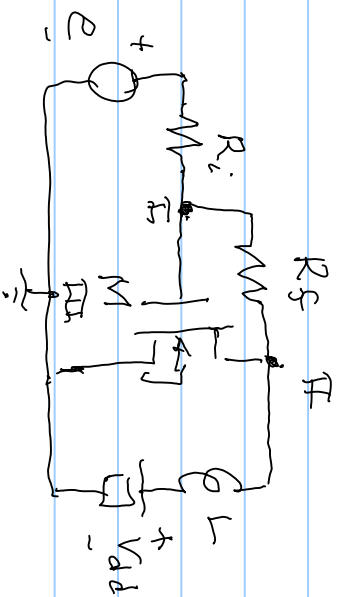KCL  $\Rightarrow \sum \text{currents into a node} = 0$   
 KVL  $\Rightarrow \sum \text{voltages around closed path} = 0$



$n = 3$  nodes  
 $b = 5$  branches  
 $T = 2$  trees  
 $R = 3$  links  
 $b = T + R$

$$v_b = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}, \quad i_b = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} v_T \\ v_R \end{bmatrix} = \begin{bmatrix} v_T \\ v_R \end{bmatrix}$$


KCL

$$0 = 1 \cdot i_1 + 0 \cdot i_2 + 1 \cdot i_3 + 1 \cdot i_4 + 1 \cdot i_5$$

$$0 = 0 \cdot i_1 + 1 \cdot i_2 + 0 \cdot i_3 - 1 \cdot i_4 - i_5$$

$$\Rightarrow \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \end{bmatrix} i_b \Rightarrow 0 = E i_b$$

KVL

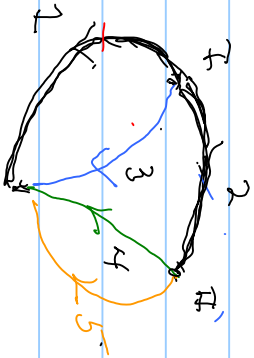

the vertices.

$$Q = \begin{bmatrix} -1 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 \\ -1 & 1 & 0 & 0 & 1 \end{bmatrix} v_b \Rightarrow Q = \sigma_j \cdot v_b$$

known Pin from outside = 0

$$l_b^T \cdot v_b = [l_1 \ l_2 \ l_3 \ l_4 \ l_5] \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = 0$$

$$Kv \Rightarrow Q = \sigma_j \cdot \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = [k_r \ | \ 1] v_b \Rightarrow v_b = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} 1 \\ \pm \\ -k_r \end{bmatrix} v_1$$


$$Kc \Rightarrow Q = c \begin{bmatrix} c_1 \\ c_2 \\ c_3 \\ c_4 \\ c_5 \end{bmatrix} = [1 \ \pm \ | \ k_c] \begin{bmatrix} c_1 \\ c_2 \\ c_3 \\ c_4 \\ c_5 \end{bmatrix} = 0 \quad l_c^T = -k_c \cdot l_r \Rightarrow l_c = \begin{bmatrix} c_1 \\ c_2 \\ c_3 \\ c_4 \\ c_5 \end{bmatrix} = \begin{bmatrix} -k_c \\ c_1 \\ 1 \end{bmatrix} l_r$$

$$I_b^T V_b = I_R^T [-K_v^T \vdots I_R] V_t = 0 \Rightarrow [-K_v^T \vdots I_R] \begin{bmatrix} 1 \\ t \\ -K_{rv} \end{bmatrix} = 0_{8 \times t}$$


$$\Rightarrow -K_v^T \cdot 1_t - K_{rv} \cdot 1_R = 0_{8 \times t} \Rightarrow -K_v^T = K_{rv}$$

$E = \begin{bmatrix} 1_t & -K_{rv}^T \end{bmatrix}$  } laws of connections for electronic circuits  
 $G_i = \begin{bmatrix} K_{rv} & 1_R \end{bmatrix}$




Y matrix for asymmetric lattice

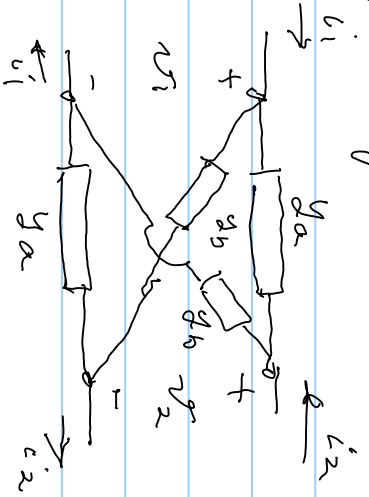
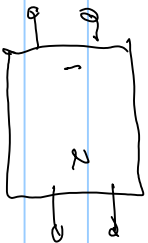
$$I = Y V \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$



$$y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$$

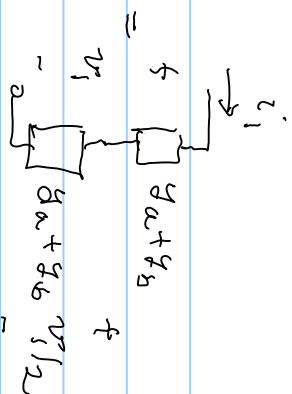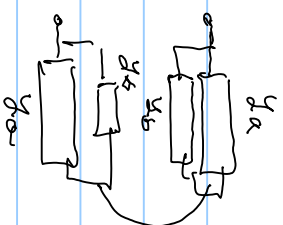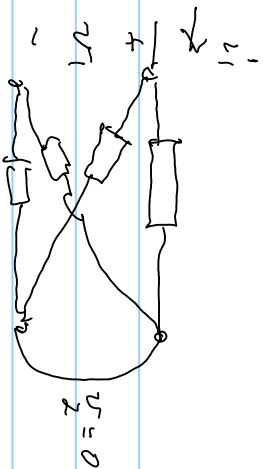

$$i_1 = (y_a + y_b) \cdot \frac{v_1}{2} \Rightarrow y_{11} = y_{22} = \frac{1}{2} (y_b + y_a)$$

$$y_{12} = \frac{1}{2} (y_b - y_a)$$

$$Y = \frac{1}{2} \begin{bmatrix} y_b + y_a & y_b - y_a \\ y_b - y_a & y_b + y_a \end{bmatrix}$$