

EE 610  
09/17/15

## Equivalent circuits

$$E \dot{x} = Ax + Bu$$

$$y = Cx$$

$$x = \text{semi-state} = \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix} = \text{b-vectors}$$

 $A$  is  $b \times b$ 

Let premultiply by a  $P$  that is nonsingular

$$PE \dot{x} = PAx + PBu, \quad y = Cx$$

and  $x = Q \tilde{x}$ ,  $Q$  nonsingular

$$PEQ \tilde{x} = PAQ \tilde{x} + PBu, \quad y = CQ \tilde{x}$$

$$y = T(\alpha)u, \quad T(\alpha) = C \left( \alpha I - A \right)^{-1} B = CQ \left( \alpha PEQ - PAQ \right)^{-1} PB$$

$$= CQ \left[ \alpha PE - PA \right] Q^{-1} PB$$

$$= CQ Q^{-1} \left( \alpha PE - PA \right)^{-1} PB$$

$$= C \left( P \left[ \alpha E - A \right] \right)^{-1} PB$$

$$= C \left( \alpha E - A \right)^{-1} P^{-1} PB$$

$$= C \left( \alpha E - A \right)^{-1} B$$

if we PBD to diagonalize  $E$  can get

$$1) \begin{bmatrix} A_{11} & 0 \\ 0 & 0_{b-r} \end{bmatrix} \begin{bmatrix} \hat{x} \\ x_{b-r} \end{bmatrix} = \begin{bmatrix} A_{11} & A_{12} \\ A_{21} & A_{22} \end{bmatrix} \begin{bmatrix} x \\ x_{b-r} \end{bmatrix} + \begin{bmatrix} B_1 \\ B_2 \end{bmatrix} u \quad \hat{x} = \begin{bmatrix} x \\ x_{b-r} \end{bmatrix}$$

$$2) \quad y = [C_1 \quad C_2] \begin{bmatrix} x \\ x_{b-r} \end{bmatrix}$$

$$3) \quad \dot{x}_e = A_{11} x_e + A_{12} x_{b-r} + B_1 u$$

$$4) \quad -A_{22} x_{b-r} = A_{21} x_e + B_2 u$$

if  $A_{22}$  is nonsingular then we can state variables equation


$$5) \quad x_{b-r} = -A_{22}^{-1} A_{21} x_e - A_{22}^{-1} B_2 u$$

$$5) \rightarrow 3) \quad \dot{x}_e = [A_{11} - A_{12} A_{22}^{-1} A_{21}] x_e + [B_1 - A_{12} A_{22}^{-1} B_2] u$$

$$5) \rightarrow 2) \quad y = [C_1 - C_2 A_{22}^{-1} A_{21}] x_e - C_2 A_{22}^{-1} B_2 u$$

these are state variables equations,  $x_e = \text{state}$

Sensitivity via the adjoint circuit

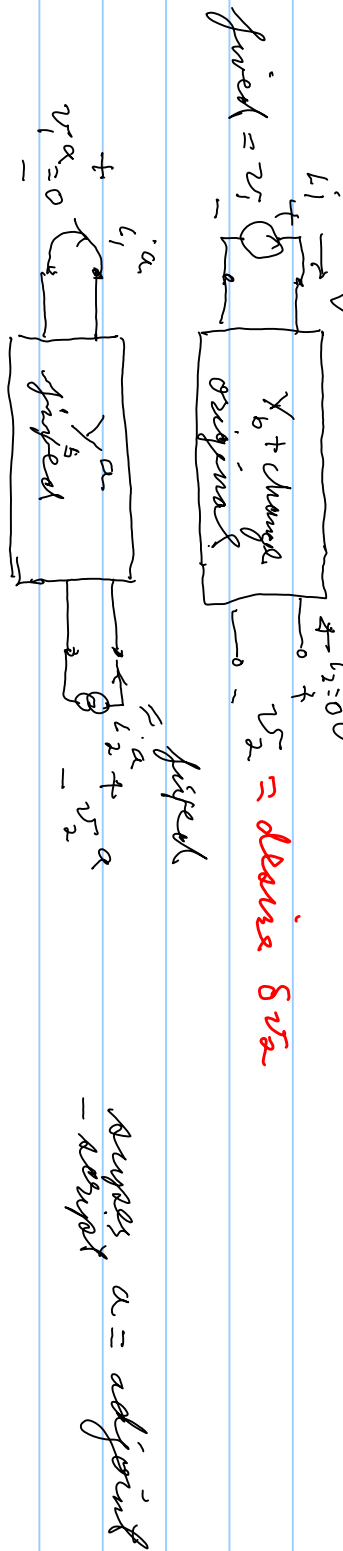

$$+ i_1^a \cdot v_1^a + v_1^a \cdot i_1^a + i_2^a \cdot v_2^a + v_2^a \cdot i_2^a + i_b^T \cdot v_b^a + v_b^a \cdot i_b^T = 0$$

Changes on this, use \$S\$ for derivates

$$\delta(i_1 \cdot v_1^a) + \delta(v_1 \cdot i_1^a) + \delta(i_2 \cdot v_2^a) + \delta(v_2 \cdot i_2^a) + \delta(i_b^T \cdot v_b^a) + \delta(v_b^a \cdot i_b^T) + \delta(v_2 \cdot i_2^a) + \delta(i_2 \cdot v_2^a) = 0$$

$$\Rightarrow \delta i_b = \delta Y_b \cdot v_b^a + Y_b \cdot \delta v_b^a, \quad \delta i_b^a = \delta Y_b^a \cdot v_b^a + Y_b^a \cdot \delta v_b^a \equiv 0 \text{ no change in adjoint circuit}$$

$$i_a \cdot \delta v_a = + \delta i_b^T v_b - i_b \cdot \delta v_b = + [v_b^T \cdot \delta Y_b^T + \delta v_b^T Y_b^T] v_b - [v_b^{aT} Y_b^{aT}] \delta v_b$$

Transformer = same result

$$i_a \delta v_a = i_b^{aT} [ \delta Y_b v_b + Y_b \delta v_b ] - v_b^{aT} Y_b^{aT} \delta v_b = + v_b^{aT} [ \delta Y_b v_b + Y_b \delta v_b - Y_b^{aT} \delta v_b ]$$

choose adjoint circuit

$$Y_b^{aT} = Y_b$$


$$\Rightarrow i_a \cdot \delta v_a = + v_b^{aT} \cdot \delta Y_b \cdot v_b$$

if  $g_{ij}$  changes then  $v_a$  changes as  $\delta v_a = v_b^{aT} \cdot \delta g_{ij} \cdot v_b / i_a$

$\frac{\delta v_a}{\delta g_{ij}} = \frac{v_b^{aT} \cdot v_b}{i_a}$   $\Leftarrow$  no assumption on RLT side only circuit analysis


$$\frac{\delta v_a / v_a}{\delta g_{ij}} = \frac{\frac{\partial v_a / v_a}{\partial g_{ij}}}{\frac{v_a / v_a}{g_{ij}}} \Rightarrow S_x^T = \frac{\partial T / \partial x}{T/x} \text{ sensitivity of } T(x) \text{ w.r.t. } x$$

Ex:

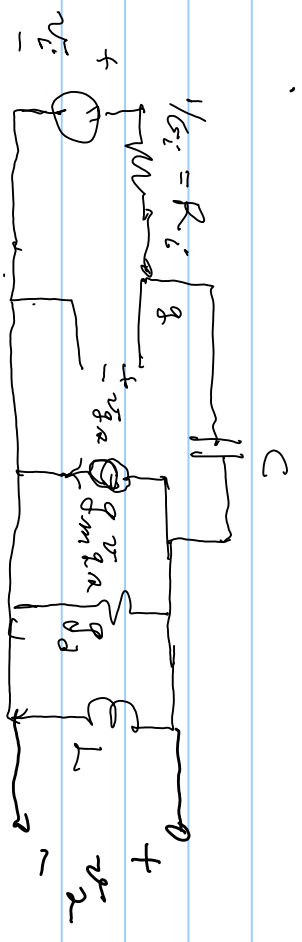

clears
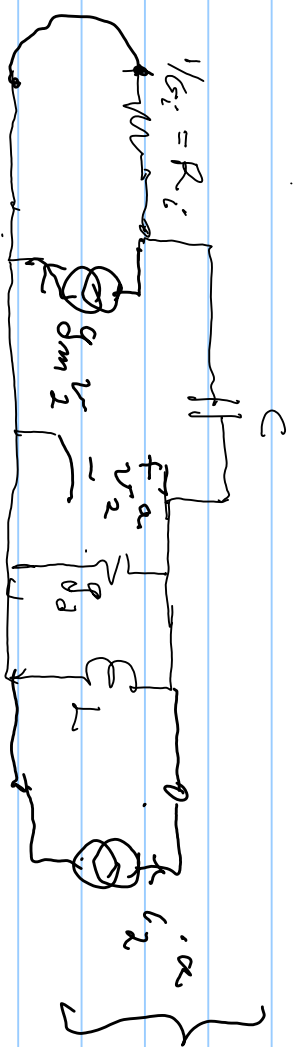
$$\frac{dv_2}{dg_m} = \frac{v_2 v_2^a}{i_2}$$



adjoint