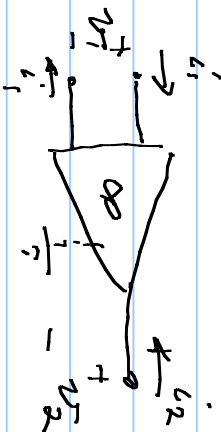



EE 610

09/22/15

op-amps (ideal)





$i_1 = 0$   
 $v_1 = 0$

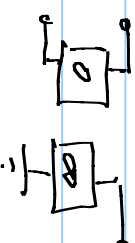

$$AV = B i$$

$$\begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

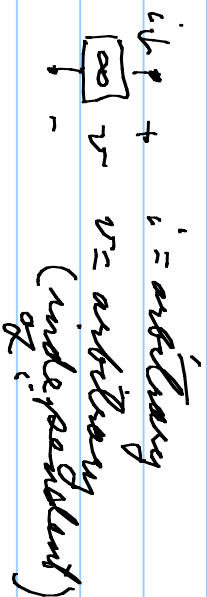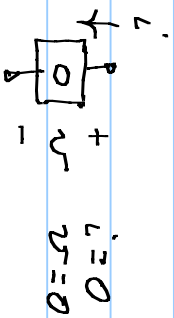$i = B^{-1} A v$ ;  $Y = B^{-1} A$   
 $v = A^{-1} B i$ ;  $Z = A^{-1} B$



multiplier


$$\begin{bmatrix} 1 \\ 0 \end{bmatrix} [v] = \begin{bmatrix} 0 \\ 1 \end{bmatrix} [i]$$

inverter

$$\begin{bmatrix} 0 \\ 1 \end{bmatrix} [v] = \begin{bmatrix} 0 \\ 0 \end{bmatrix} [i]$$

$i_1 = 0$  arbitrary  
 $v_1 = 0$  arbitrary (independent)  
or  $i_2$

design from state equations

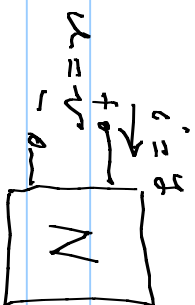


$$\dot{x} = Ax + Bu, \quad x = \text{e-vector}$$

$$y = Cx + Du \quad \text{design } N \text{ given state eqs.}$$

$x = v_c = \text{capacitor voltages}$
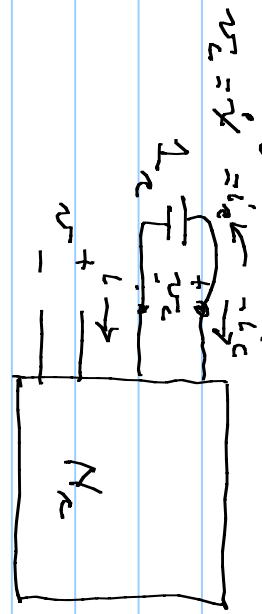
$$i_{\text{cap}} = Av_c + Bv = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_c \\ v \end{bmatrix} = \begin{bmatrix} i_{\text{cap}} \\ i \end{bmatrix} \Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} = Y$$



$$Y_c \cdot \begin{bmatrix} v_c \\ v \end{bmatrix} = \begin{bmatrix} -i_c \\ i \end{bmatrix}$$

$$Y_c = \begin{bmatrix} -A & -B \\ C & D \end{bmatrix}$$

constant  
com make  
with differential  
pairs

$$y = \frac{1}{s} (a) = D + C [sI_n - A]^{-1} B$$

Admittance

Example:  $y(s) = \frac{5s+3}{s^2+\omega_0 s+\omega_0^2} = D + C [sI_2 - A]^{-1} B$ ,  $D = y(\infty) = 0$  falls

$$sI_2 - A = \begin{bmatrix} s-0 & +1 \\ -\omega_0^2 & s+\omega_0/Q \end{bmatrix} \quad \det(sI_2 - A) = \text{denominator}$$

$$s^2 + \frac{\omega_0}{Q}s + \omega_0^2 = (s-0) \left( s + \frac{\omega_0}{Q} \right) - 1 (-\omega_0^2)$$

$$= s^2 + \frac{\omega_0}{Q}s + \omega_0^2$$

$$A = \begin{bmatrix} 0 & -1 \\ +\omega_0^2 & -\omega_0/Q \end{bmatrix}$$

$$\frac{5s+3}{s^2+\omega_0 s+\omega_0^2} = C (sI_2 - A)^{-1} B = [c_1 \ c_2] \frac{1}{s^2+\omega_0 s+\omega_0^2} \begin{bmatrix} s+\omega_0/Q & -1 \\ \omega_0^2 & s \end{bmatrix} \begin{bmatrix} b_1 \\ b_2 \end{bmatrix}$$

$$5s+3 = \text{numerator} = [c_1 \ c_2] \begin{bmatrix} s+\omega_0/Q & -1 \\ \omega_0^2 & s \end{bmatrix} \begin{bmatrix} b_1 \\ b_2 \end{bmatrix}$$


$$= [c_1 \ c_2] \begin{bmatrix} b_1(s+\omega_0/Q) - b_2 \\ \omega_0^2 b_1 + b_2 s \end{bmatrix} = c_1 b_1 (s+\omega_0/Q) - c_1 b_2 + c_2 \omega_0^2 b_1 + c_2 b_2 s$$

$$5R = c_1 b_1 R + c_2 b_2 R = (c_1 b_1 + c_2 b_2) R \quad \left. \begin{array}{l} \text{try } c_2 = 0 \\ c_1 (b_1 \omega_0 / Q - b_2) = 3 \end{array} \right\} \Rightarrow c_1 b_1 = 5$$

$$3 = c_1 b_1 \omega_0 / Q - c_1 b_2 + b_1 c_2 \omega_0^2$$

Let  $c_1 = 1, b_1 = 5 \Rightarrow 1 \cdot (5 \omega_0 / Q) - b_2 = 3 \Rightarrow b_2 = \frac{5 \omega_0}{Q} - 3$
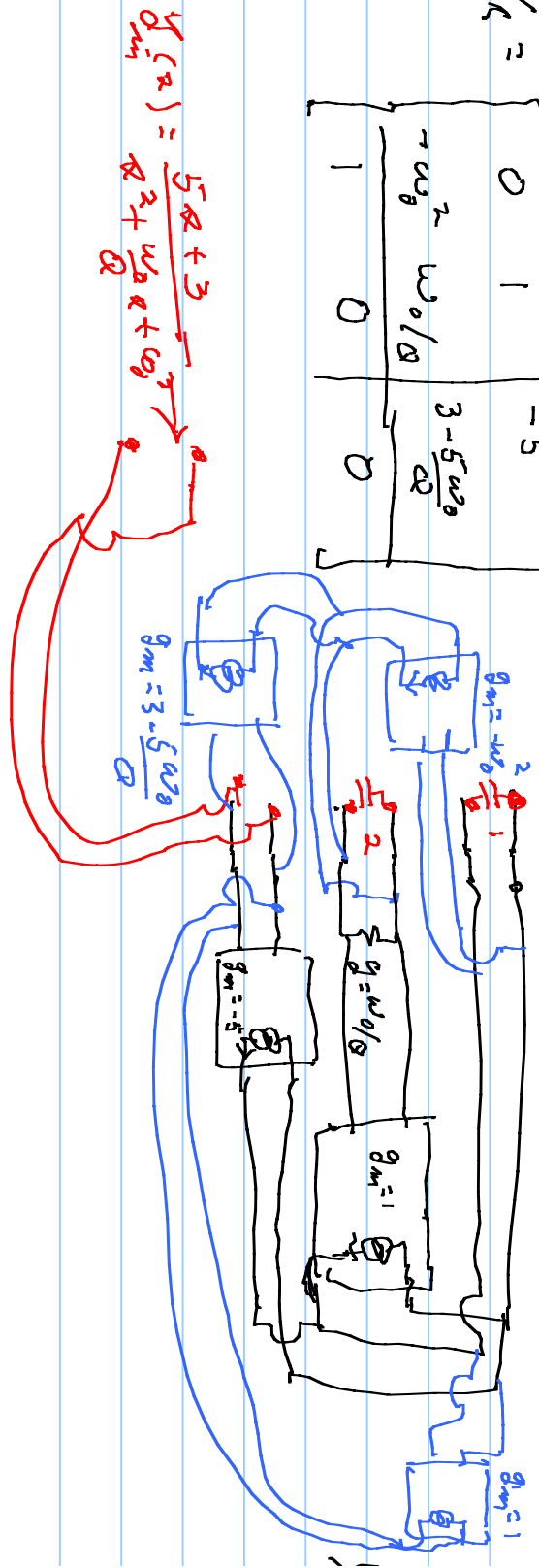
$$Y_R = \begin{bmatrix} 0 & 1 & -5 \\ -\omega_0^2 & \omega_0 / Q & 3 - \frac{5 \omega_0}{Q} \\ 1 & 0 & 0 \end{bmatrix}$$




$$Y_m(s) = \frac{5R + 3}{s^2 + \omega_0/Q + \omega_0^2}$$

If  $x = v_2$  &  $u = v_1$  then  $T(a)$ .  $v_1 = v_2$

$$\dot{x}_a = Ax_a + Bv_1$$

$$v_2 = Cx_a + Dv_1$$

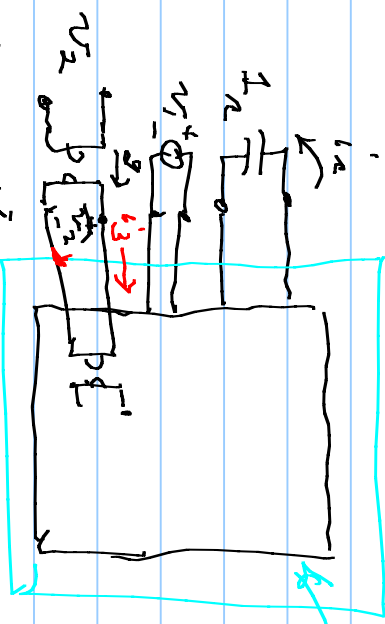

leave admittance of this  
make as  $Y_c$   
attach gyrator for  
3rd ports

choose gyrator

$$-x_0 = \begin{bmatrix} -i_c \\ i_{v_1} \\ i_3 = v_2 \end{bmatrix} = \begin{bmatrix} -A - B \\ D_a \\ C \end{bmatrix} \begin{bmatrix} x_a \\ v_1 \\ v_2 \end{bmatrix}$$

$g$  or  $i_3 = v_2$ ;  $+g = 1 \Rightarrow i_3 = v_2 = i_{g_2} = g v_1$

$D_c =$  don't care  
choose to give nice answer

$$\begin{bmatrix} -i_c \\ i_{v_1} \\ i_3 = v_2 \end{bmatrix} = \begin{bmatrix} -A - B & D_c \\ D_a & D_c \\ C & D \end{bmatrix} \begin{bmatrix} x_a \\ v_1 \\ v_2 \end{bmatrix}$$

choose

$$Y_c = \begin{bmatrix} A & -B & -C^T \\ B^T & 0 & -D^T \\ C & D & 0 \end{bmatrix}$$

build this

