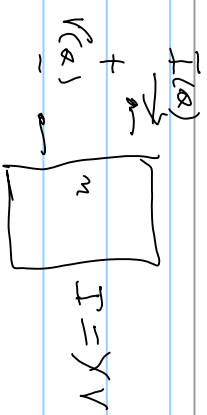


Low rank synthesis of passive 1-ports



$$P_{ave}(g(j\omega)) = \text{Re} \left[ V^*(j\omega) I(j\omega) \right] = \frac{1}{2} \left[ V^* I + (V I^*)^T \right] \frac{1}{2}$$

$$= \frac{1}{2} \left[ V^* I + I^* V \right] \frac{1}{2}$$

$\frac{1}{2} \left[ V^* Y(j\omega) V + V^* Y^*(j\omega) V \right] \frac{1}{2} = 0$  if lossless

$$V^* \left[ Y(j\omega) + Y^*(j\omega) \right] V = 0 \Rightarrow Y(j\omega) + Y^*(j\omega) = 0_n$$

If rational & PR means real for real  $\omega > 0$

$$L(x) : y(x) = \frac{m(x)}{d(x)} = \frac{m^m + m^{m-1} + \dots + m_0 x^0}{d^m + d^{m-1} + \dots + d_0 x^0}$$

$m_i$  &  $d_i$  real

If  $y(j\omega)$  is conjugate real  $\Rightarrow y^*(j\omega) = y(-j\omega)$  as  $\uparrow$

$$y(j\omega) + y^*(j\omega) = \left[ y(a) + y(-a) \right] \text{ if } a = j\omega = 0 \text{ for } a = j\omega$$

$\Rightarrow$  0 for all  $\alpha$  any analytic continuation  $\alpha = 0$  on a dense set of  $\alpha = j\omega$   $y(\alpha) = -y(-\alpha)$

if a pole of  $y(-\alpha)$  it is also a pole of  $y(\alpha) \Rightarrow$  no poles of a transfer function

$z(\alpha)$  in the LHP or RHP also true for  $z(\alpha) = 1/y(\alpha)$

$\Rightarrow$  also no zeros of  $y(\alpha)$  ( $z(z(\alpha))$  in LHP or RHP)



These are singular as a multiple pole leads to stability

$$y(\alpha) \approx \frac{k}{(\alpha - j\omega_0)^m} \dots$$

$\text{Re } y(\alpha) > 0$  in the RHP

$$\text{Re } y(\alpha) = \frac{1}{|\alpha - j\omega_0|^m} \text{Re } k$$

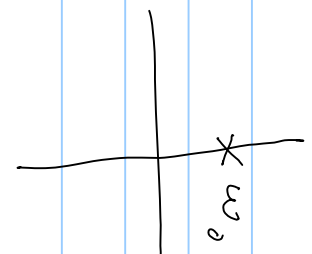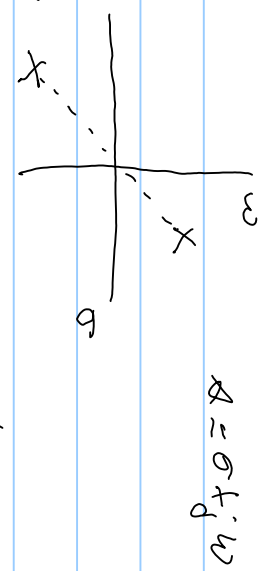near  $\alpha = j\omega$  but with  $\sigma > 0$



$$y(x) = \frac{\text{Re} \{ e^{ix} \}}{(\text{Im} \{ e^{i(x-k)m} \})^n} = \frac{|k|}{|k|} e^{j(x-k-mk)} \cdot \frac{1}{|k|} e^{j(x-k-mk)}$$

$-\frac{\pi}{2} < \theta < \frac{\pi}{2}$

Re  $y(x)$  will get negative if  $\cos(x-k-mk)$  is  $< 0$   
 means  $m=1$  &  $k=0$


means a pole  $y(x) = \frac{k}{A-j\omega_0} + \frac{k}{(A+j\omega_0)}$  + (... ) same for all poles

$$y(x) = \frac{2kA + j\omega_0 k - k j \omega_0}{(A+j\omega_0)(A-j\omega_0)} + \dots = \frac{2kA}{A^2 + \omega_0^2} + \dots = \frac{k\omega_0}{A} + k\omega_0 A$$

Similarly  $y(x) = \frac{k\omega_0}{A} + k\omega_0 A + \sum_{l=1}^{m-1} \frac{2k_l A}{A^2 + \omega_l^2}$


$$y_1 = \frac{2k_1 A}{A^2 + \omega_1^2} = \frac{1}{\frac{A^2}{2k_1 A} + \frac{\omega_1^2}{2k_1 A}} = \frac{1}{\frac{A}{2k_1} + \frac{1}{\frac{2k_1 A}{\omega_1^2}}} = \frac{1}{\frac{1}{\omega_1^2} + \frac{1}{\omega_2^2}}$$

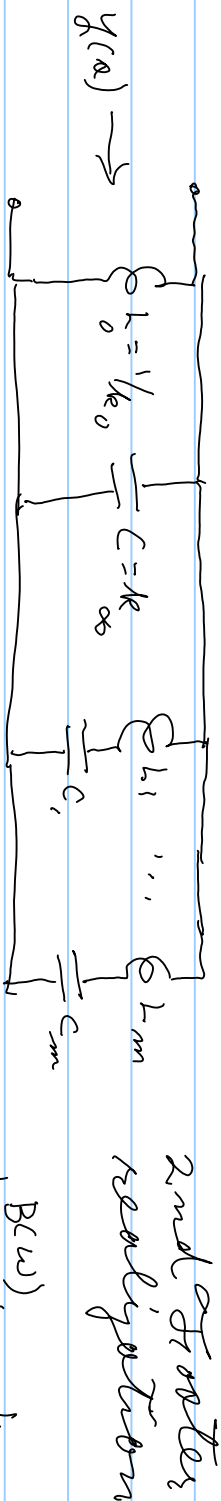synthesizing  $Y(s)$  by parallel active elements circuit



$$Y(s) = j B(\omega)$$
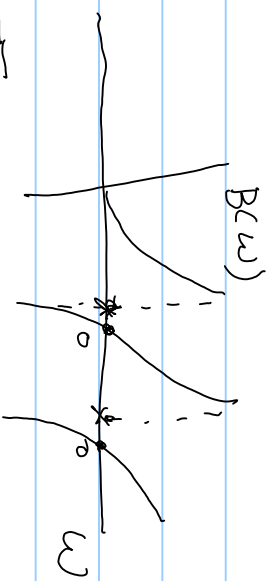
$$\frac{dB(\omega)}{d\omega} ; \quad B(\omega) = -\frac{k_0}{\omega} + k_{\infty} \omega + \sum_{i=1}^m \frac{2k_i \omega}{-\omega^2 + \omega_i^2}$$



$$\begin{aligned} \frac{dB(\omega)}{d\omega} &= -\left(-\frac{1}{\omega^2}\right) k_0 + k_{\infty} + \sum_{i=1}^m \frac{2k_i \omega_i}{(-\omega^2 + \omega_i^2)^2} + \overset{-2\omega}{\times} \frac{k_i \omega_i}{(-\omega^2 + \omega_i^2)^2} (-2\omega) \\ &\approx \frac{1}{\omega^2} k_0 + k_{\infty} + \sum_{i=1}^m \frac{2k_i \omega_i \left[ (-\omega^2 + \omega_i^2) + 2\omega^2 \right]}{(-\omega^2 + \omega_i^2)^2} \\ &= \frac{1}{\omega^2} k_0 + k_{\infty} + \sum_{i=1}^m \frac{2k_i (\omega^2 + \omega_i^2)}{(-\omega^2 + \omega_i^2)^2} > 0 \end{aligned}$$

$\Rightarrow$  poles & zeros alternate;  $Y(s) = -Y(-s) \Rightarrow$  odd


$$g(r) = \frac{r(r^2+2)}{(r^2+1)} \quad \text{no PR zeros}$$

$$= r + \frac{2kr_1}{r^2+1} \quad \times \frac{r^{2+1}}{r} \Rightarrow r^2+2 = g(r) = \frac{r(r^2+1)}{r} + 2k_1$$

$$= r + \frac{r}{r^2+1} \quad \text{set } r^2 = -1 \Rightarrow 2k_1$$

$$= r + \frac{r}{r^2+1} \quad r^2+2 = -1+2 = 2k_1, \quad k_1 = 1/2 > 0$$

$$= r + \frac{r}{r^2+1} \quad r^2 < -1$$

$$\approx \frac{r^3 + r + r}{r^2+1} = r \frac{(r^2+2)}{r^2+1} \Rightarrow g(r)$$


$$y_1 = \frac{r}{r^2+1} = \frac{1}{r + 1/r}$$

1st order  $\Rightarrow$  dual  $z(r) = k_{r0} + k_{r1}r + \sum_{i=1}^m \frac{2k_i \cdot r}{r^2 + \omega_i^2}$

$$z(r) = \frac{r^2+1}{r(r^2+2)} = \frac{k_{r0}}{r} + \frac{2k_1 r}{r^2+2} = \frac{k_{r0}}{r} + \frac{k_1}{r+j\sqrt{2}} + \frac{k_1}{r-j\sqrt{2}}$$

$$k_{r0} \Rightarrow r z(r) = \frac{r^2+1}{r^2+2} = k_{r0} + \frac{2k_1 r}{r^2+2} = k_{r0} = r z(r) = \frac{r^2+1}{r^2+2} = 1/2$$


$r=0 \qquad r=0$

$$\sqrt{k} \Rightarrow \frac{R^2 + 2}{2R} \cdot Z(R) = \frac{R^2 + 1}{2R^2} = \frac{R^2(R^2 + 2)}{2R^2} + \sqrt{k}$$

$$\text{set } R^2 = -2$$

$$\Rightarrow \frac{-2+1}{2(-2)} = \frac{-1}{-4} = \frac{1}{4} = 0 + \sqrt{k} \Rightarrow \sqrt{k} = 1/4$$
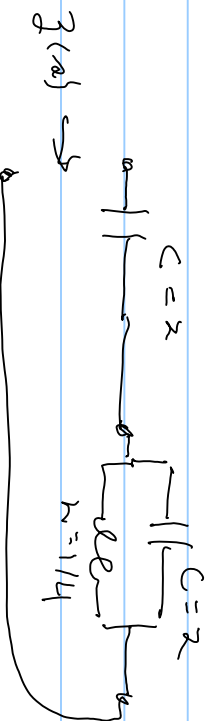
$$Z(R) = \frac{R^2 + 1}{R(R^2 + 2)} = \frac{1}{2R} + \frac{2R \times 1/4 R}{R^2 + 2} = \frac{1}{2R} + \frac{1/2 R}{R^2 + 2} = \frac{1}{2R} + \frac{1}{2R + 4/2}$$



1st trials form

$\delta[y(s)] = \text{degree} = 3 = \delta[Z(s)] \Rightarrow$  need at least 3 components  
 at we need the minimum  
 numbers  $\approx$  canonical