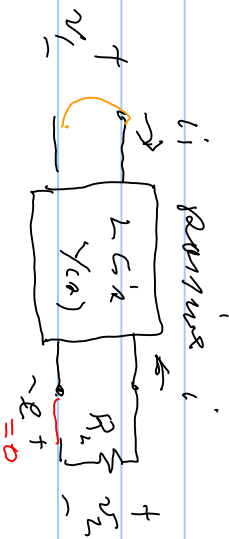


EE 610
10/08/15

Transfer polynomial: $\sigma > 0$, $P(s)$, $\sigma = \sigma + j\omega$
 (8 simple if on $j\omega$ axis) \Rightarrow if none on $\sigma = j\omega \Rightarrow$ strictly Hurwitz



y_{or2} is a loadless PR function

$$i_1 = y_{11} v_1 + y_{12} v_2 \quad \text{if } v_1 = 0$$

$$i_2 = y_{21} v_1 + y_{22} v_2 \quad i_2 = y_{22} v_2$$

shunting point
loadless $y(s)$

$$e = R_L i_2 + v_2 = \frac{e - v_2}{R_L} = i_2 \Rightarrow e = \frac{1}{y_{22}} + R_L i_2$$

$$i_2 = \frac{y_{22} e}{1 + R_L y_{22}} \Rightarrow \text{if } e = 0 \Rightarrow i_2 \neq 0 \text{ all zeros of } 1 + R_L y_{22}$$

want be on $j\omega$ axis as R_L damp them.

$$\text{Let } 1 + R_L y_{22} = \frac{M}{d} = 1 + R_L M_{22} / d_{22} = \frac{d_{22} + R_L M_{22}}{d_{22}} = \frac{P(a)}{d_{22}}$$

$$P(a) \text{ is identity} = E_S(P(a)) + \Theta_{dL}(P(a)) = E(a) + \Theta(a) \\ = E(a) [1 + \Theta(a)/E(a)] = E(a) [1 + y(a)] = O(a) [1 + \frac{E(a)}{2}]$$

\Rightarrow if $P(a)$ is identity then can get a lower PR
PR $y(a)$ as $\Theta(a)/E(a)$ or $E(a)/O(a)$

$$\text{Ex: } P(a) = a^4 + 2a^3 + 3a^2 + 3a + 2 = (a^4 + 3a^2 + 2) + (2a^3 + 3a)$$


$$y(a) = \frac{2a(a^2 + 3/2)}{a^4 + 3a^2 + 2} \quad \text{is this lower PR}$$

$$\text{Let } z(a) = \frac{1}{y(a)} = \frac{2a^3 + 3a}{2a(a^2 + 3/2)} = \frac{1}{2} a \frac{a^4 + 3a^2 + 2}{a^4 + 3/2 a^2} \\ \frac{3}{2} = \frac{(3 - \frac{3}{2})a^2 + 2}{2a^3 + 3a}$$


$$2a^3 + 3a \quad \frac{1}{2} a \\ \frac{9-8}{3} \quad a = \frac{1}{3} a \quad \frac{3a^2 + 2}{2} \quad \frac{1}{3} a \\ \frac{3a^2}{2} \quad \frac{1}{3} a \\ \frac{2}{2} \quad \frac{1}{3} a$$

$$y(s) = \frac{1}{\frac{1}{2}s + \frac{4}{3}} + \frac{1}{\frac{1}{2}s + \frac{1}{2}}$$

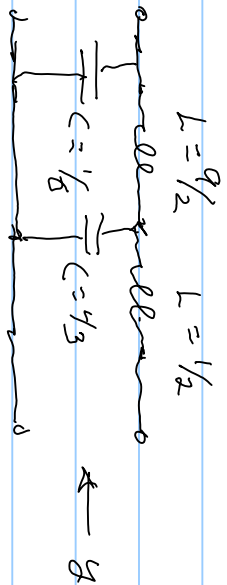as this can be split from a passive LC circuit, $P(s)$ is strictly Hurwitz



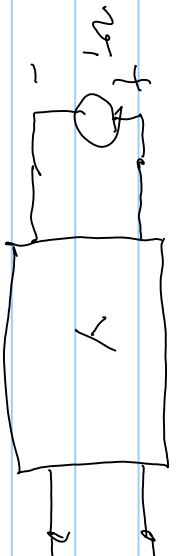had all zeros for an g_{21} @ ∞ (as can't synthesize remember poles there)



$$v_2 = y_{21} v_1 + y_{22} v_2 = -G_L v_2$$

$$\Rightarrow y_{21} v_1 = -(G_L + y_{22}) v_2$$

$$\frac{v_2}{v_1} = \frac{-y_{21}}{G_L + y_{22}} = \frac{-y_{21} R_L}{1 + R_L y_{22}}$$

normalize $R_L = 1$

$$\frac{v_2}{v_1} = \frac{-y_{21}}{1 + y_{22}} = \frac{-m_{21}/d_{21}}{1 + m_{22}/d_{22}} = \frac{d_{22} \cdot (-m_{21})}{d_{21} (m_{22} + d_{22})}$$

assume $d_{z1} = d_{z2}$ then $A_{D^2}(a) = \frac{D_2^2}{D_1^2} = \frac{-a^2 z_1}{a^2 z_2 + d_{z2}}$

So: $A_{D^2}(a) = \frac{-(a^2+4)}{a^4+2a^3+3a^2+3a+2} = \frac{-(a^2+4)}{1+2a^3+3a}$

$P(a) = (a^2+1)(a^2+2)$ a^4+3a^2+2

$q(a) = \frac{2a(a^2+3/2)}{(a^2+1)(a^2+2)}$ need a different synthesis way

1st cover removes poles @ ∞

2nd cover " " " " @ ∞

1st of poles " " of $3(a)$

and " " " " of $q(a)$

max positive pole removals to get zeros of h_1 or other points of $j\omega$ axis





drive to shift curve down
by an operation of part of
the poles @ ∞

$$\frac{1}{y(s)} - L R = \frac{R^4 + 3R^2 + 2}{2R^3 + 3R} - L R = \frac{P(R)}{2R^3 + 3R}$$

$$P(R^2 = -4) = 0$$

$$= \frac{R^4 + 3R^2 + 2 - 2R^4 - L3R^2}{2R^3 + 3R}$$

$$= \frac{16 - 12 + 2 - 32L + 12L}{R(-8+3)} \stackrel{x_D}{=} 0$$


$$R^2 = -4 \Rightarrow 6 - 20L = 0 \Rightarrow L = 3/10$$

$$Z_1(R) = \frac{R^4 + 3R^2 + 2}{2R^3 + 3R} \rightarrow \frac{3}{10} R =$$

$$= \frac{R^4 + 3R^2 + 2 - \frac{3}{5}R^4 - \frac{9}{5}R^2}{2R^3 + 3R}$$

$$= \frac{\frac{2}{5}R^4 + \frac{21}{10}R^2 + 2}{2R^3 + 3R} = \frac{(R^2 + 4)(R^2 + 6)}{(2R^3 + 3R)}$$
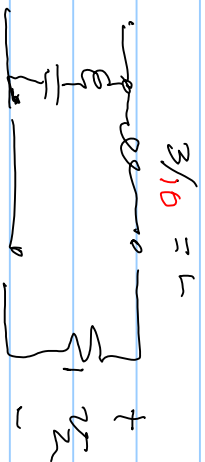
$$= \frac{(R^2 + 4)(\frac{2}{5}R^2 + 1/2)}{2R^3 + 3R}$$



$$y = \frac{2R R}{R^2 + 4} + \dots$$

$$\frac{a^2+4}{\frac{2}{5}a^2 + \frac{1}{2}} \Rightarrow \frac{1}{\frac{2}{5}a^2 + \frac{1}{2}} = \frac{2a^3+3a}{(a^2+4)\frac{2}{5}(a^2+\frac{5}{4})} = \text{answer of } a_2$$

$$y_2 = \frac{k_1 a}{a^2+4} + \frac{k_2 a}{a^2+\frac{5}{4}}$$

$$k_1 = y_2 \times (a^2+4) \Big|_{a^2=-4} = \frac{2a^2+3}{\frac{2}{5}(a^2+\frac{5}{4})} \Big|_{a^2=-4} = \frac{-8+3}{\frac{2}{5}(-\frac{16+5}{4})} = \frac{5}{2} \frac{(-5)}{(-\frac{11}{4})} = \frac{25}{1/2} = \frac{50}{11}$$

created this problem