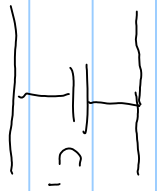




$$A_{y_2}(a) = \frac{(a^2+4)}{a^4+2a^3+3a^2+3a+2} = \frac{1}{1 + \frac{(a^2+4)(2a^3+3a)}{2a^3+3a}} = \frac{-y_{21}}{1+y_{22}} \quad R_L = 1 \Omega \text{ normalized}$$

$$y_{22} = \frac{(a^2+1)(a^2+2)}{2a(a^2+3/a)} \quad \text{PR load}$$




$$z_2 = \frac{1}{y_{22}} = \frac{2ka}{a^2+4} + \frac{ak_2}{a^2+a}$$

split

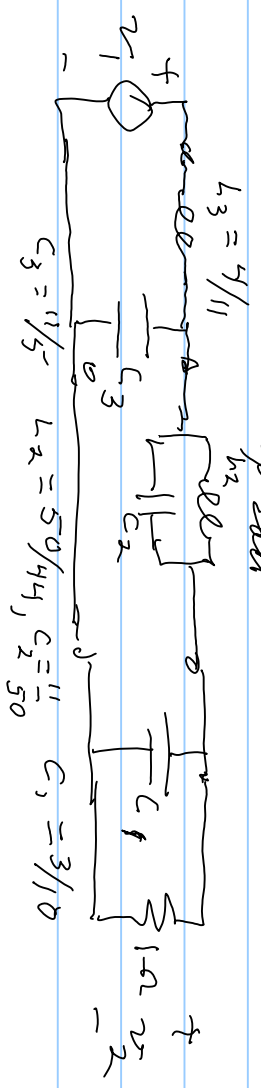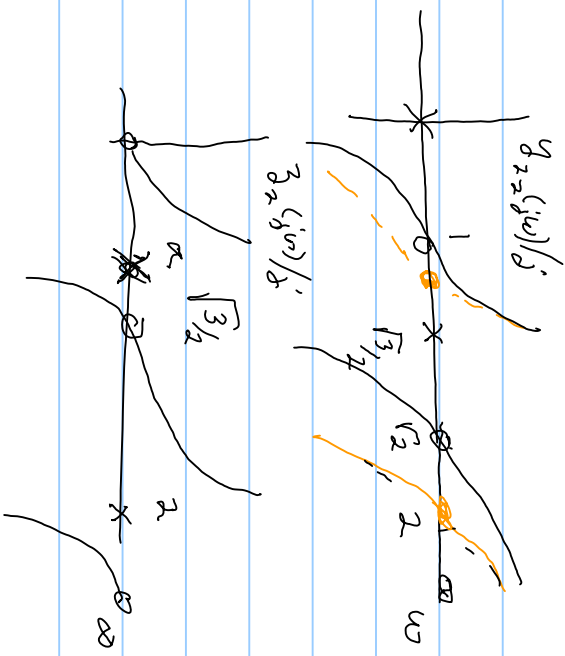

$$y_{22} - y_{21} = \frac{1}{2} \frac{(a^2+4)}{(a^2+3/a)}$$

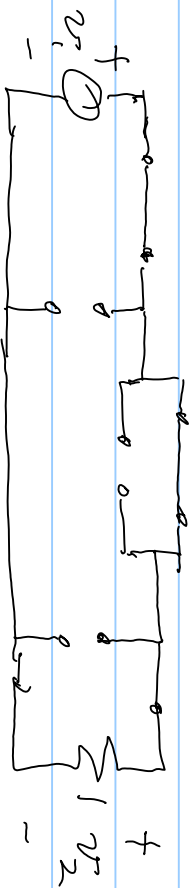
To find R_0 : $H_{VS}(0) = R_0 \times 4/2$



$$\frac{v_2}{v_1}(0) = 1 = R_0 \cdot 2 \Rightarrow R_0 = 1/2$$

$$A_{VS} = \frac{\frac{1}{2}(R^2 + 4)}{R^4 + 2R^3 + 3R^2 + 3R + 2} = \frac{1/2}{2/2} \begin{bmatrix} g_{11} & -g_{12} \\ -g_{21} & g_{22} \end{bmatrix}$$

Why is R_{21} odd:

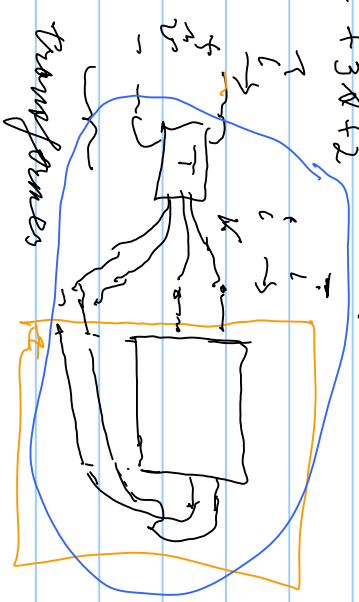

$$i = \gamma v$$

$v^T i + v^T \gamma i = 0$ = Total power inter

$$\begin{aligned} v^T &= T^T v & i &= v^T T \cdot i + v^T \gamma i = 0 & \text{for all } v & \text{Transformers} \\ \gamma &= -T^T \gamma & & \Rightarrow \gamma &= -T^T \gamma & \end{aligned}$$

$$\vec{I} = Y \vec{V} \approx -\vec{I} = + T^{-T} \vec{I} = Y^T \vec{V} \Rightarrow \vec{I} = T^T Y^T \vec{V}$$

$$\vec{Y} = T^T Y^T$$

Ass: $T = \begin{bmatrix} t_1 \\ t_2 \end{bmatrix}$ as $\vec{V} = 1$ port voltage

$$\vec{Y} = \begin{bmatrix} t_1 & t_2 \end{bmatrix} \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} t_1 \\ t_2 \end{bmatrix} = t_1^2 y_{11} + t_2^2 y_{22} + 2 t_1 t_2 (y_{12} + y_{21})$$

if Y is lossless 2-port then \vec{Y} is a lossless positive-real function if a ladder $\vec{Y} \in PR$, $y_{21} = y_{12}$ if a ladder as the 2-port is reciprocal & real residues

$$y_{11} = t_1^2 y_{11} + t_2^2 y_{22} + 2 t_1 t_2 y_{21} \Rightarrow \text{simple poles on } j\omega \text{ axis, positive \& real residues}$$

Here y_{11} must have simple $j\omega$ poles with real residues $\Rightarrow y_{21}$ is an odd function of ω with its poles contained

in y_{11} and y_{22} and near a pole, residues matrix is positive semi-definite $K = \begin{bmatrix} K_{11} & K_{12} \\ K_{12} & K_{22} \end{bmatrix}$
 $K_{11} \geq 0, K_{22} \geq 0, \det = K_{11}K_{22} - K_{12}^2 \geq 0$

Richards' functions p. 361

$$R(a) = \frac{Rz(a) - aZ(a)}{Rz(a) - aZ(a)}$$

$R(a)$ is PR if $Z(a)$ is PR we $a-k$ cancels $\delta[R(a)] = \delta[Z(a)]$

unless another cancellation occurs

This happens if $Z(a) = -Z(-a)$ then $a+k$ cancels
then $\delta[R(a)] = \delta[Z(a)] - 1$