

EE610

10/15/15

Note Title

10/15/2015

$$R(a) = \frac{Rz(a) - aZ(a)}{Rz(a) - aZ(a)} \quad \text{is PR if } z(a) \text{ is } \& k \text{ is real } \& \omega > 0$$

for Bode - Bode gain asymptotes use this:

$$\text{asymptote for } (Rz(k) - aZ(a))R(a) = kZ(a) - aZ(k)$$

$$z(a) (-aR(a) - k) = -aZ(k) - kZ(a)R(a)$$

$$z(a) = \frac{R \cdot Z(k) + kZ(a)R(a)}{k + aR(a)} = \frac{1}{\frac{k + aR(a)}{RZ(k)}} + \frac{1}{\frac{k + aR(a)}{RZ(k)R(a)}}$$

$$\Rightarrow y = \frac{s}{k_a} + \frac{1}{\frac{k \cdot a}{a^2 + \omega^2} + R_2} = \frac{1}{\frac{1}{R \cdot Z(k)} + \frac{1}{Z(a)R(a)}} + \frac{1}{\frac{1}{Z(a)R(a)} + \frac{a}{kZ(k)R(a)}}$$

before using $R(a) = z(a)$ extract all poles and zeros on $j\omega$ axis, on $j\omega$ axis, real part has a minimum of z after remove poles, $z(j\omega) = R(\omega) + jX(\omega) \Rightarrow R(\omega) = \text{minimum}$

Refract out $R(\omega) \geq 0 \Rightarrow$ positive (if so) resistances
 \Rightarrow passive

given $Z(s)$ that is minimum \Rightarrow PR, no poles or zeros on
 purely $R(s)$ for this minimum $Z(s)$
 $Z'(s) = jX_1$

$$R(j\omega_1) = \operatorname{Re} Z(j\omega) - \frac{j\omega_1 Z'(k_1)}{k_1 Z'(k_1) - j\omega_1 Z'(j\omega_1)} = \frac{j k_1 X_1 - j\omega_1 Z'(k_1)}{k_1 Z'(k_1) - j\omega_1 Z'(j\omega_1)} = \frac{j(k_1 X_1 - \omega_1 Z'(k_1))}{k_1 Z'(k_1) - j\omega_1 Z'(j\omega_1)}$$

assume $X_1 > 0$ (if not use denominator)


choose $k_1 X_1 = \omega_1 Z'(k_1) \Rightarrow k_1 = \frac{\omega_1}{X_1} Z'(k_1)$

then $R(\omega_1) = 0$

$k = k_1$ this means $Z(s) = \frac{1}{sR(s)}$ is PR with a pole at $s = \pm j\omega_1$



$$y = \frac{ka}{a^2 + w^2}$$

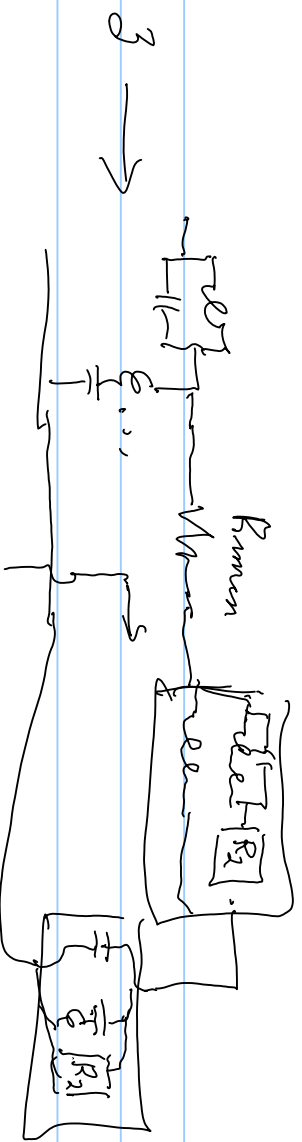

continuous R_2
 R_2 is PR
 synthesizes any
 PR function
 as $S[R_2] < S[1] = S[R_2]$

Both Bode gives a Transfer function
 of any PR function.

For a lossless PR $y(a) = 1/z(a)$ comes $R(a)$ by k zeros of

Let a cancellation of $k - a^2$ if k is a zero of $S(z(a))$
 $z(z(a)) = z(a) + z(-a)$ if k is a zero of $S(z(a))$ then $z(k) = -z(-k)$



$$R(a) = \frac{kz(a) - a^2z(k)}{kz(k) - a^2z(a)}$$

$a = -k$

$$= \frac{kz(-k) - (-k)z(k)}{kz(k) - (-k)z(-k)} = \frac{k(-z(k)) + kz(k)}{kz(k) + (-z(-k))} = \frac{0}{0}$$

if k is a zero of $S(z(a))$

zeros of $Z_3(s)$

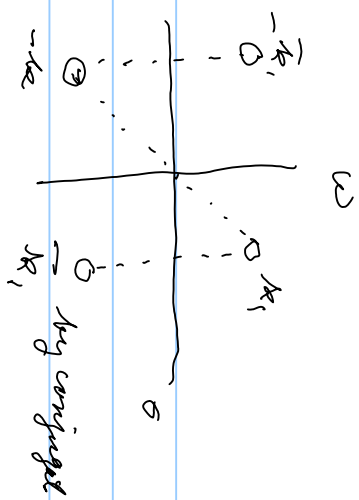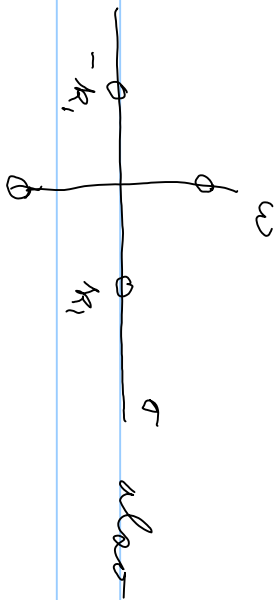


PR lossless $Y(s) = -Y(-s)$


$$= \sum \frac{2k_i \alpha}{\alpha^2 + \omega_i^2} + k_0 \alpha + \frac{k_0}{\alpha} \Rightarrow \text{odd if lossless}$$

\Rightarrow any $\alpha = k$ will cancel $\alpha^2 - k^2$ in a lossless PR $Y \rightarrow R(s)$.

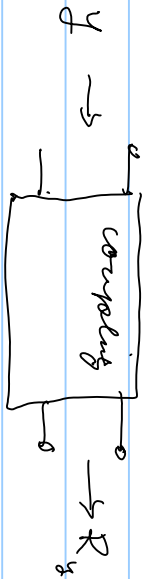\therefore need a coupling circuit to get $Y(s)$ to $R(s)$





Both-Duffin gives

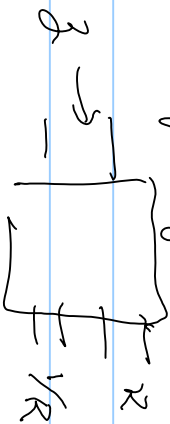

$$R_{3(s)} = \frac{K_3(s) - a_3(s)}{R_3(s) - a_3(s)} \Rightarrow \text{let } z = 1/y \Rightarrow \frac{K \frac{1}{g(s)} - a \frac{1}{g(s)}}{\frac{K \frac{1}{g(s)} - a \frac{1}{g(s)}}{g(s)} - a \frac{1}{g(s)}} = \frac{K y(s) - a y(s)}{K y(s) - a y(s)}$$

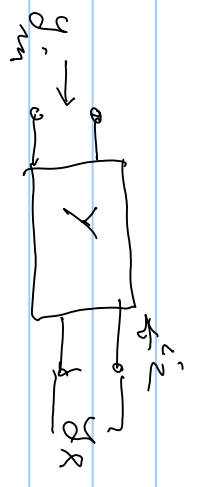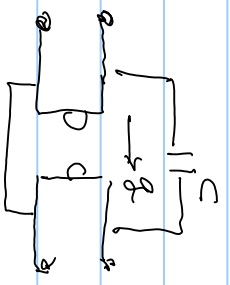also $1/R(s)$ no PR $\Rightarrow R_y(s) = \frac{K y(s) - a y(s)}{K y(s) - a y(s)}$



$$Y = \begin{bmatrix} c_a & -c_a - g \\ -c_a + g & a_a \end{bmatrix}$$

$$-y_{22} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$(-y_{22} - y_{22}) v_2 = g_{21} v_1$$

$$v_1 = y_{21} v_2 = \frac{y_{12} y_{22} v_2}{g_{21} + y_{22}}$$

$$\Delta y + y_{22} y_{11} = g + a c y_{22}$$

$$y_{in} y_{22} + a c y_{in} = g + a c y_{22} \Rightarrow y_{22} = \frac{g + a c y_{22}}{g_{21} + y_{22}} \Rightarrow y_{22} = \frac{g + a c y_{22}}{g(s) - a c}$$

$$R_g = \frac{K_g(k_e) - K_g(r)}{K_g(r) - K_g(k_e)} \times g(k_e) \Rightarrow \text{given } k_e, g(k_e) \text{ as element of } r \text{ has}$$