


303H Fall 2016 – Homework 1 Due Tu 09/13/16

The PARAM part is in the SPECIAL library

1. (40 points, Diode DC curves) [note some data will be used in problem 2]
 - a) In Spice do a DC run to get the DC diode curves of i_D versus v_D for the 1N4001 diode, submitting your curve. Compare the 1N4001 model with that of the 1N4007.
 - b) Repeat the curves for the npn transistor 2N3904 formed into a diode by connecting the collector to the base.
 - c) Repeat part b) but with the diode formed by connecting the emitter to the base.
 - d) Comment on differences and why they come about.

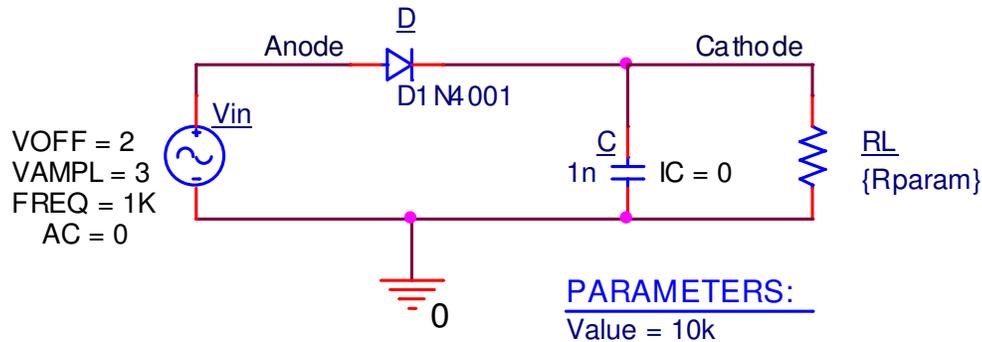2. (60 points, Diode biasing and ac & transient analysis).

Set up the following circuit in Spice (but first with a DC source). Then do a DC run on V_{in} (about 0 to 3V) along with a parametric run to find R_L to give a diode current of 2mA when $V_{in}=2V$ DC.



- a) Record 1) the resistance R_{Lbias} of the resistor R_L for the diode current to be 2mA, when the input DC voltage is 2V, 2) the diode voltage, V_{dio} , at this diode current Q point, and 3) the conductance (slope), g_d , of the diode current vs diode voltage at this Q point (use the curves of problem 1)..
- b) Make R_L the value found for the above Q point. Set up, and submit, the small signal differential equation when the initial value of the capacitor voltage is $2+V_{dio}$.
- c) Do a transient analysis for about 4mSec in PSpice with a 3V amplitude sin input at 1KHerz with the capacitor IC value = 0. Submit your transient analysis curves of diode cathode voltage (with respect to ground) and diode current [best obtained as two plots of one run].