

303H Fall 2016 – Homework 4 Due Tu 10/11/16

For the following problems assume a 9Volt battery available.

1. (50 points, BJT CE design)
 - a) Design a common emitter amplifier using a 2N3904 transistor for a voltage gain of $A_v = -20$ with the collector current near 10mA.
 - b) Check your design by running Spice with sinusoidal input signals at a frequency near 10KHerz. .
 - c) In Spice do a frequency response, looking at magnitude and phase from 10Hz to 1GHerz (on a log of frequency scale) and comment on the results.

2. (50 points, current mirrors)

For transistors use 2N3904, 2N3906, and BiCMOS12 0.5u transistors

 - a. Using resistors and transistors design four current mirrors to mirror 10mA, two for sinking and two for sourcing, one of each of these two using BJTs.
 - b. Repeat but for 10uA using CMOS.
 - c. Check your designs in Spice by placing a resistor load on an output transistor and comment upon what values of the load the circuit acts as a valid mirror.
 - d. By replacing the current determining resistor by a PMOS transistor, repeat the above two parts for the current sinking MOS mirror.
 - e. Repeat part c. for a CMOS sink made as a cascade.