

303H Fall 2016 – Homework 5 Due Tu 10/25/16 (two weeks)

1. (100 points; VCO)

Design a VCO using the circuits in the report of Liang Dai “Low Phase Noise Voltage-Controlled Oscillator” Using the 0.5micron transistor models in the bicmosis12 Spice library; these are the HP05L7N & HP05L7P [use no dimension for W or L than 2micon=2u].

The end result is a transistorization of the VCO block diagram of Figure 10.

- a) Use the first type of loads of Figure 1, the (a) diode connected MOS, and individually design and test each component (the inverters and the multipliers) before inserting them in the final circuit. Choose bias battery voltages of  $V_{DD}=3V=-V_{SS}$ .
- b) Test the full circuit in Spice submitting the oscillations and showing them when voltage controlled.

Justify your design choices and their effect on the VCO's behavior. Compare your results with those predicted by the equations in the Dai report.