

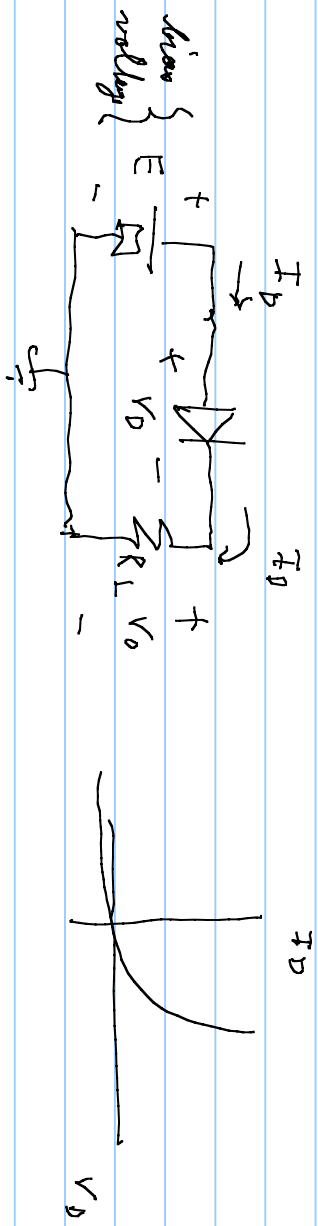


EE 303H
09/06/16

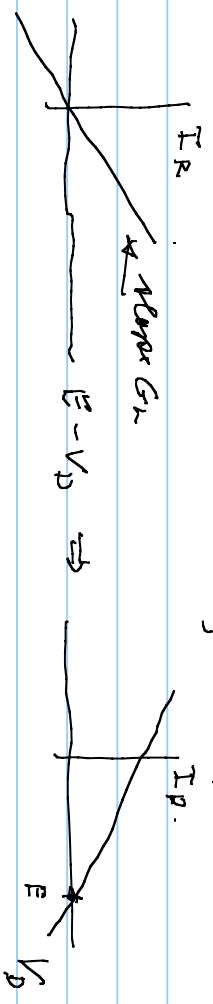
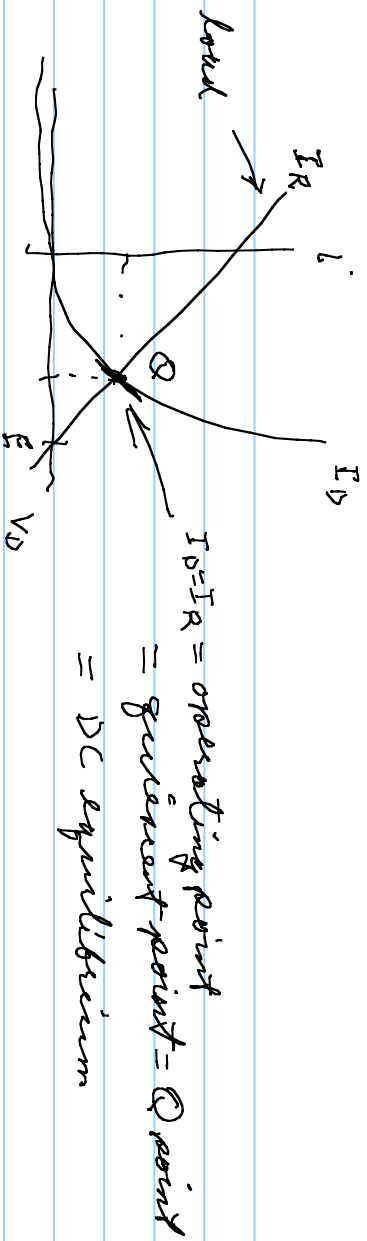
$$I_D = I_R = G_L \cdot V_0 = G_L (E - V_D) \quad , \quad G_L = 1/R_L$$





$$I_A (e^{V_D/V_T} - 1) = G_T (E - V_D)$$

also Spice for DC circuit, secondary sweeps, PARAM part