
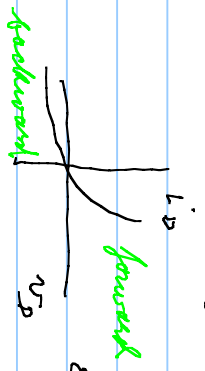


EE303H  
09/08/16

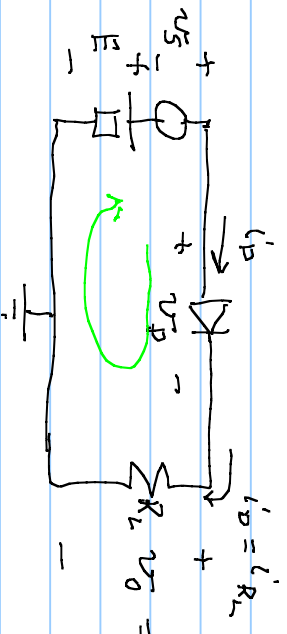Small linear, Q point, etc but goes over chapters 5 on MOS, eq. (5.16) & (5.23)





Eq. for small-signal model  
 $i_D \approx I_{DQ} (e^{v_{DQ}/V_T} - 1)$   
 thus in saturation



$+v_D + v_S - E - v_S = 0$  by KVL  
 $v_D = E + v_S - v_S$

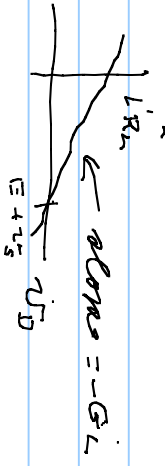
$R_L i'_D = G_L v_D = G_L (E + v_S - v_D) = G_L (E + v_D) - G_L v_D$



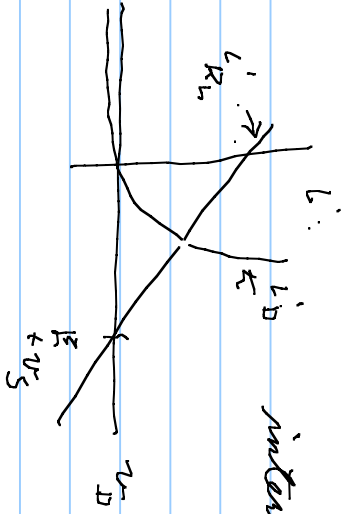

intersection  $i_D = i_{R_L} \Rightarrow$  operating point  
 $\Rightarrow$  Q point if  $v_S = 0$

||  
 AC bearing

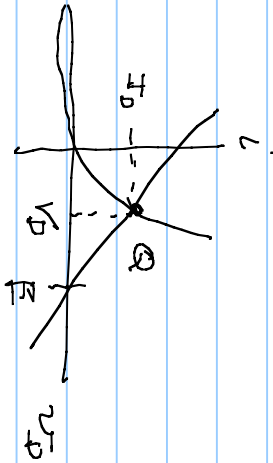


DC operation  
 at no signal



if  $v_D$  small use Taylor series


$$i_D = f(v_D) = I_S (e^{v_D/V_T} - 1)$$

$$= f(v_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} (v_D - V_D) + \left. \frac{d^2 f(v_D)}{2 dv_D^2} \right|_{v_D=V_D} (v_D - V_D)^2 + \dots$$

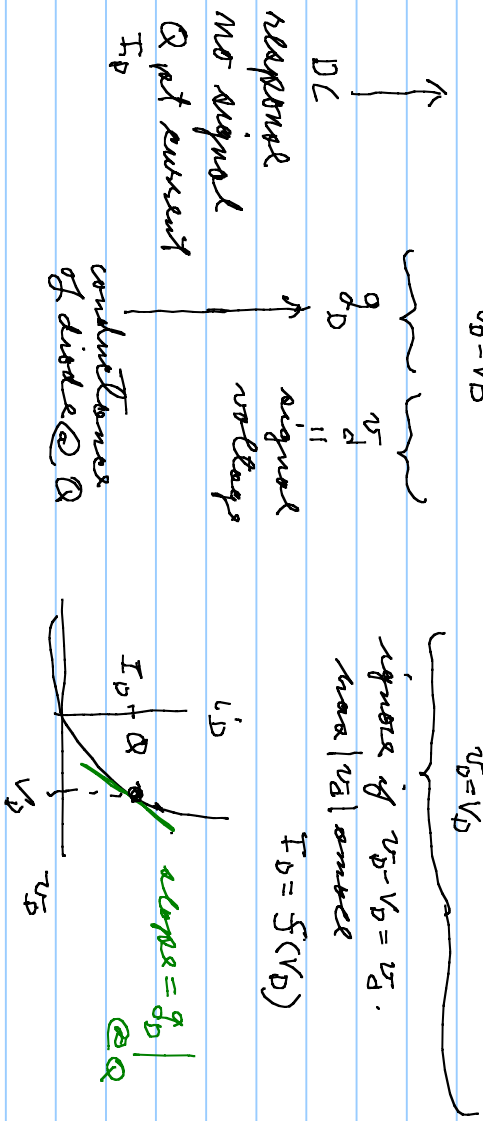

$i_D - I_D = i'_D = \text{signal current} = \text{total current} - \text{bias current}$   
 $x_Y = X_Y - X_g$

$i'_D = i'_B - I_B = g_D \cdot v_D$  (+ higher order terms  $\approx 0$  if  $|v_D|$  small)


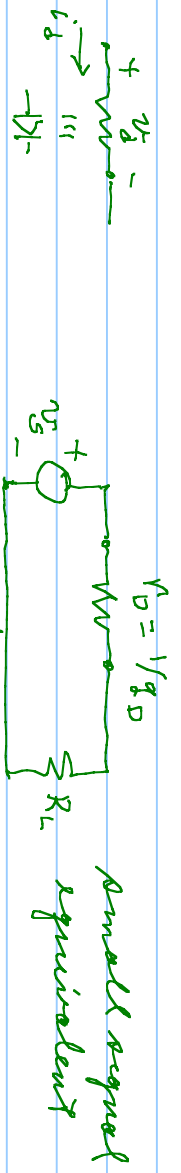


here:  $i'_D = I_S (e^{v_D/V_T} - 1)$  ;  $\frac{di'_D}{dv_D} = \frac{1}{V_T} \cdot I_S e^{v_D/V_T}$

$v_D = V_D$



If  $V_D > 0$  then  $i_D = I_S (e^{v_D/V_T} - 1) \approx I_D = I_S e^{v_D/V_T}$

or  $\left. \frac{d i_D}{d v_D} \right|_{V_D > 0} = \frac{1}{V_T} I_D = g_D$

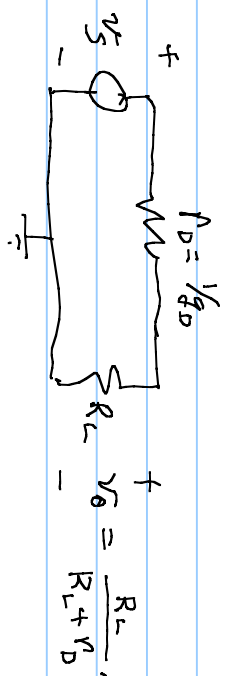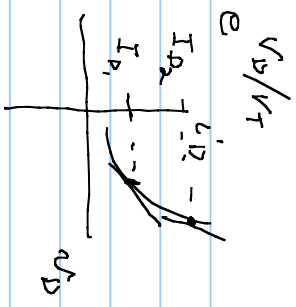



$v_D = \frac{R_L}{R_L + R_D} \cdot v_S$  ;  $i_D = \frac{v_D}{R_L + R_D} \cdot v_S$

Tunnel diode

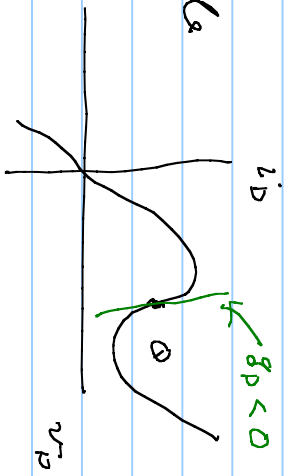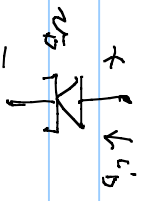



$i_D \cdot v_D = \text{power}$   
 into the diode

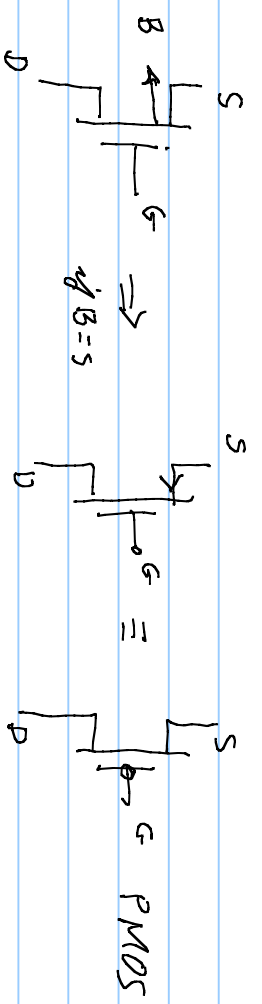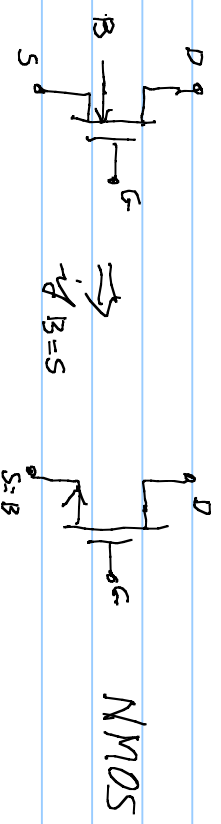MOS Transistors: CMOS  $\Rightarrow$  PMOS with NMOS





for NMOS

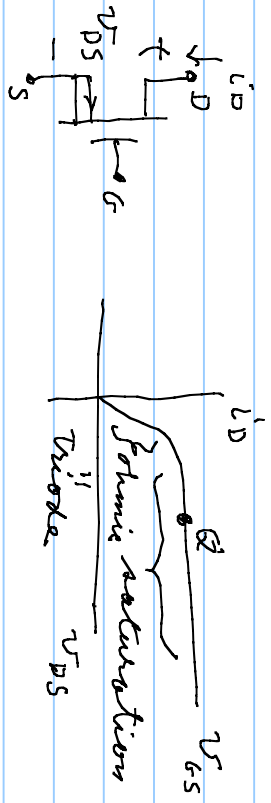

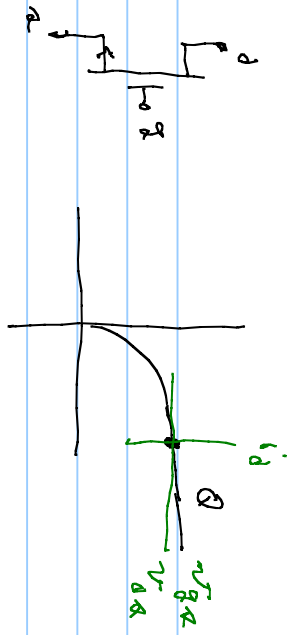

here  $i_D = f(v_{DS}, v_{GS})$

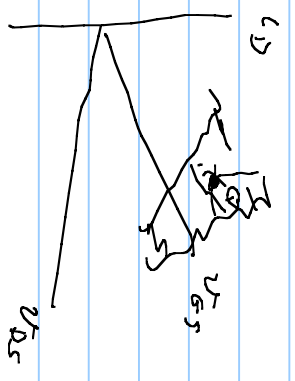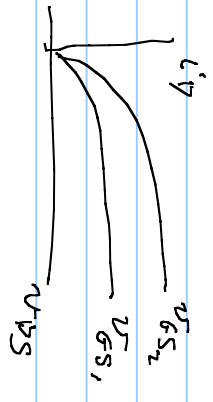

⇒ admittance matrix

