

$\pi$  equivalent circuit  $i = y_{ov}$

p. 718 for BJT & p. 714 for MOS


fig. 10.14(a) fig. 10.12 (b)

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

if linear

$$P_{in} = v_1 i_1 + v_2 i_2 = v^T \cdot i$$



in time domain

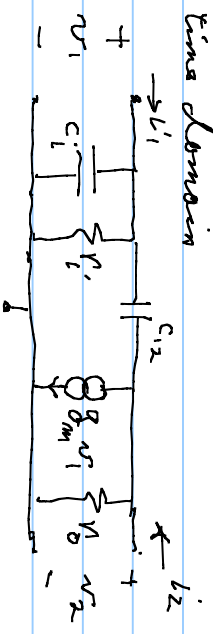

$$i_1 = g_{11} v_1 + g_{12} v_2$$

$$i_2 = g_{21} v_1 + g_{22} v_2$$




$$g_{12} = \frac{L_1}{L_2} \Big|_{v_2=0}$$

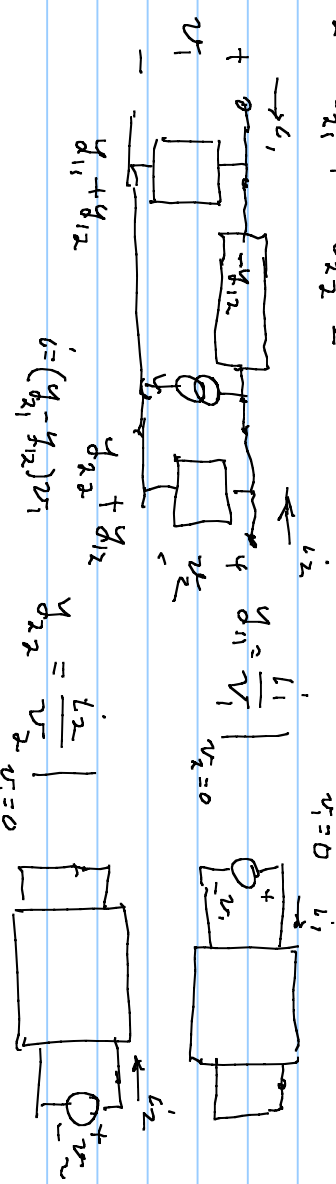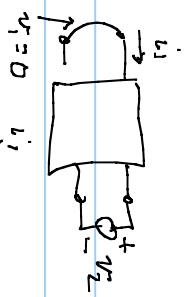

$$g_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$$

$$g_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$


$$i = (g_{21} - g_{12}) v_1$$

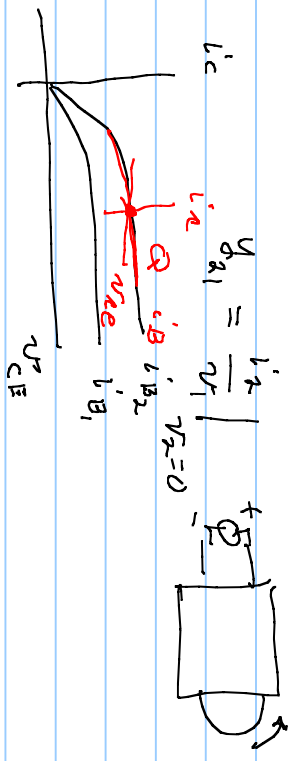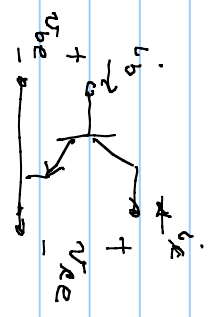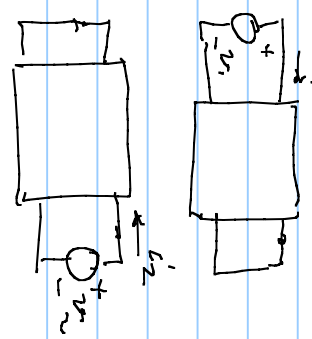

$$i'_C (v_{CE}, i_B) = I_C + \frac{\partial i_C}{\partial v_{CE}} (v_{CE} - V_{CE}) + \frac{\partial i_C}{\partial i_B} (i_B - I_{B0})$$

+ higher order terms,
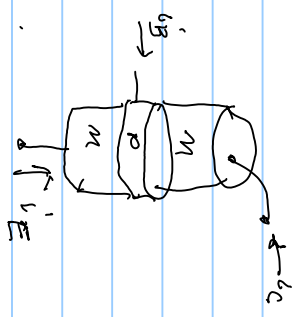
$$i'_C = (i_C - I_C) = g_0 \cdot v_{CE} + \beta \cdot i_B$$



$$i_C + i_B + i_E = 0 \quad KCL$$

we know  $i_C = -\alpha i_E$      $\alpha \approx 1$

$$i_C = -\alpha i_E = -i_B - i_C \Rightarrow i_E (1-\alpha) = -i_B$$

$$\Rightarrow i_E = \frac{1}{1-\alpha} i_C \Rightarrow i_B = \frac{1-\alpha}{\alpha} i_C$$

$$\Rightarrow i_C = \frac{\alpha}{1-\alpha} i_B ; \quad i_C = \beta i_B, \quad \beta = \frac{\alpha}{1-\alpha} = \beta_{forward} = \beta_{EAF} \quad (\text{approx})$$

$i_B$  needs to be (base  $i_C = \beta i_B$  with the same  $\beta$ )

found in terms of  $v_{CE}$  &  $v_{CE} = v_{CE}$  as  $\beta_{eff} \cdot v_{CE}$