

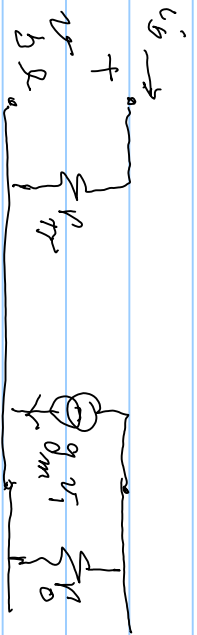
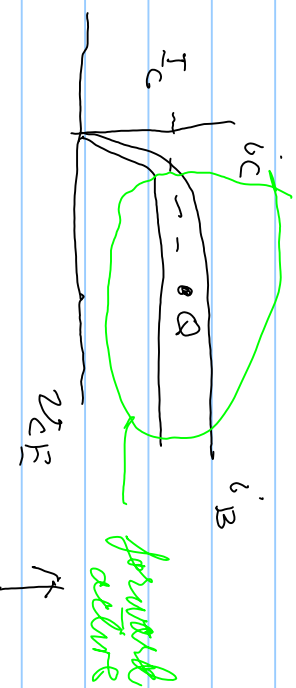


09/20/16

303H

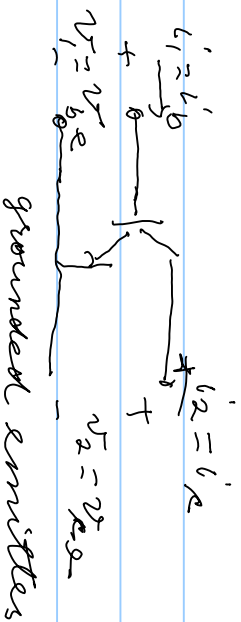

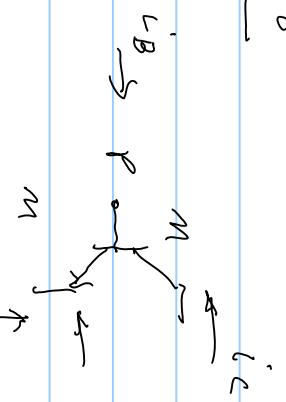v_{CE} feedback bias
 v_{BE} forward bias



$v_{BE}/V_T \approx -v_{be}$
 $v_{CE} \approx I_C R_L = I_S e^{v_{BE}/V_T} R_L$

$$\frac{\partial i_D}{\partial v_{BE}} \Big|_Q = \frac{1}{V_T} I_{SE} e^{v_{BE}/V_T}$$


$$\frac{\partial i_D}{\partial v_{BE}} \Big|_Q = \frac{-I_E}{V_T} = g_m$$

; $i_c \approx \alpha (-i_E) = \beta i_b$
 $r_c = -\alpha r_e = \beta r_b$

device $r_m \Rightarrow v_{be}$ var i_b

\rightarrow $i_b = g_m v_{be}$ $\Rightarrow i_b = \frac{1}{\beta} \frac{I_C}{V_T} v_{be}$

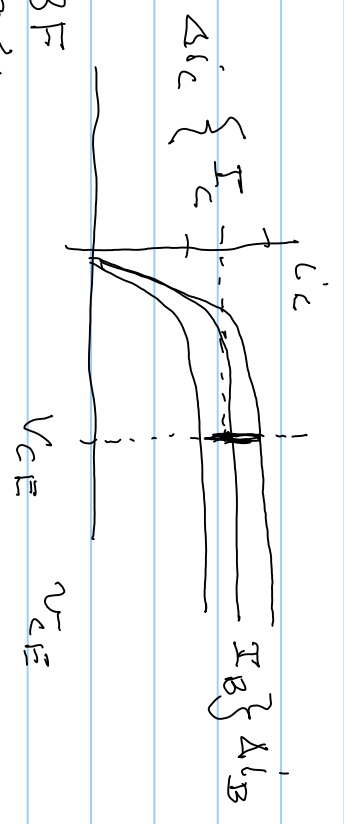
$\Rightarrow g_m = \frac{1}{V_T} = \frac{1}{\beta} \frac{I_C}{V_T}$




$\beta = \frac{\partial I_C}{\partial I_B} \Rightarrow \beta_{forward} = \beta_{reverse}$

$g_m = \frac{\partial I_C}{\partial v_{BE}} = \frac{\partial I_C}{\partial I_B} \cdot \frac{\partial I_B}{\partial v_{BE}} = \beta \cdot g_m = \beta \cdot \frac{1}{\beta} \frac{I_C}{V_T} = \frac{I_C}{V_T} = g_m$

Other $V_0 = 1/g_0$

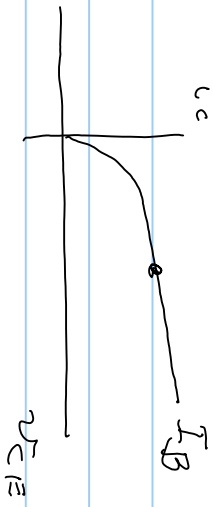


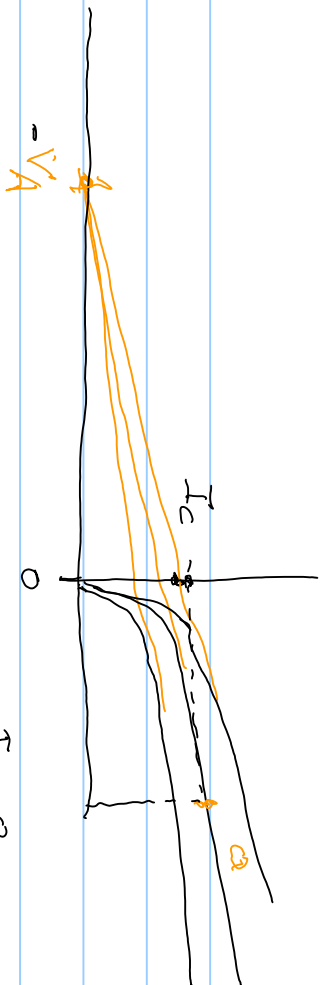

= Early voltage

$$\frac{I_C - 0}{0 - (-V_A)} = \frac{I_C}{V_A} = g_o$$

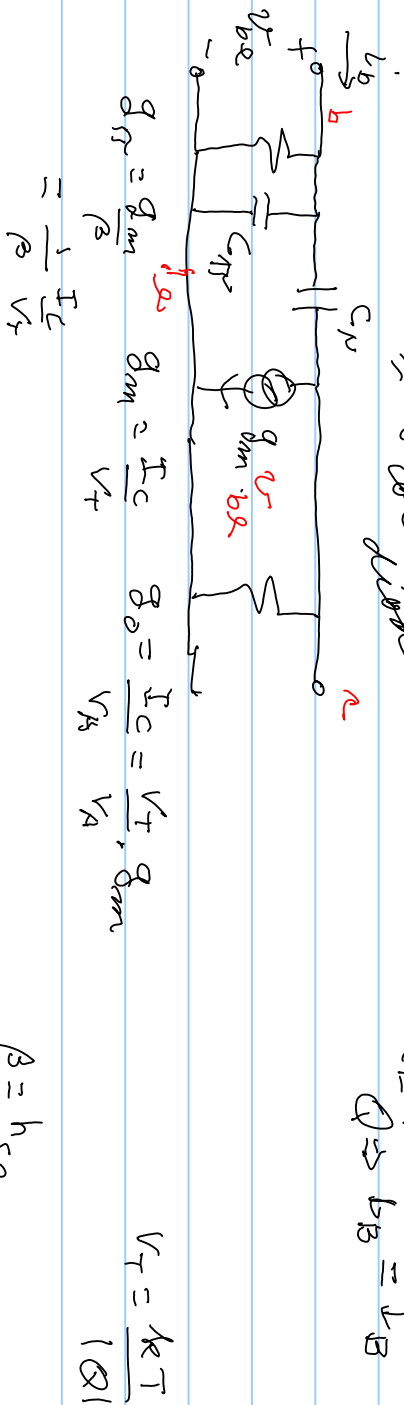capacitance V_T of base-emitter $\approx \frac{C_M}{10-100} = \frac{\partial I_C}{\partial V_{CE}} \Rightarrow I_B = I_B'$



C_{π} = capacitance of (junction)


base to emitter diode

$S =$ forward, $R =$ grounded emitter

$$\beta = h_{FE}$$

$f_T = \text{Transition frequency}$

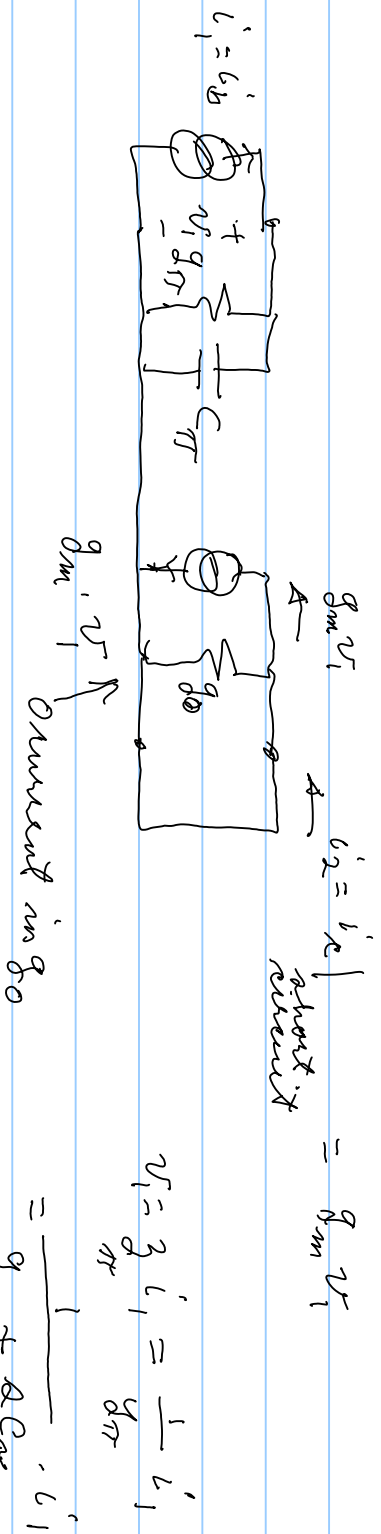l_2 or l_1 as a function of $\omega = \sigma + j\omega$ when $\sigma = 0$



$$l_2 = g_m \cdot \frac{1/C\pi}{1 + (g\pi/C\pi)} \cdot l_1 \Rightarrow l_2 = \beta(\omega) \cdot l_1$$

① DC, $\omega = 0$; $\beta(\omega) = \frac{g_m/C\pi}{1 + (g\pi/C\pi)} \approx \frac{g_m/g\pi}{C\pi \omega + 1}$ ② DC = $\beta = \beta_0$


If $|\beta g_m A_s| = 1$ then the transistor is not of much use


$$A = j\omega C_T$$

$$\omega = 2\pi f$$

$$|\beta g_m A_s| = \frac{(g_m / C_T)}{j\omega + (g_m / C_T)} = \frac{g_m}{C_T} \cdot \frac{1}{\sqrt{(g_m / C_T)^2 + \omega^2}} \Rightarrow 1 \text{ @ } \omega_{\text{th}} (\omega = \omega_T)$$
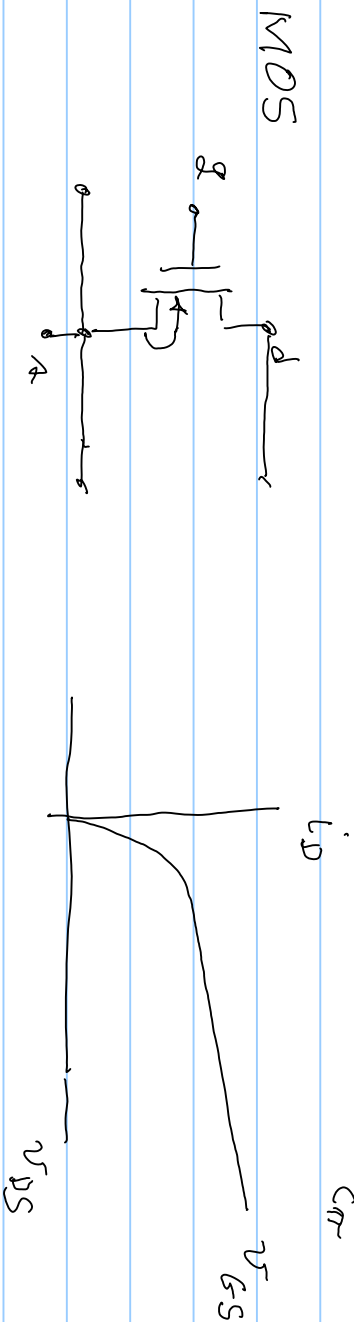
$$\Rightarrow 1 \cdot \left[(g_m / C_T)^2 + \omega^2 \right] = (g_m / C_T)^2 \Rightarrow \omega_T = \sqrt{(g_m / C_T)^2 - (g_m / C_T)^2} = \frac{g_m}{C_T} \sqrt{1 - (1/\beta)^2} \approx \frac{g_m}{C_T}$$



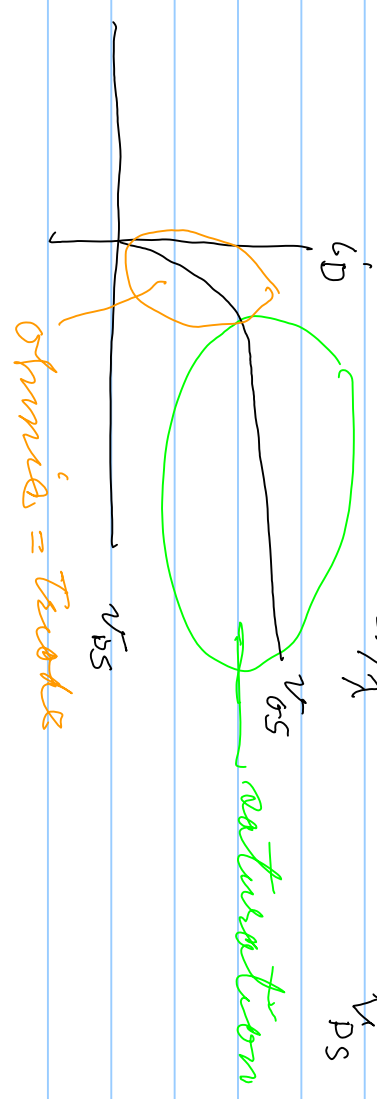

$\Delta I_D = I_{DQ}$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$\Rightarrow V_{GS} = V_{GS}$$