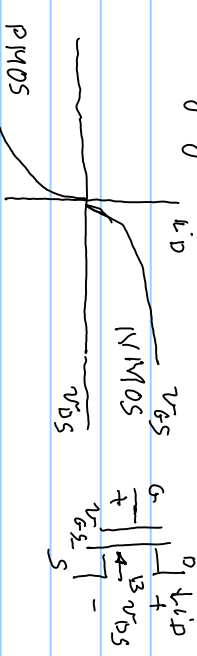



Redesign of block forward:



For NMOS in saturation region $v_{GS} - V_{th} < v_{DS}$
 $I_D = \frac{K_P \cdot W}{2 \cdot L} (v_{GS} - V_{th})^2 (1 + \lambda v_{DS})$ if on
 ($v_{GS} > V_{th}$)

$C = 0$ if off, $v_{GS} \leq V_{th}$
 $V_{th} = V_{T0}$ if $B = 5$

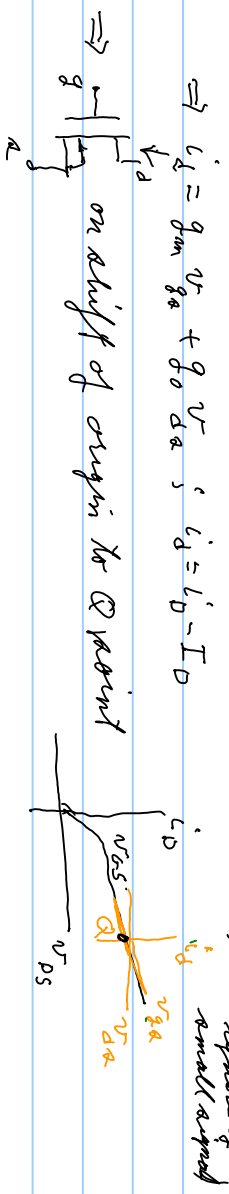$I_D = I_D + g_m (v_{GS} - V_{GS}) + g_o (v_{DS} - V_{DS}) + (higher order terms if small signal)$




From eq. $g_m = \frac{\partial I_D}{\partial v_{GS}} = 2 \frac{K_P W}{2 L} (v_{GS} - V_{th}) (1 + \lambda v_{DS}) = 2 \frac{I_D}{(v_{GS} - V_{th})}$ $v_{GS} - V_{th} = V_{ov}$ or $v_{GS} - V_{th} = V_{ov}$

$$g_o = \frac{\partial i_D}{\partial v_{DS}} = \frac{K_P \mu}{2 L} (V_{GS} - V_{th})^2 \times \lambda ; \text{ for } \lambda \text{ small, } g_o \approx \lambda I_D$$




gives equivalent circuit

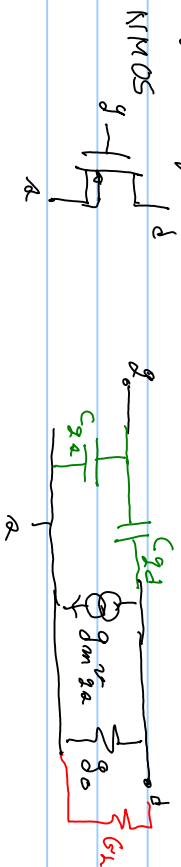

if load in $R_L \approx 1/g_o$ & $g_o \ll 0$ then $v_o = \frac{v_{gs}}{g_o} = -g_m R_L$

add in C_{gs} & C_{gd} from g_{gs} $C_g = C_{gs} + C_{gd} = C_{ox} W \cdot L$
 in saturation $C_{gs} = \frac{2}{3} C_g$, $C_{gd} = \frac{1}{3} C_g$

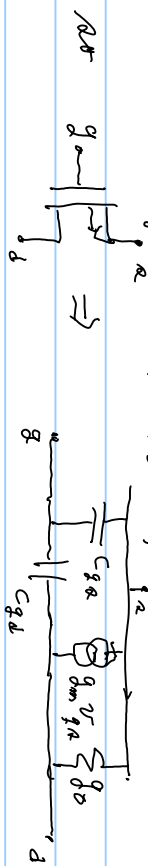Other PMOS slopes, etc, give positive derivatives $g_m = \frac{\partial i_D}{\partial v_{GS}}$, $g_o = \frac{\partial i_D}{\partial v_{DS}}$
 even though $v_{DS} < 0$, $v_{GS} < 0$, $v_{GS} < 0$



Need to know @ Q point for get $A_v = -g_m R_L \Rightarrow$ need to get


$$I_D = I_B, \quad V_{GS} = V_{GS}, \quad V_{DS} = V_{DS} \text{ (when no signal) at DC Q point.}$$

A big problem in general we need to isolate signal circuit from bias circuit.

Bias circuit: Given one battery $V_{DD} \Rightarrow$ here $I_G = 0$ as

we a capacitor at the

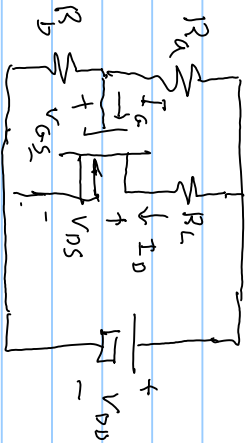gate $\Rightarrow V_{GS}$ via voltage divider



$$V_{GS} = \frac{R_B}{R_A + R_B} V_{DD}$$

$$\Rightarrow \frac{R_A}{R_B} = \frac{V_{DD} - V_{GS}}{V_{GS}} = \frac{V_{DD}}{V_{GS}} - 1$$

\Rightarrow only ratio given we choose very large

for small current obtained from V_{DD}

\therefore get V_{GS} by R_A, R_B , if given V_{GS} then $V_{DD} - V_{GS} = R_L I_D$ (\Rightarrow load line)

Given I_D from curve or in saturation $I_D = \frac{K_P}{2} \frac{W}{L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS})$
 $\approx \frac{K_P W}{2} (V_{GS} - V_{TO})^2$

$$8 g_m \approx \frac{2 I_D}{(V_{GS} - V_{TO})}$$

but also want $A_v = -g_m R_L$

Ex: $I_D = 2 \times 10^{-4} (V_{GS} - V_{TO})^2$ If $V_{GS} = 3$, $V_{TO} = 1 \Rightarrow I_D = 2 \times 4 \times 10^{-4}$


$$g_m = \frac{2 I_D}{V_{GS} - V_{TO}} = \frac{8 \times 10^{-4}}{4} = 2 \times 10^{-4} = 0.2 \text{ mS} = 0.8 \text{ mA}$$

If $A_v = -12 = -g_m R_L \Rightarrow R_L = \frac{12}{g_m} = \frac{12}{2 \times 10^{-4}} = 60 \times 10^3 = 60 \text{ k}\Omega$

If $V_{DS} = 9 \text{ V}$ then for $V_{GS} = 3 \Rightarrow \frac{R_A}{R_B} = \frac{V_{DD} - 1}{V_{GS} - 1} = \frac{9 - 1}{3 - 1} = 5$


\therefore if $R_B = 10 \text{ MEG}\Omega \Rightarrow R_A = 50 \text{ MEG}\Omega$

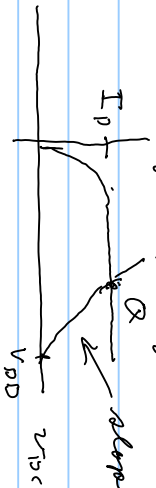for lambda good, & if $\lambda = 0$ is ok, but if $\lambda \neq 0$ there is a mistake in a monkey word



slope $= -1/R_L$; can choose any V_{DS} if $\lambda = 0$
 but not if $\lambda \neq 0$; we use above
 as 1st approx of in sat \Rightarrow turn to series


Gate connected

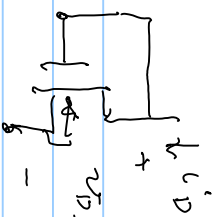

$V_{DS} = V_{GS}$ then $V_{GS} - V_{TO} < V_{GS} = V_{DS}$

or in saturation

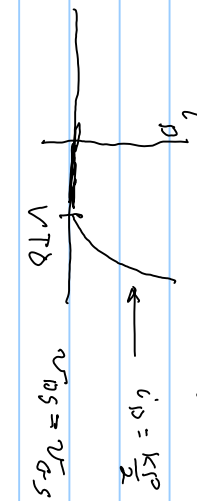or if $V_{GS} - V_{TO} < 0$; if $V_{TO} > 0$ (\equiv enhancement mode)



makes curve slightly above $\frac{K_P W}{2 L} (V_{DS} - V_{TO})^2$

If $V_{TO} < 0$ then we have depletion mode (\Leftrightarrow depletes the channel)

