

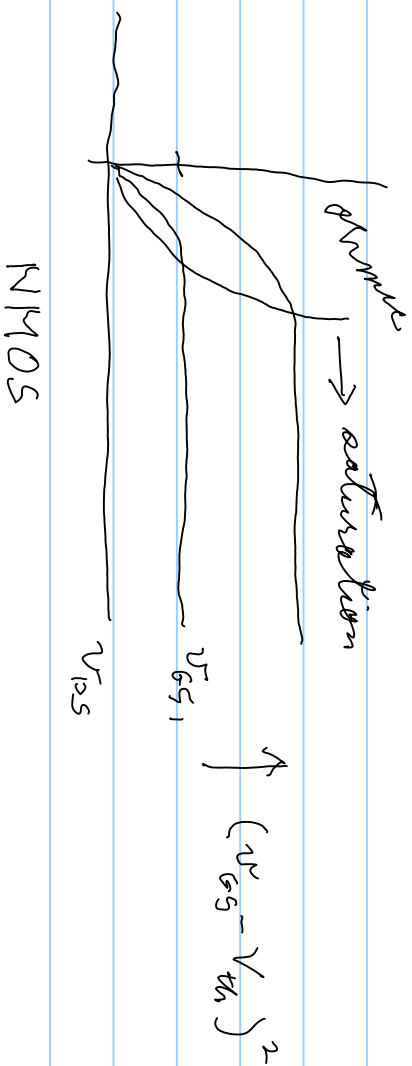


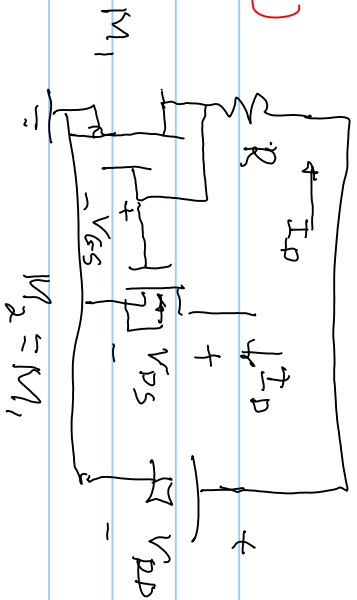
$B_n$  bias of lowest potential on the strip } to back bias  
 $B_p$  highest " " " " " " } source to bulk to  
 avoid back current  
 $V_D$



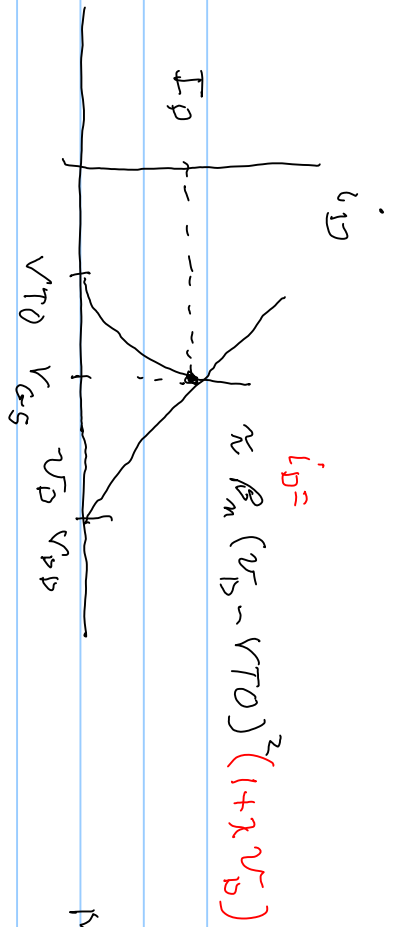





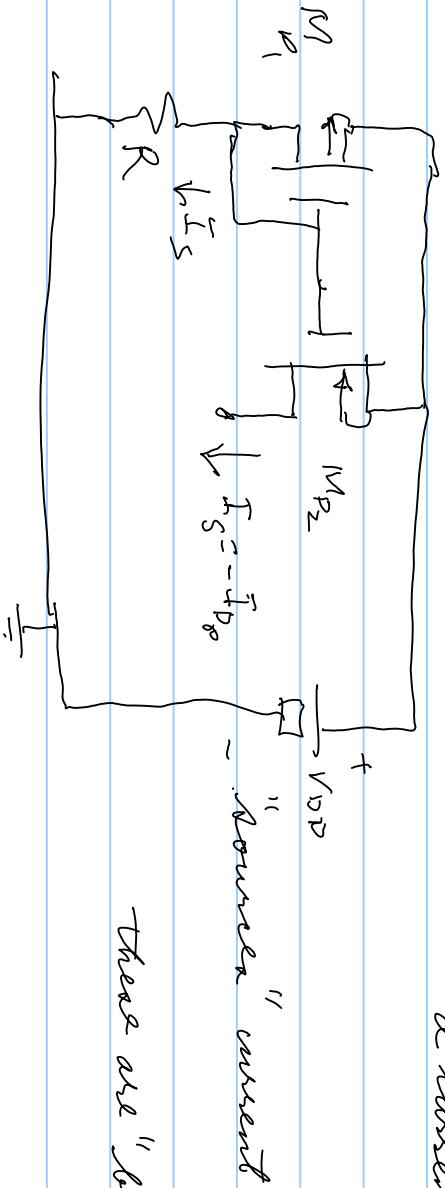$V_{GS} > V_{GS} - V_{T0}$   
a current "sinks"





"source" current  
these are "sink" current


# BJT relations

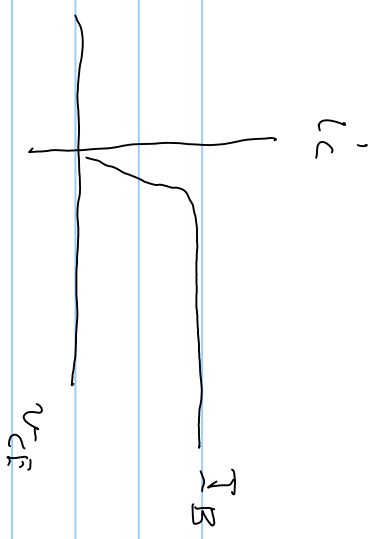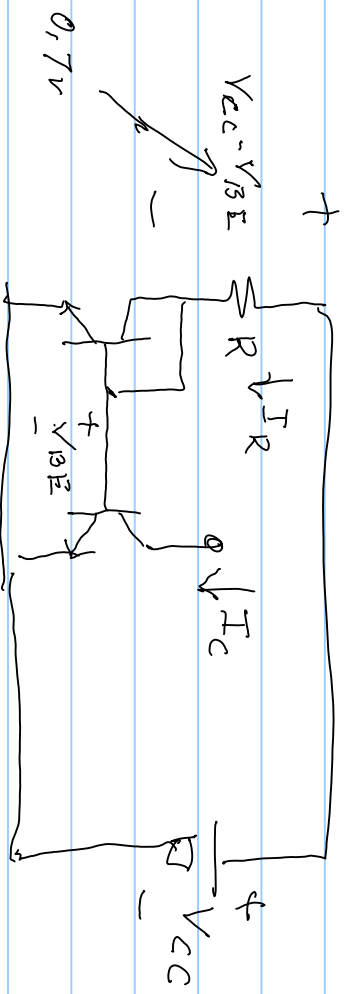


$$I_c \approx I_R = \frac{1}{R} (V_{cc} - V_{BE}) \Rightarrow R = \frac{V_{cc} - V_{BE}}{I_c} \text{ gives design eq.}$$

Differential pair

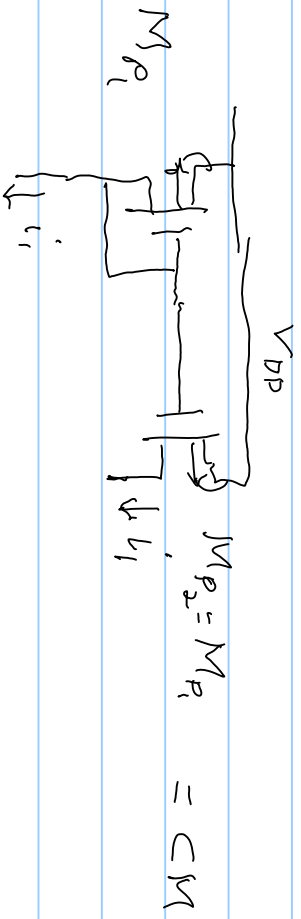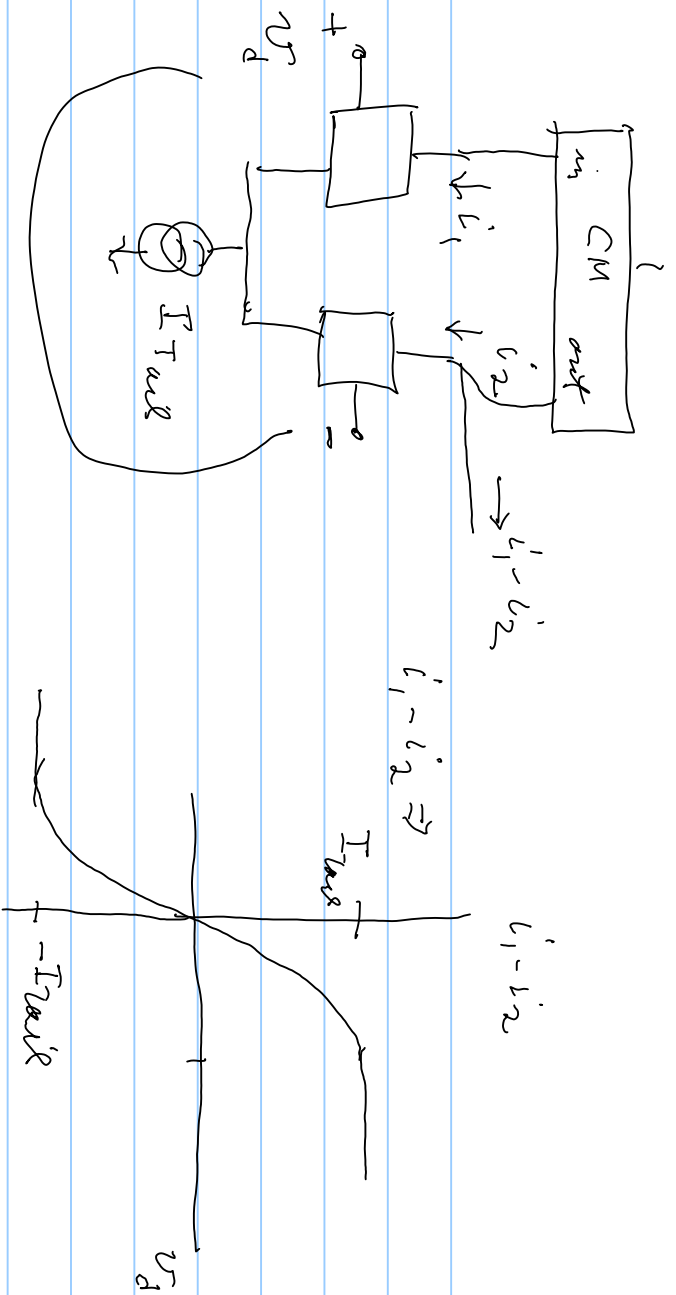


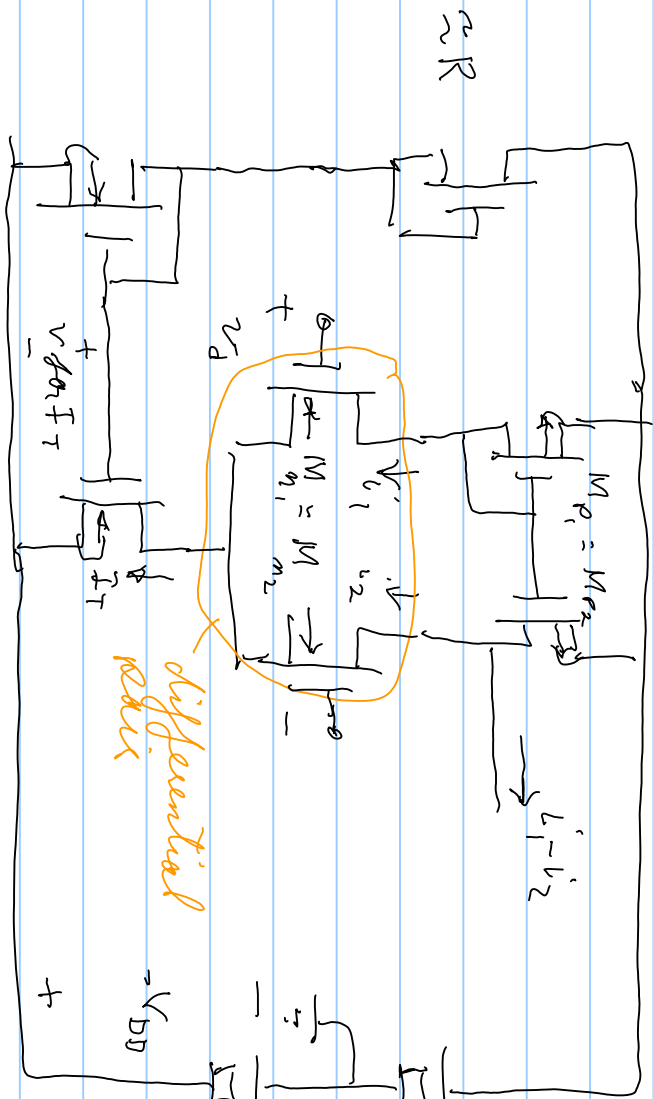


*differential  
axis*

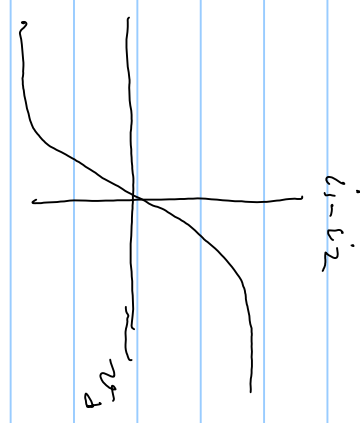

here the load on  $M_{n2}$   
differs from that on  $M_{n1}$ ,

$$-V_{GS} = +V_{DD}$$

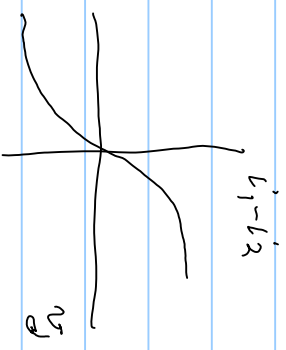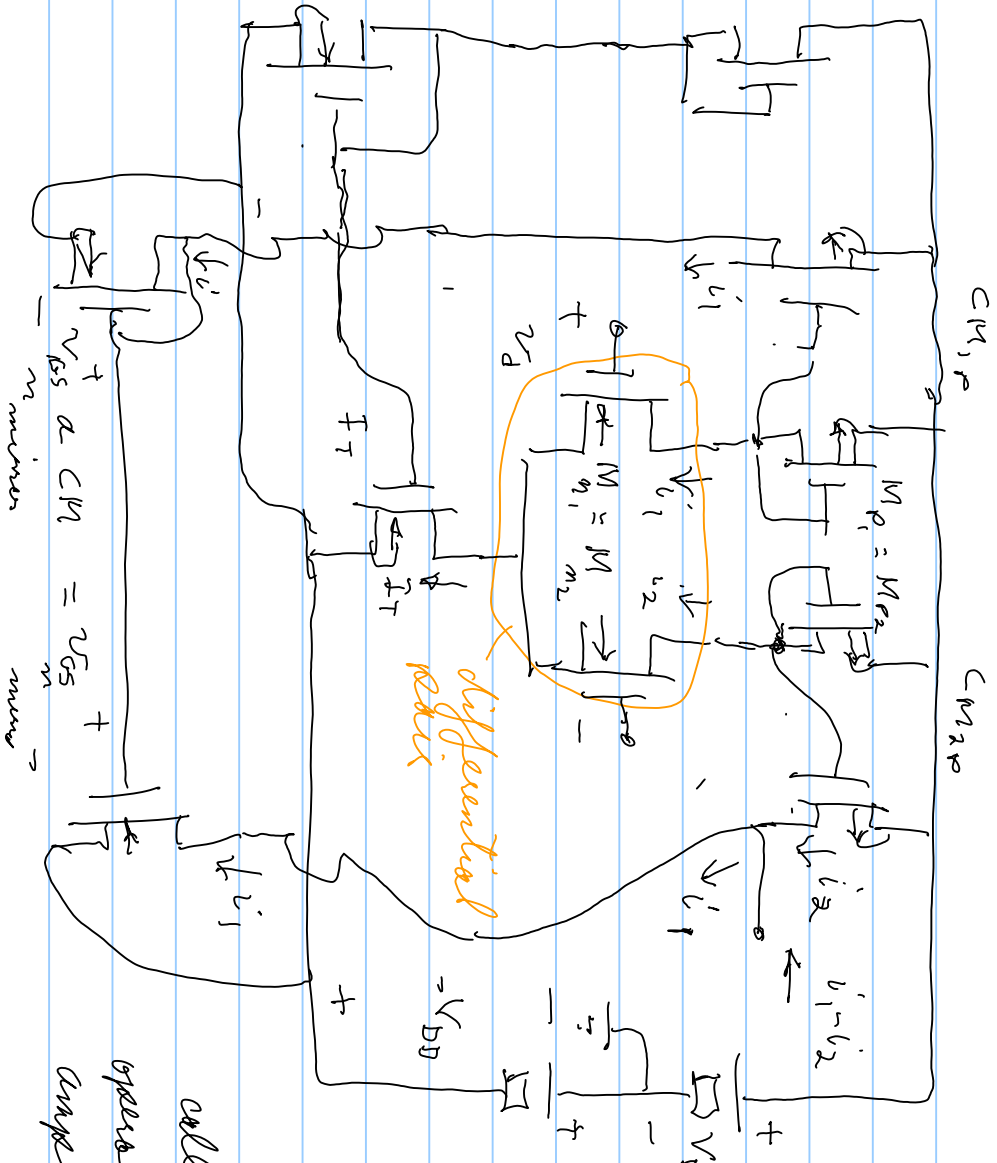

if MOS  $\Rightarrow$  BJT  

$$v_d = v_{i1} - v_{i2} = I_T \tanh\left(\frac{v_d}{2V_T}\right)$$

called an OTA  
 operational transconductance  
 amplifier