
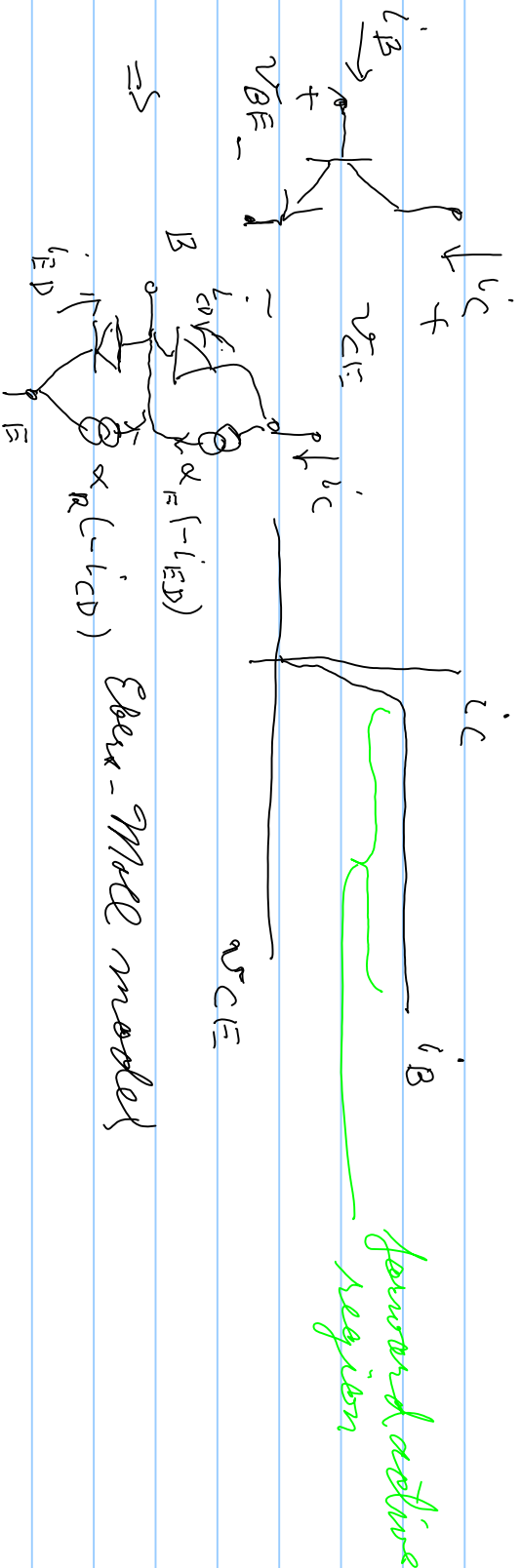


EE303H


10/06/16

Lesson kinds
with BJT

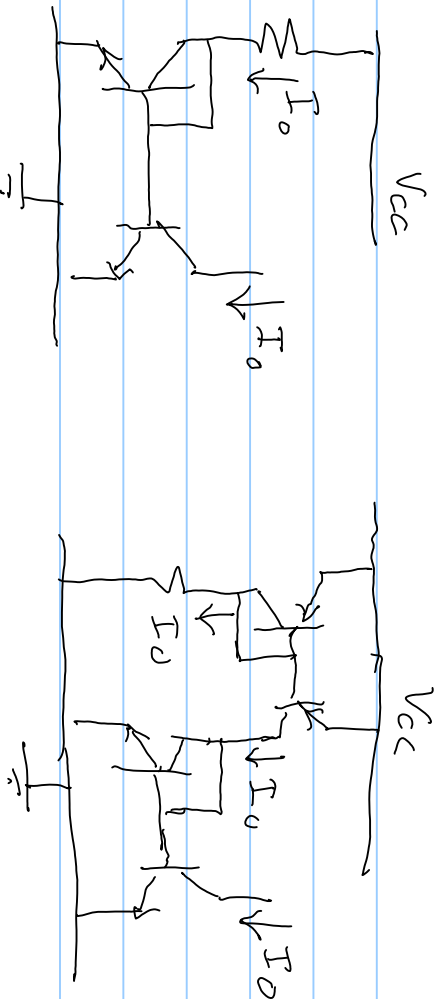

class-model model

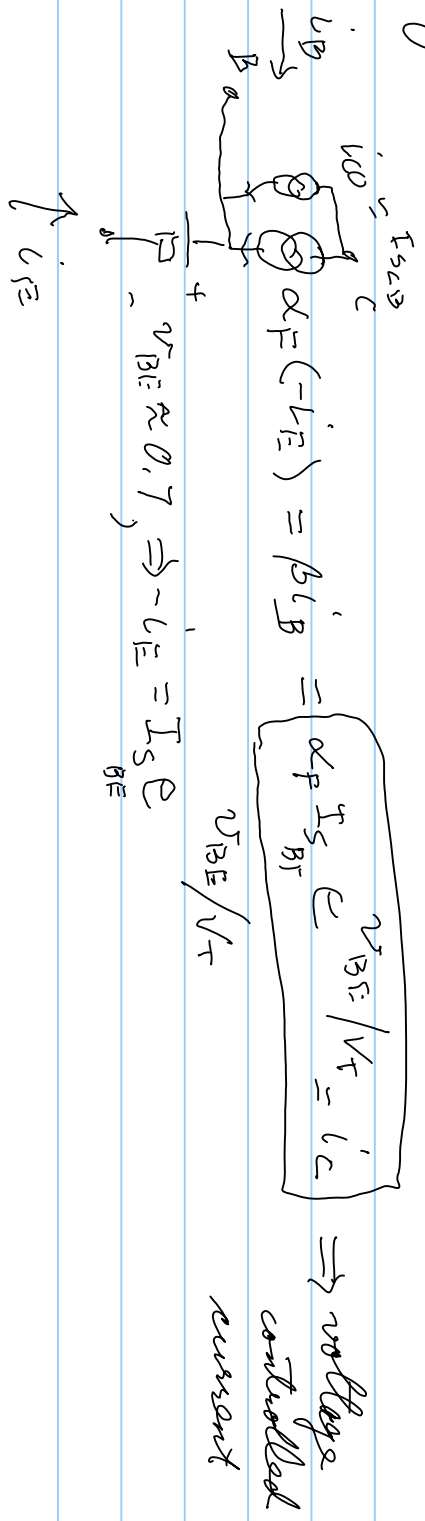If we forward bias base to emitter & back bias base to collector





$$Q_1 = Q_2$$

$$KVL = 0 = -v_1 + V_{BE1} - v_{BE2} + v_2 \Rightarrow v_1 - v_2 = v_{BE1} - v_{BE2}$$

$$T = \text{constant}$$

$-V_{CC}$

$$i_1 = \alpha I_S e^{v_{BE1}/V_T} ; i_2 = \alpha I_S e^{v_{BE2}/V_T} \quad V_T = \text{thermal voltage} = kT/q$$

$$i_1 + i_2 = I_T \quad v_1 = v_o = v_1 - v_2$$

$$\ln i_1 = (\ln \alpha I_S) + \ln(e^{v_{BE1}/V_T}) ; \ln i_2 = \ln(\alpha I_S) + \ln(e^{v_{BE2}/V_T})$$

$$\ln i_1 - \ln i_2 = \frac{v_{BE1}}{V_T} - \frac{v_{BE2}}{V_T} = v_i / V_T = \ln i_1 / i_2$$

$$e^{\operatorname{Re}(i_1/i_2)} = \frac{i_1}{i_2} = e^{v_i/v_T}, \quad \text{but } i_1 = I_T - i_2$$



$$I_T - i_2 = e^{v_i/v_T} i_2 \Rightarrow i_2 (1 + e^{v_i/v_T}) = I_T$$

$$i_2 = \frac{I_T}{1 + e^{v_i/v_T}}, \quad i_1 = I_T - i_2 = I_T \left(1 - \frac{1}{1 + e^{v_i/v_T}} \right) = \frac{I_T e^{v_i/v_T}}{1 + e^{v_i/v_T}}$$

$$i_2 - i_1 = I_T \left(\frac{1 - e^{v_i/v_T}}{1 + e^{v_i/v_T}} \right) = I_T \frac{e^{v_i/2v_T} \left[\frac{e^{-v_i/2v_T} - e^{+v_i/2v_T}}{e^{-v_i/2v_T} + e^{+v_i/2v_T}} \right] / 2}{(e^{-v_i/2v_T} + e^{+v_i/2v_T}) / 2}$$

$$= I_T \frac{\sinh(v_i/2v_T)}{\cosh(v_i/2v_T)} = I_T \tanh(v_i/2v_T)$$



$$i_2 - i_1 < 0$$

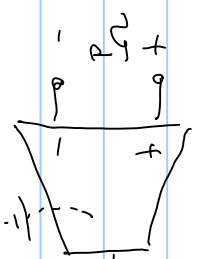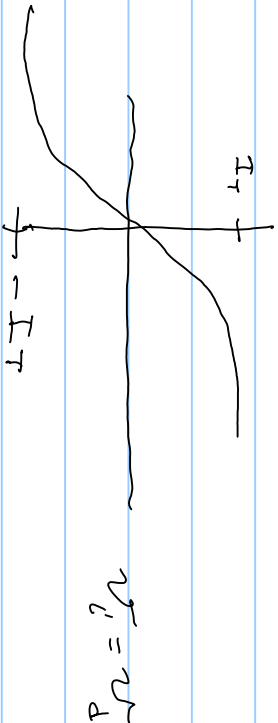

$$i_0 = I_T \tanh(v_i/2v_T)$$

operational
transconductance
amplifiers

colloquial
OTA

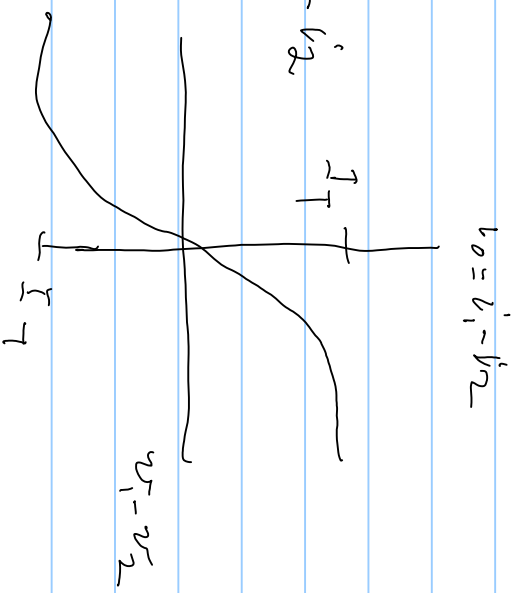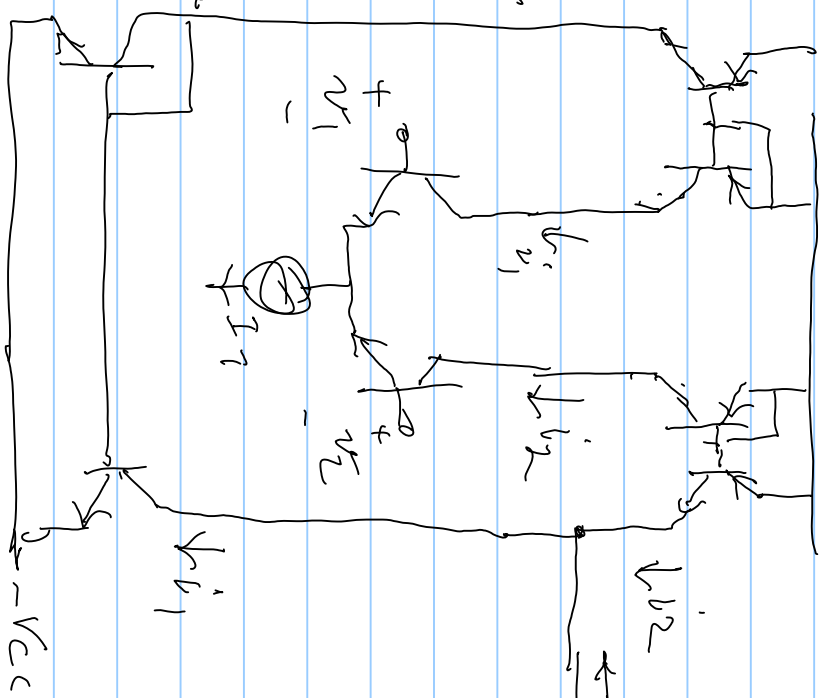


small signal $v_o = I_T \left(\frac{v_i}{2V_T} \right)$

$$v_o = I_T \tanh\left(\frac{v_i}{2V_T}\right) \approx I_T \left(\frac{v_i}{2V_T} \right) \quad \text{for } v_i \ll 2V_T$$


$$G_m \approx \frac{dI_{\text{tanh}}(v_i/2V_T)}{dv_i} \bigg|_{v_i=0} = I_T \frac{1}{2V_T} \frac{d(\tanh x)}{dx} \bigg|_{x=0} = \frac{I_T}{2V_T} (1 - \tanh^2 x)$$

$$= \frac{I_T}{2V_T}$$

small signal OTA

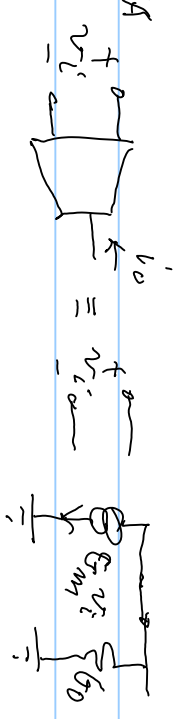


$V_A =$ Early voltage

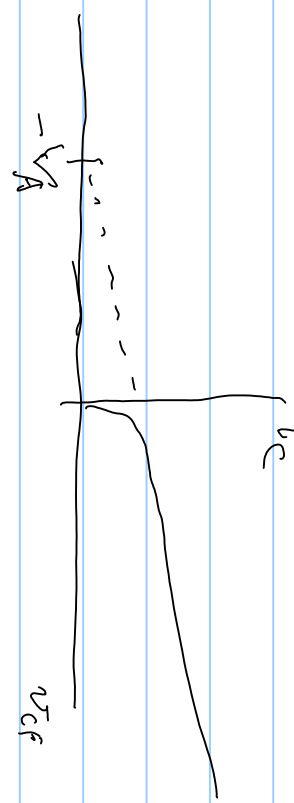

OTA is a 4-quadrant multiplier use I_T & I_{T2} as inputs to get 2-differential & get I_T & I_{T2} as currents & sign of

one differential pair

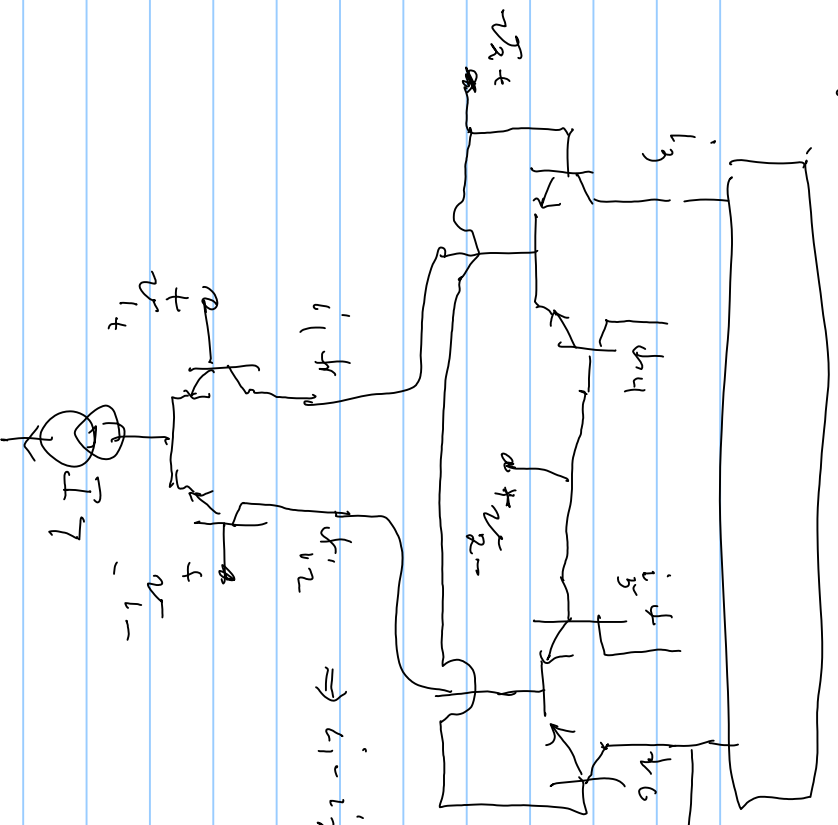

$$i_D' = I_T \tanh\left(\frac{v_{in,dm}}{2V_T}\right) + I_T \tanh\left(\frac{v_{in,cm}}{2V_T}\right)$$

$$\Rightarrow i_{D1}' = i_{D2}' = I_T \tanh\left(\frac{v_{in,dm}}{2V_T}\right)$$