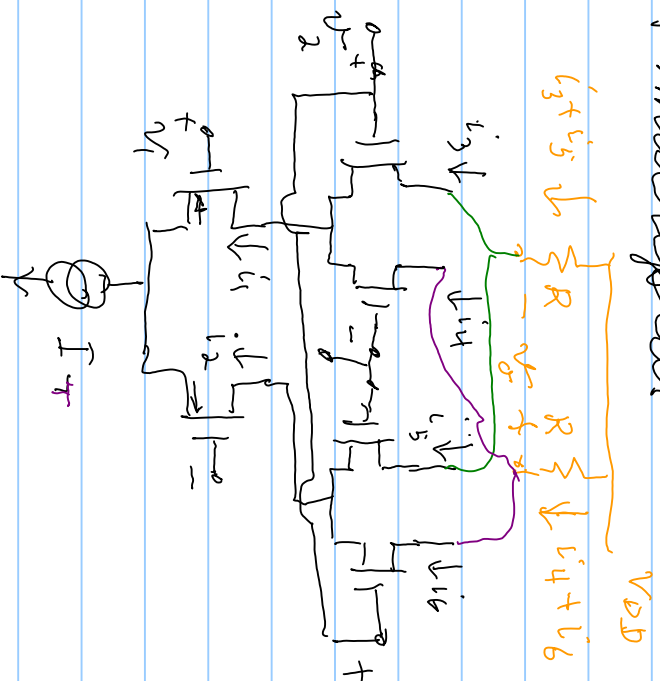


Widder multiplier



$$0 = -v_o - R(i_4 + i_6) + R(i_3 + i_5)$$

$$v_o = R[(i_3 + i_5) - (i_4 + i_6)] \\ = R \cdot I_T f(v_1) f(v_2)$$

$$i_1 = \frac{I_T}{2} (1 + f(v_1)) \quad i_2 = \frac{I_T}{2} (1 - f(v_1))$$

$$i_3 = \frac{i_1}{2} (1 + f(v_2)) \quad i_4 = \frac{i_1}{2} (1 - f(v_2))$$


$$i_5 = \frac{I_2}{2} (1 - f(v_{a2})) \quad i_6 = \frac{I_2}{2} (1 + f(v_{a2}))$$


$$\begin{aligned} i_3 + i_5 &= \frac{I_1}{4} (1 + f(v_{a1})) (1 + f(v_{a2})) + \frac{I_1}{4} (1 - f(v_{a1})) (1 - f(v_{a2})) \\ &= \frac{I_1}{4} \left[(1 + f(v_{a1}) + f(v_{a2}) + f(v_{a1}) \cdot f(v_{a2})) + (1 - f(v_{a1}) - f(v_{a2}) + f(v_{a1}) \cdot f(v_{a2})) \right] \\ &= \frac{I_1}{2} [1 + f(v_{a1}) f(v_{a2})] \\ i_4 + i_6 &= \frac{I_1}{4} (1 + f(v_{a1})) (1 - f(v_{a2})) + [1 - f(v_{a1})] [1 + f(v_{a2})] \\ &= \frac{I_1}{4} (1 + f(v_{a1}) - f(v_{a2}) - f(v_{a1}) \cdot f(v_{a2}) + 1 - f(v_{a1}) + f(v_{a2}) - f(v_{a1}) f(v_{a2})) \\ &= \frac{I_1}{2} (1 - f(v_{a1}) \cdot f(v_{a2})) \end{aligned}$$

$$(i_3 + i_5) - (i_4 + i_6) = I_1 f(v_{a1}) f(v_{a2}) \quad \text{small signals} \approx k v_1, v_2$$

Översättning för I_1
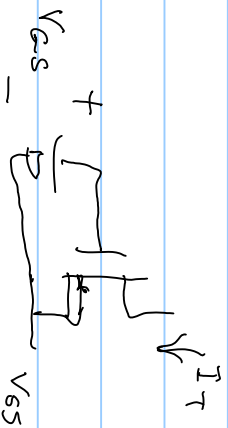
$$I_1 \approx \frac{k_P \cdot v}{2 n} (V_{GS} - V_{T0})^2$$



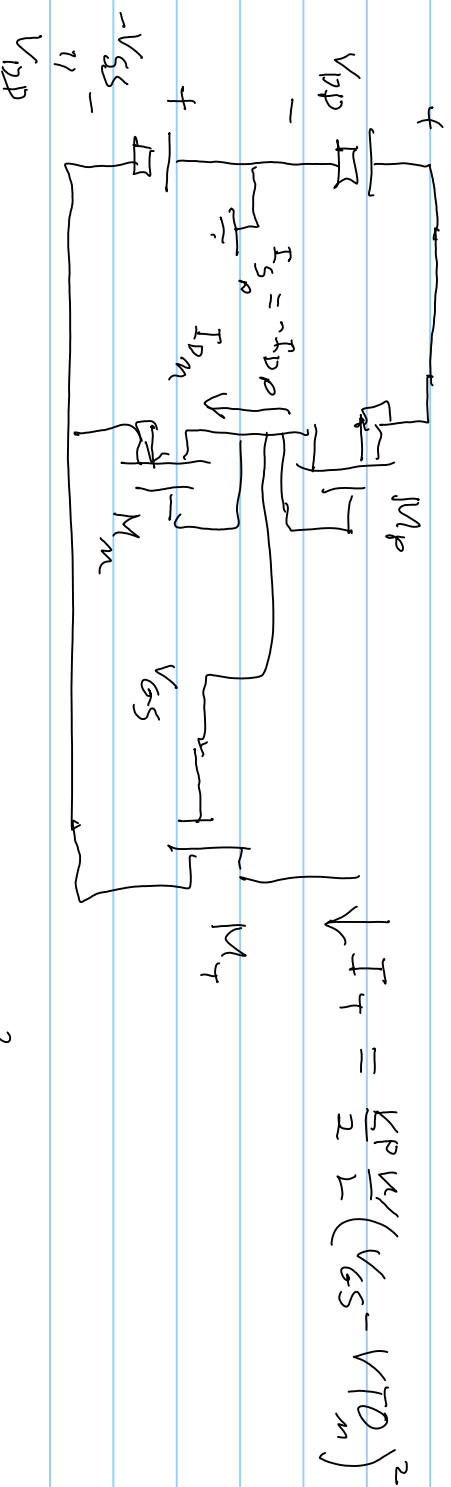

$$I_{Dp} = \frac{K_{Pp}}{2} \left(\frac{W}{L} \right)_p (V_{DD} - V_{GS} - |V_{T0p}|)^2$$

$$= \frac{K_{Pm}}{2} \left(\frac{W}{L} \right)_m (V_{GS} - |V_{T0m}|)^2$$

$$\left(\frac{W/L} \right)_p \times \frac{K_{Pp}}{K_{Pm}} \left(\frac{V_{DD} - V_{GS} - |V_{T0p}|}{V_{GS} - |V_{T0m}|} \right)^2 = 1$$

$$\left(\frac{W/L} \right)_p = \left(\frac{W/L} \right)_m \times \frac{K_{Pm}}{K_{Pp}} \left(\frac{V_{GS} - |V_{T0m}|}{V_{DD} - V_{GS} - |V_{T0p}|} \right)^2$$

gives a design
formula for $\frac{W}{L}_p$

Differential equations

linear time invariant

$$a_n \frac{d^n v_o}{dt^n} + a_{n-1} \frac{d^{n-1} v_o}{dt^{n-1}} + \dots + a_1 \frac{dv_o}{dt} + v_o = b_m \frac{d^m v_i}{dt^m} + \dots + b_1 \frac{dv_i}{dt} + b_0 v_i$$

if $v_i(t) = V_i e^{at}$ for $-\infty < t < \infty$ then a solution is $v_o(t) = V_o e^{at}$


$$e^{at} [a_n V_o + a_{n-1} V_o + \dots + a_1 V_o + a_0 V_o] = [b_m a^m V_i + \dots + b_1 a V_i + b_0 V_i] e^{at}$$

$$[a_n a^n + a_{n-1} a^{n-1} + \dots + a_1 a + a_0] V_o = [b_m a^m + b_{m-1} a^{m-1} + \dots + b_1 a + b_0] V_i$$

$$T(s) = \frac{V_o}{V_i}(s) = \frac{b_m s^m + \dots + b_1 s + b_0}{a_n s^n + \dots + a_1 s + a_0} \Rightarrow \text{the voltage transfer function}$$

at $s = j\omega \Leftrightarrow$ sinusoidal steady state

$$\frac{V_o}{V_i}(j\omega) = |T(j\omega)| e^{j\angle T(j\omega)}$$

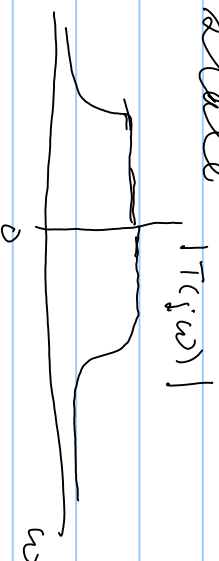

for linear plots, $m \leq n$ normally $b_i = 0$ except $b_0 \neq 0$