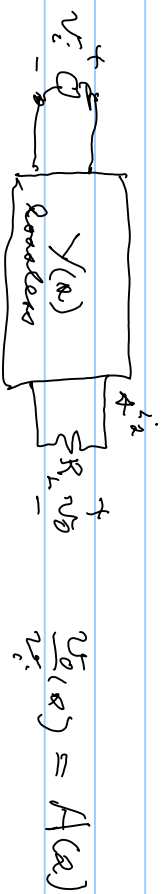


EE 303 14

10/20/16




$$\frac{v_0(s)}{v_1(s)} = A(s)$$

$$-G_1 v_2 = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}, \quad \begin{bmatrix} v_1 = v_1 \\ v_2 = v_0 \end{bmatrix} \quad i_2 = -G_1 v_0$$

$$\rightarrow G_1 v_2 = y_{21} v_1 + y_{22} v_2 \Rightarrow (-G_1 - y_{22}) v_0 = y_{21} v_1$$

$$\frac{v_0}{v_1} = \frac{-y_{21}}{G_1 + y_{22}} = \frac{-y_{21}/G_1}{1 + y_{22}/G_1} = \frac{-N_{21}/D_{22}}{D_{22} + N_{22}}$$

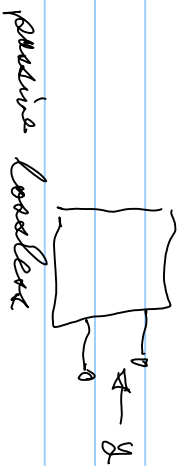Ex: $\frac{v_0(s)}{v_1(s)} = \frac{5s}{s^6 + 5s^5 + 9s^4 + 6s^3 + 23s^2 + 8s + 15} \Rightarrow$ a four-pole system with 6 degree denominator



$$\begin{aligned}
 \text{Res}(jw) = 0 &= \text{Re}(V^* I) \\
 &= \frac{V^* I + V I^*}{2} = \frac{V^* y(jw) V + V y^*(jw) V^*}{2} \\
 &= \frac{|V|^2 (y(jw) + y^*(jw))}{2} = 0 \quad \uparrow \text{Real part}
 \end{aligned}$$


$$y(t; \omega) = -y^*(j\omega) = -y(-j\omega)$$

Real components \Rightarrow real coefficients $\Rightarrow y(a) = \frac{N(a)}{D(a)}$

for an analytic continuation $\omega = a/j$

$$y(a) = -y(-a) \Rightarrow y(a) + y(-a) = 2 \text{Re}(y(a)) = 0, \text{Er} = \text{Even}$$
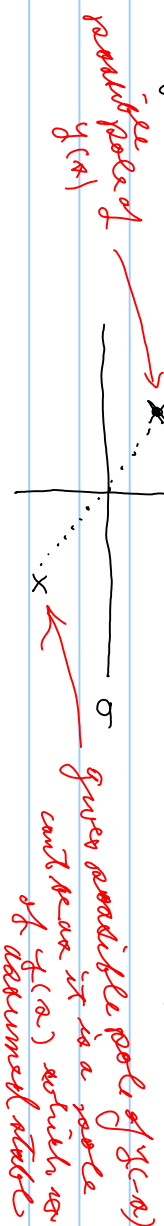
$$\Rightarrow y(a) \text{ is odd} \quad \text{A plane} = \sigma + j\omega$$



\therefore all poles of $y(s)$ (real/complex) are on $j\omega$ axis have to be simple

$$y(s) \approx \frac{k}{s - j\omega_0} \quad \text{near } s = j\omega_0 = \frac{k^*}{s + j\omega_0} \quad \text{near } s = -j\omega_0 = -s^*$$

$$y(s) \approx \frac{k}{s - j\omega_0} + \frac{k^*}{s + j\omega_0} + \text{other terms}$$

$$\approx \frac{s(k + k^*) + j\omega_0(k - k^*)}{s^2 + \omega_0^2} + \dots \Rightarrow k = k^* \\ = \frac{2k\omega_0}{s^2 + \omega_0^2} + \dots \text{ other similar terms} + \frac{k_0}{s} + \frac{k_\infty}{s}$$

no $y(s)$ is odd then @ $s \rightarrow \infty$ $y(s) \approx k_0/s$, $k_\infty > 0$
 as a possible design to to remove poles at ∞ or
 at $1/s$ at ∞ ,



$$\begin{aligned}
 & \frac{1}{s} \frac{R^6 + R^5 + 9R^4 + 6R^3 + 23R^2 + 8R + 15}{(R^5 + 6R^3 + 8R)} = \frac{15}{s} = \frac{-y_{21}}{1 + 8R} \\
 & = \frac{1 + \frac{R^6 + 9R^4 + 23R^2 + 15}{R^5 + 6R^3 + 8R}}{1 + 8R} \quad y_{21} = 1
 \end{aligned}$$

$y_{22} = \frac{R^6 + 9R^4 + 23R^2 + 15}{R^5 + 6R^3 + 8R} \Rightarrow$ get a continued fraction expansion about $R = \infty$ (to give low pass)

$$\begin{array}{r}
 \underbrace{R^5 + 6R^3 + 8R}_{R} \overline{) R^6 + 9R^4 + 23R^2 + 15} \\
 \underline{R^6 + 6R^4 + 8R^2} \\
 3R^4 + 15R^2 + 15 \\
 \underbrace{R^5 + 6R^3 + 8R}_{\frac{1}{3}R} \overline{) 3R^4 + 15R^2 + 15} \\
 \underline{R^5 + 5R^3 + 5R} \\
 3R^3 + 3R \\
 \underbrace{3R^4 + 15R^2 + 15}_{3R^4} \overline{) 3R^3 + 3R} \\
 \underline{3R^4 + 9R^2} \\
 6R^2 + 15 \\
 \underbrace{R^3 + 3R}_{\frac{1}{6}R} \overline{) 6R^2 + 15} \\
 \underline{R^3 + 3R} \\
 R^2 - 5R \\
 \underbrace{R^2 - 5R}_{\frac{1}{2}R} \overline{) R^2 - 5R} \\
 15
 \end{array}$$


$$y(a) = \frac{24}{12} \left(\frac{1}{3} \frac{1}{2} \frac{1}{3} + \frac{1}{3a} + \frac{1}{3a^2} \right)$$
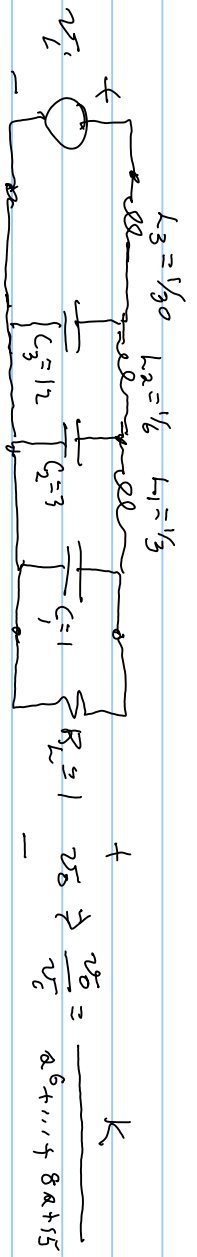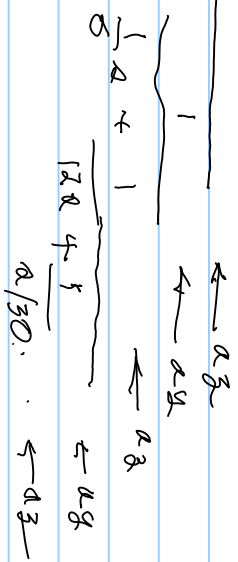
$$\frac{1}{2} \sqrt{\frac{6a^3 + 15}{6a^2}} \cdot \frac{12a}{15} \cdot \frac{4}{30} \cdot \frac{1}{2}$$



to get K, set $a=0$

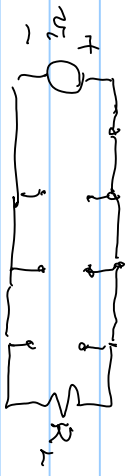given $\frac{v_0}{v_1} = \frac{15}{a^6 + a^5 + 9a^4 + 6a^3 + 23a^2 + 8a + 15}$



$\Rightarrow K=15$

$\frac{v_0}{v_1} = \frac{K}{a^6 + \dots + 8a + 15}$

