 





EE3303H
11/08/16


Page 1093 = pull-up & pull-down CMOS



$$Y = \overline{A + B}$$

$$\text{and} = \text{or} = +$$

   


 

pull-up


$$Y = \overline{A \cdot B} \quad , \quad \overline{\overline{A \cdot B}} = A + B$$

connected

 


$$\overline{Y} = A + B$$


mos

 


pull down


 


pull up



 


 


inverter combination

  






pass Transistor

   

 
\Rightarrow CMOS pass Transistor Page 1193
 is at gate B_p at V_{DD}
_n



Sketch, page 1239

     

3 equilibrium points

 

S R = set - next flip flop

