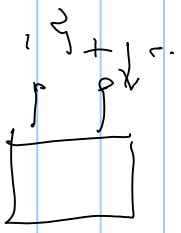


in saturation  
 $i_D = k_n (v_{GS} - V_{TO_n})^2 (1 + \lambda v_{DS})$   
 in ohmic

exponential

square law

$= k_n (2(v_{GS} - V_{TO_n})(v_{DS} - V_{DS}^2))$   
 iff  $i_D = 0$



$v = g v$ ,  $i = y v$

$g = 1/y$   
 $= y^{-1}$

Y eq. circuit



Y components in S-para  
 $Y = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$

hence no Z as  $\det Y = 0$

for our circuit  
 $Y = \begin{bmatrix} C_{11}R & -C_{12}R \\ -AC_{12} + g_m & AC_{22} + g_D \end{bmatrix}$

$$Y_1 = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}, Y_2 = \begin{bmatrix} 0 & -g_m \\ 0 & 0 \end{bmatrix} \Rightarrow Y = \begin{bmatrix} 0 & -g_m \\ g_m & 0 \end{bmatrix} \Leftarrow \text{a gyrator}$$

active

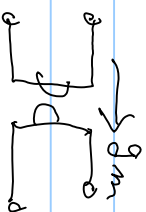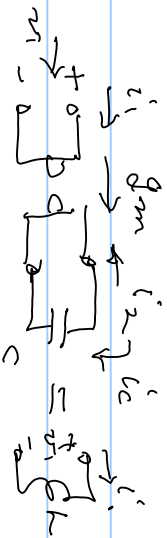

passive

$$+v_1 \text{ across } i_1 \quad \rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & -g_m \\ g_m & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


$$\rightarrow AC v_2 = -i_2 = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \Rightarrow i_1 = -g_m v_2$$

$$\rightarrow AC v_2 = g_m v_1, \quad i_1 = -g_m v_2$$

$$v_2 = -\frac{1}{g_m} i_1 \Rightarrow \text{AC} \left( \frac{-1}{g_m} \right) i_1 = g_m v_1 \Rightarrow v_1 = \frac{AC}{g_m} i_1$$

$$\frac{v_1}{i_1} = g_m = \frac{AC}{g_m} = AL \Rightarrow L = C/g_m \quad \text{if } g_m = 10^{-3} \Rightarrow L = 10^6 C$$
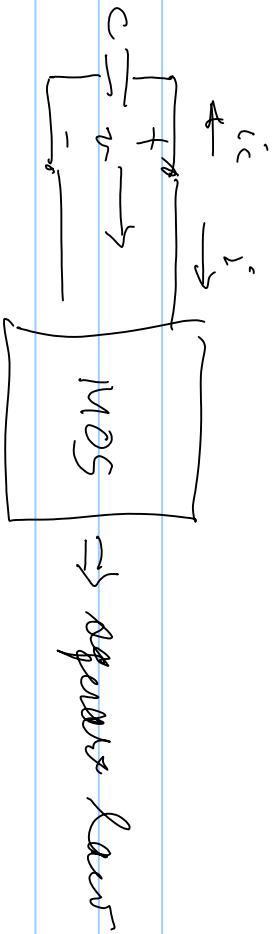
$$\text{if } C = 1 \mu F \Rightarrow L = 1 \text{ Henry}$$



$$\ddot{x} + ax^2 + bx + c = 0 \quad \text{Riccati equation}$$

$$\frac{dx}{dt} = -kx^2 + bx + c = -a(x-\alpha_1)(x-\alpha_2)$$

$$-a dt = \frac{dx}{(x-\alpha_1)(x-\alpha_2)} \Rightarrow \int_0^t (-a dx) = \int_{x(0)}^{x(t)} \frac{dx}{(x-\alpha_1)(x-\alpha_2)}$$

$$-a t = \int_{x(0)}^{x(t)} \left[ \frac{k_1}{(x-\alpha_1)} + \frac{k_2}{(x-\alpha_2)} \right] dx ; \quad \frac{1}{(x-\alpha_1)(x-\alpha_2)} = \frac{k_1}{(x-\alpha_1)} + \frac{k_2}{(x-\alpha_2)}$$


$$k_1 = \frac{1}{x-\alpha_2} \Big|_{x=\alpha_1} = \frac{1}{\alpha_1-\alpha_2}, \quad k_2 = \frac{1}{\alpha_2-\alpha_1}$$

$$= \int_{x(0)}^{x(t)} \left[ \frac{k_1}{x-\alpha_1} dx + \frac{k_2}{x-\alpha_2} dx \right] = \int_{x(0)-\alpha_1}^{x(t)-\alpha_1} \frac{k_1 dy}{y} + \int_{x(0)-\alpha_2}^{x(t)-\alpha_2} \frac{k_2 dy}{y}$$

$$-at = k \ln \left( \frac{\alpha(t) - \alpha_1}{\alpha(0) - \alpha_1} \right) + k \ln \left( \frac{\alpha(t) - \alpha_2}{\alpha(0) - \alpha_2} \right) = R_{e1} \left( \ln \left( \frac{\alpha - \alpha_1}{\alpha(0) - \alpha_1} \right) \right)$$


$$-\frac{a}{R_1} t = \ln \left( 3(\alpha) \right) \Rightarrow \frac{\alpha - \alpha_1}{\alpha - \alpha_2} \left( \frac{\alpha(0) - \alpha_2}{\alpha(0) - \alpha_1} \right) = e^{-at/R_1}$$

Current mirrors: F component in Spice

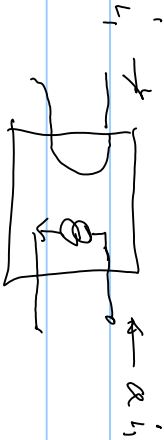

$$R_{D1} = \frac{V_{DD} - V_{GS}}{I_1}$$

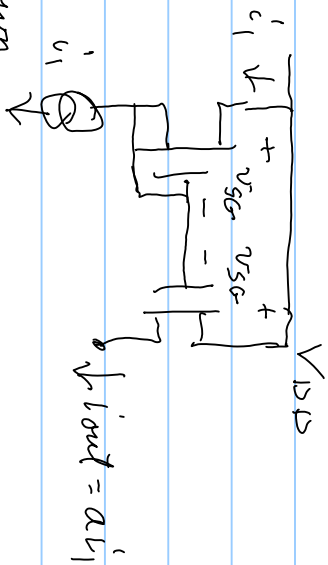
current only down  
 $\Rightarrow$  remaining current



$$I_1 = R_{D1} (V_{SG} - |V_{thp}|)^2$$

$$I_2 = R_{D2} (V_{SG} - |V_{thp}|)^2$$
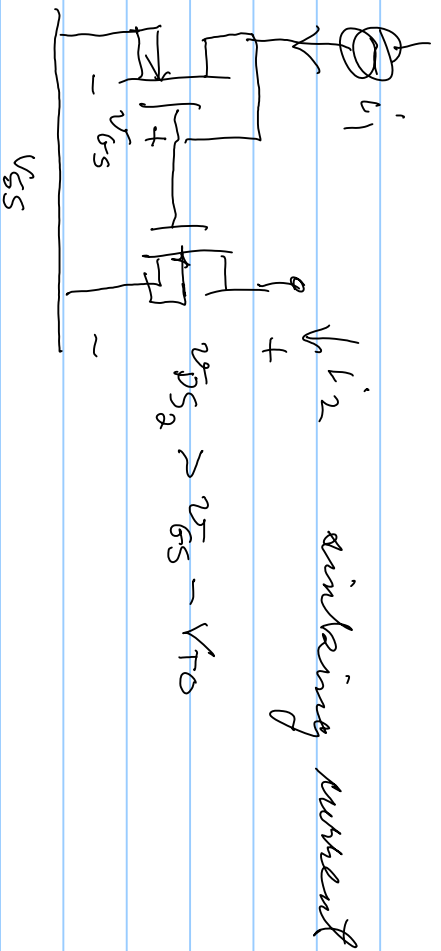
$$\frac{I_2}{I_1} = \frac{R_{D2}}{R_{D1}} = \frac{(W/L)_2}{(W/L)_1}$$



if bulk not at source then  $V_{T0} \rightarrow V_{th} = V_{T0} + \gamma (\sqrt{V_{SB} + \phi} - \sqrt{\phi})$

grounded drain amplifiers

