

Solutions 303K F2016 final


1. a) as $I_{DQ} = 1 \text{ mA}$, $v_{O1} = R I_{DQ} = 10^3 \times 10^{-3} = 1 \text{ V} \Rightarrow V_{DSQ} = V_{DD} - v_{O1} = 6 - 1 = 5 \text{ V} = V_{DSQ}$, $V_{GSQ} = V_{GS} - v_{O1} = 3 - 1 = 2 \text{ V} = V_{GSQ}$
 as $V_{DSQ} = 5 > V_{GSQ} - V_{TQ} = 2 - 1 = 1 \Rightarrow \text{saturation}$

b) as $I_{DQ} = 1 \text{ mA} = 10^{-3} = k(V_{GSQ} - V_{TQ})^2 (1 + \lambda V_{DSQ}) = k(1)^2 (1 + \frac{1}{10} \times 5) = k \times 1.5 = k \Rightarrow k = \frac{10^{-3}}{1.5} = \frac{2}{3} \times 10^{-3} \text{ A/V}^2$

c) $g_m = \frac{\partial I_D}{\partial V_{GS}} = 2k(V_{GS} - V_{TQ})(1 + \lambda V_{DS}) = 2 \cdot \frac{10^{-3}}{1.5} (1)^2 (1.5) = 2 \times 10^{-3} = g_m$

$g_o = \frac{\partial I_D}{\partial V_{DS}} = k(V_{GS} - V_{TQ})^2 \lambda = \frac{10^{-3}}{1.5} (1)^2 \cdot \frac{1}{10} = \frac{1 \times 10^{-4}}{1.5} = \frac{2}{3} \times 10^{-4} = 0.667 \times 10^{-4} = 0.0667 \times 10^{-3} = g_o$

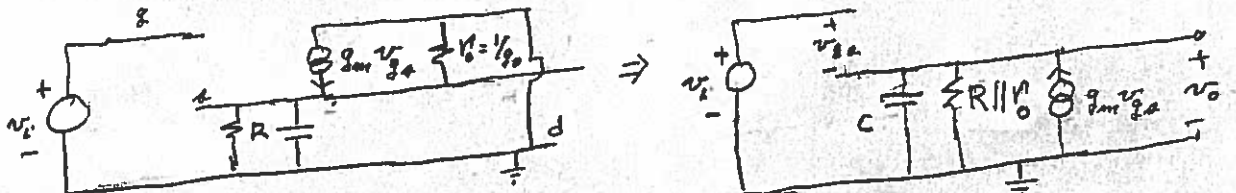d) as $C_{gs} = C_{gd} = 0$ the only capacitor is C ; $d \rightarrow$ find $v_{sd} = 0$



e) a) $v_{gs} = v_i - v_o$ by KVL, (b) $C \dot{v}_o + G_o v_o - g_m v_{gs} = 0$ by KCL; ($G_o = G + g_o$, $G = 1/R$)
 a) \Rightarrow b) $\Rightarrow C \dot{v}_o + G_o v_o - g_m v_i + g_m v_o \Rightarrow C \dot{v}_o + G_o v_o + g_m v_o = g_m v_i$, let $s = s = d/dt$
 $\frac{v_o}{v_i} = \frac{g_m}{sC + G_o + g_m} = \frac{2 \times 10^{-3}}{10^{-6} s + (10^{-3} + 0.067 \times 10^{-3} + 2 \times 10^{-3})} = \frac{2 \times 10^3}{s + 3.067 \times 10^3}$
 (note $\frac{v_o}{v_i}(0) = \text{DC gain} = \frac{2}{3.067} \approx 0.65$)

*2. $v_o(0_+) = \frac{V_{DD}}{3} \Rightarrow v_o(0_+) = 0 \Rightarrow v_{GS}(0_+) = 0 \Rightarrow M_n \text{ off}$
 $= v_o(0_+) = 3$

$\Rightarrow v_{SGM_n} = V_{DD}$ & $v_{SGM_p} = V_{DD} - v_o(0_+) = \frac{V_{DD}}{2} = 3$

$\Rightarrow |v_{SGM_p} - |v_{TPM_p}| = V_{DD} - \frac{1}{8}V_{DD} = \frac{5}{8}V_{DD} \gg \frac{V_{DD}}{2} = v_{SGM_p} = 3 \Rightarrow M_p \text{ on}$

as v_o increases with t , $v_{SD} = V_{DD} - v_o$ decreases while $v_{SG} = V_{DD} \Rightarrow$ remains in $\frac{1}{3} = 1$

$i_s = k_p \left[2(v_{SG} - |v_{TPM_p}|)v_{SD} - v_{SD}^2 \right] = k_p \left[2(V_{DD} - \frac{1}{8}V_{DD})(V_{DD} - v_o) - (V_{DD} - v_o)^2 \right]$

\therefore let $x = V_{DD} - v_o$, $x(0_+) = \frac{1}{2}V_{DD}$

$i_s = C \frac{dv_o}{dt} = C \frac{d(V_{DD} - x)}{dt}$, as $\frac{dV_{DD}}{dt} = 0$

at $x = V_{DD} - v_o \Rightarrow x(t_5) = V_{DD} - 5 = 1V$

$\Rightarrow -C \frac{dx}{dt} = k_p \left[2(\frac{5}{8}V_{DD})x - x^2 \right] \Rightarrow \frac{dx}{dt} + \frac{k_p}{C} \left[\frac{10}{8}V_{DD}x - x^2 \right] = 0 = \frac{dx}{dt} + \frac{k_p}{C} x(10 - x) = 0$

$\Rightarrow \frac{dx}{x(x-10)} = \frac{-k_p}{C} dt \Rightarrow \int_{x(0)}^{x(t)} \frac{dx}{x(x-10)} = \int_0^t \frac{-k_p}{C} dt = \frac{-k_p}{C} t$

Left side, use $\frac{1}{x(x-10)} = \frac{k_0}{x} + \frac{k_1}{x-10}$; $k_0 = \frac{x}{x(x-10)} \Big|_{x=0} = -\frac{1}{10}$, $k_1 = \frac{1}{x} \Big|_{x=10} = \frac{1}{10}$
 $= -\frac{1/10}{x} + \frac{1/10}{x-10}$

$\Rightarrow \int_{x(0)}^{x(t)} \frac{1}{10} \left[-\frac{1}{x} dx + \frac{1}{x-10} dx \right] = \frac{1}{10} \left[-\ln|x| + \ln|x-10| \right] \Big|_{x(0)}^{x(t)} = \frac{1}{10} \ln \left(\frac{|x-10|}{|x|} \right) \Big|_{x(0)=3}^{x(t)=1}$

$\therefore \frac{1}{10} \ln \left(\frac{|x(t)-10|}{|x(t)|} \cdot \frac{|x(0)|}{|x(0)-10|} \right) = \frac{-k_p}{C} t \Rightarrow \left| \frac{x(t)-10}{x(t)} \right| = \left| \frac{x(0)-10}{x(0)} \right| e^{10 \frac{k_p}{C} t} = \frac{7}{3} e^{10t}$

time to change = $t_5 = \frac{C}{k_p} \cdot \frac{1}{10} \ln \left(\left| \frac{1-10}{1} \right| \cdot \left| \frac{3}{7} \right| \right) = \frac{10^{-6}}{10^{-6}} \cdot \frac{1}{10} \ln \left(\frac{27}{7} \right) = \frac{1}{10} (1.35) = 0.135 \text{ sec}$

#3. a) Each branch has $y_j(s) = \frac{1}{R_j + \frac{1}{sC_j} + sL_j} = \frac{sC_j}{s^2L_jC_j + R_jC_js + 1} = \frac{\frac{1}{L_j} s}{s^2 + \frac{R_j}{L_j}s + \frac{1}{L_jC_j}} \neq 0$
as $R_j^2 > 4 \frac{1}{L_jC_j} > 0$

By KCL, the currents in there add to give the input current vs the input voltage which is the same for all

a) $y(s) = \frac{I}{V} = \sum_{j=1}^m y_j \cdot \frac{V}{V} = \sum_{j=1}^m y_j(s) = \sum_{j=1}^m \frac{\frac{1}{L_j} s}{s^2 + \frac{R_j}{L_j}s + \frac{1}{L_jC_j}} = s \sum_{j=1}^m \frac{\frac{1}{L_j}}{s^2 + \frac{R_j}{L_j}s + \frac{1}{L_jC_j}}$

The poles are at the zeros of the denominator polynomials so

a2) $p_j = -\frac{R_j}{2L_j} \pm \frac{1}{2} \sqrt{\left(\frac{R_j}{L_j}\right)^2 - 4 \frac{1}{L_jC_j}} \quad j=1, \dots, m$

a3) There is a zero at $s=0$

b) $y = \frac{s}{s^2+1} + \frac{s}{s^2+\frac{1}{4}}$

$I(s) = y V(s), V(s) = 1/s \Rightarrow I(s) = \frac{1}{s^2+1} + \frac{1}{s^2+\frac{1}{4}}$
(for $V(t)=1(t)$)

Using s as Laplace transform variable, $\mathcal{L}[f(t)] = \frac{1}{s^2+\omega_0^2} \Rightarrow f(t) = \frac{1}{\omega_0} \sin \omega_0 t$

$\Rightarrow i(t) = (\sin t + \frac{1}{2} \sin 2t) 1(t)$ which has $i(0_+) = i(0_-) = 0$