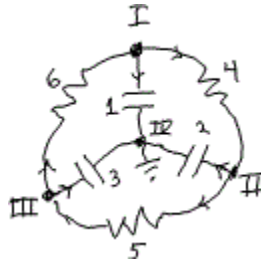


## EE 610 Final Exam Fall 2016

Open Book Open Notes 150 points, 2 hours.

Notebooks are due at the end of the exam. Good luck and have a good semester break.

1. (60 points, 40 minutes)



The above “wheel of circuit” has all resistors equal of resistance  $R=1/G$  and all capacitors of capacitance  $C$ . The nodes are numbered I, II, III, IV, the branches 1, 2, 3, 4, 5, 6, and directions are as given by the arrows.

- Use the capacitor branches as the tree and give the cut set and tie set matrices.
- Give the branch by branch admittance matrix.
- Excite by a current source connected from node IV into node I. Take as output the voltage at node I with respect to node IV. For these choices give the semi-state equations.
- Give the steps you would use to find the impedance seen by the input current source of part c).

2. (60 points, 40 minutes)

Consider the input impedance  $z(s) = [(s^2+1)(s^2+a)] / [s(s^2+4)]$

- For what values of  $a$  is this a lossless PR function?
- Give a 1st Foster synthesis for all  $a$  for which  $z(s)$  is PR.
- For any synthesis of  $z(s)$  replace every inductor by a capacitor of the same element value and vice versa (for example,  $L_{\text{new}}=C_{\text{old}}$ ). Give the resulting impedance  $z_{\text{new}}(s)$ .

3. (15 points, 10 minutes)

For the impedance of problem 2 find the sensitivity of  $z(s)$  to the parameter  $a$ .

4. (15 points, 10 minutes)

Without calculations draw the cascade synthesis of  $z(s)$  which would result from iterated use of the Richards' function. Justify your choice for load.