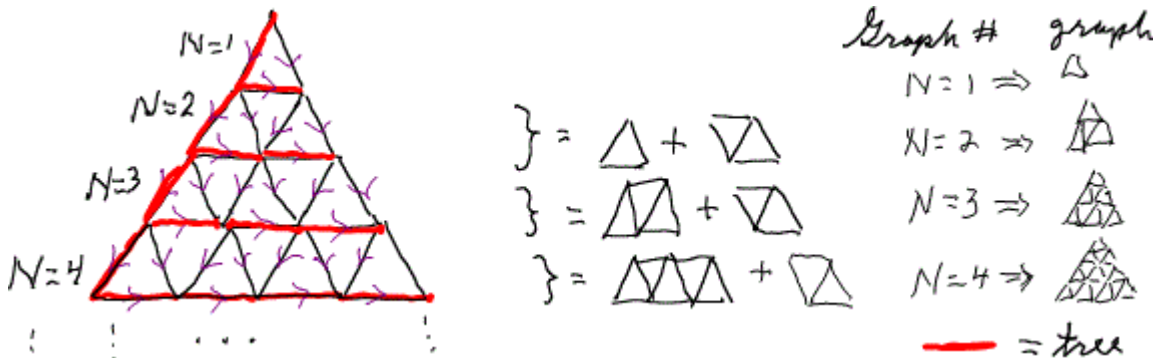
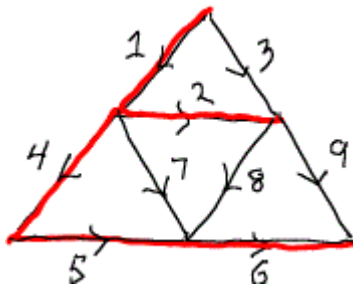


1. (40 points, Fractal Graph)

The following fractal graphs are indexed by positive integers N for which the Nth layer adds one bottom layer to the (N-1)th layer of the N-1st graph with two triangles on the right side added to the previous layers' patterns as illustrated.



- Give the total number of nodes, n_N , the total number of branches, b_N , the number of tree branches, t_N , and the total number of link branch, l_N , for $N=1,2,3$ and 4.
- Give a formula for calculating the sub-scripted-N quantities of part a) for any N.
- For the four triangle graph of $N=2$, numbered as follows, give the cut set and tie set matrices.



2. (60 points, Van der Pol Oscillator)

The Van der Pol oscillator is described by the state equations:

$$\begin{aligned} dx/dt &= y \\ dy/dt &= -\omega_0^2 x + \epsilon(r^2 - x^2)y \end{aligned}$$

- Set this up in Spice using two capacitors and G or GVALUE components. Normalize to $r=1$ and $\omega_0=1$ but with ϵ as a parameter. Run transient analysis for $\epsilon = 0.01, 1$ and 10 and for each plot the phase plane trajectory of $y(t)$ versus $x(t)$ (with x on the horizontal axis and y on the vertical; this can be set via the PLOT menu in PSpice). First use initial conditions $x(0)=y(0)=0$ and then investigate others including $x(0)=y(0)=2$.
- Draw a graph for the resulting circuit and choose a tree which includes the two capacitors. Represent a G components by two branches (these being the input voltage sensor and the output current source).

