
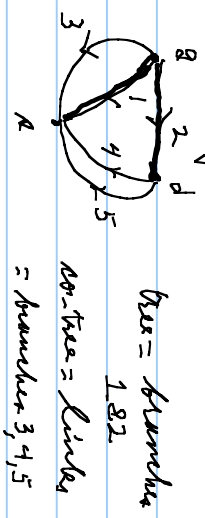


EE 610
08/30/16

Due to lack of computer facility in classroom this is a summary of blank board

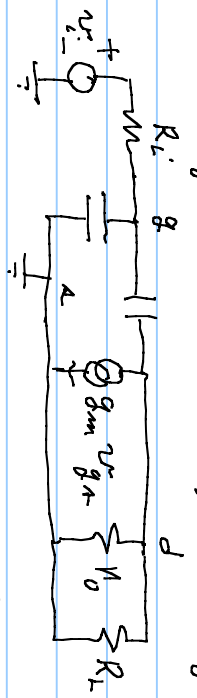Current graph example, linearized MOS amplifiers



KCL, cut I around branch 1 avoiding 2 $0 = i_1 + i_3 + i_4 + i_5$ in direction of the current

cut II around branch 2 avoiding 1 $0 = i_2 - i_4 - i_5$ in direction of the current

$$\text{or } \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = C i_b, \quad C = \text{cut set matrix} = \begin{bmatrix} 1 & 2 \\ 1 & 2 \\ 1 & 2 \\ 1 & 2 \\ 1 & 2 \end{bmatrix} K$$

general = $\begin{bmatrix} 1 & 2 \\ 1 & 2 \\ 1 & 2 \\ 1 & 2 \\ 1 & 2 \end{bmatrix} K$, $T = \#$ of tree branches

KVL for branch 3, take away 4 & 5, in direction of branch 3

Then for 4 & 5 then 5

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 \\ -1 & 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = G v_b, \quad G = \text{the set matrix} = \begin{bmatrix} -1 & 2 \\ 1 & 2 \\ 1 & 2 \end{bmatrix}$$

general = $\begin{bmatrix} -1 & 2 \\ 1 & 2 \\ 1 & 2 \end{bmatrix} K$, $K = \#$ links

$$C \cdot \mathcal{G}^T = \begin{bmatrix} A_T & K \end{bmatrix} \begin{bmatrix} -K \\ A_X \end{bmatrix} = -K + K = 0_{T \times R},$$

$T = \# \text{ of tree branches}$
 $R = \# \text{ of link branches}$
 $b = R + T = \# \text{ of branches}$
 $M = \# \text{ of nodes}$

also follows from total power in from outside a covering sphere as

$$P_n(t) = \text{sum of powers in branches} \quad \Rightarrow \quad T = M + 1$$

for a connected graph
(= 1 separate part)

using $v_b^T = C^T v_T$, $i_b = \mathcal{G}^T i_T$, $\hat{\Gamma} = \text{transpose}$

also holds if use one tree for KCL & one for KVL and if C is for one circuit and \mathcal{G} another if the circuits have the same graph.
 C and \mathcal{G} connect individual parts.