
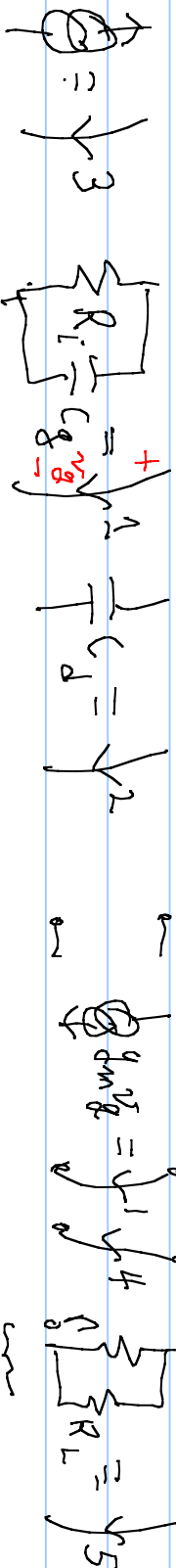
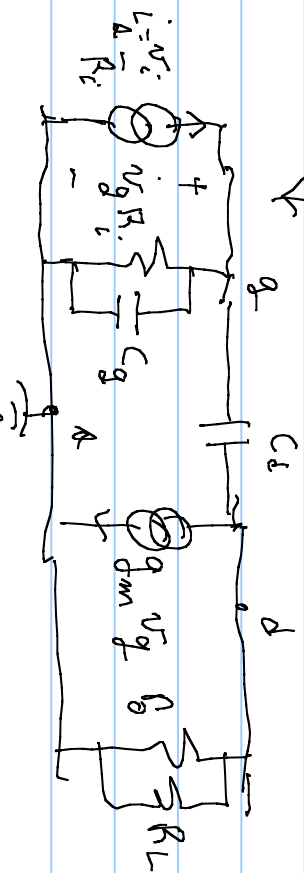


EE610
09/01/16

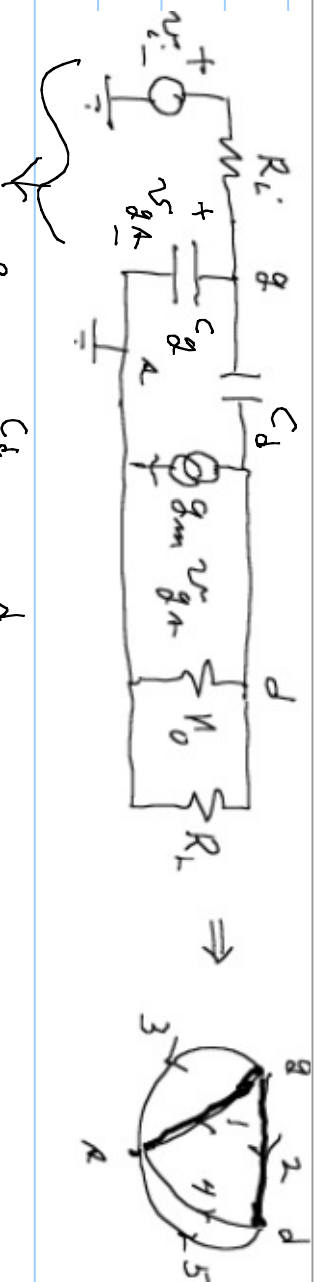

$$g_c = 1/R_i$$


$$G_o = g_o + G_L$$

$$= \frac{1}{R_o} + \frac{1}{R_L}$$

$Y_{b \times b}$ = branch by branch admittance matrix $b = \#$ of branches
 $= 5$

$$\begin{bmatrix} i_1' \\ i_2' \\ i_3' \\ i_4' \\ i_5' \end{bmatrix} = \begin{bmatrix} g_1 + sC_g & 0 & 0 & 0 & 0 \\ 0 & sC_g & 0 & 0 & 0 \\ 0 & 0 & g_m & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & G_0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}$$

$$i' = Y_{b \times b} v$$

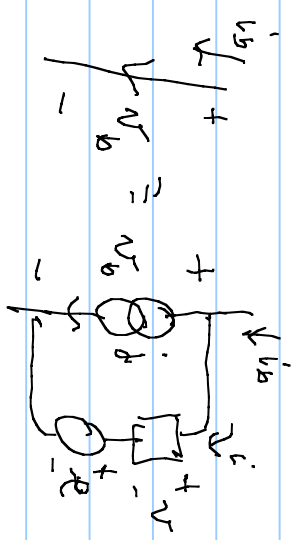

$$\Rightarrow i_b = i + j \quad \Rightarrow i_b = \sigma^T i_r, \quad O = E i_b$$

$$\Rightarrow v_b = v + e \quad \Rightarrow v_b = E^T v_f, \quad O = \sigma^T v_b$$

$$i_b = i + j = Y_{b \times b} v + j$$

$$= Y_{b \times b} (v_b - e) + j$$

$$j = \begin{bmatrix} 0 \\ 0 \\ -i_a \\ 0 \\ 0 \end{bmatrix} \quad e = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$0 = e_i b = e^{Y_{0 \times b}} v_b + 0 + e_j$$

$$= e^{Y_{0 \times b}} e^T v_f + e_j \Rightarrow -e_j = [e^{Y_{0 \times b}} e^T] v_f$$

$$Y_{f \times f} = \begin{bmatrix} 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} q_i + R G_q & 0 & 0 & 0 & 0 \\ 0 & R G_d & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ q_m & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & G_o \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & -1 \\ 1 & -1 \end{bmatrix}$$

$$-e_j = - \begin{bmatrix} 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ -G_q \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} +G_q \\ 0 \end{bmatrix} = Y_{f \times f} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\text{hence } v_f = v_f^{-1} \cdot (-e_j)$$

$$= \begin{bmatrix} 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} g_L + K C_g & 0 & 0 & 0 & 0 \\ 0 & K C_g & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ g_m & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & G_0 \end{bmatrix} = \begin{bmatrix} g_L + K C_g + g_m & 0 & 0 & 0 & 0 \\ -g_m & K C_g & 0 & 0 & -G_0 \end{bmatrix}$$

$$= E Y_{6 \times 5}$$

$$\begin{bmatrix} g_L + K C_g + g_m & 0 & 0 & 0 & G_0 \\ -g_m & K C_g & 0 & 0 & -G_0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & -1 \\ 1 & -1 \end{bmatrix} = \begin{bmatrix} g_L + g_m + K C_g + G_0 & -G_0 \\ -g_m & -G_0 & K C_g + G_0 \end{bmatrix} = E Y_{6 \times 5}^T$$

$$\begin{bmatrix} +L_A \\ 0 \end{bmatrix} = \begin{bmatrix} g_L + g_m + K C_g + G_0 & -G_0 \\ -g_m & -G_0 & K C_g + G_0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} A C_d + G_0 & G_0 \\ g_m + G_0 & g_i + g_m + G_0 + A C_g \end{bmatrix} \begin{bmatrix} i_a \\ 0 \end{bmatrix}; \Delta = \text{determinant}$$


$$= (A C_d + G_0)(g_i + g_m + G_0 + A C_g) - G_0(g_m + G_0)$$

Arbitrary components nullator $v=0, i=0$ with $n-1$ nullators, $v=$ arbitrary, $i=$ arbitrary independent

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix} v = \begin{bmatrix} 0 \\ 1 \end{bmatrix} i$$

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} [v] = \begin{bmatrix} 0 \\ 0 \end{bmatrix} [i] \Rightarrow \left[\infty \right]$$

(op amp output)

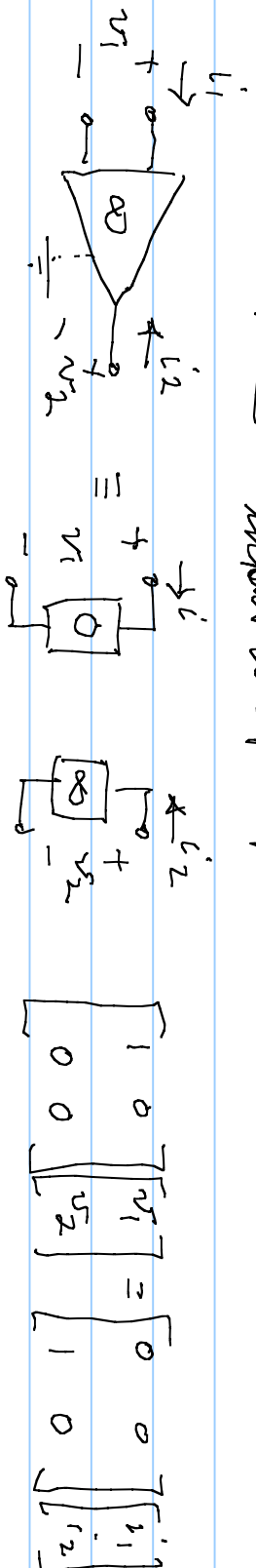

of linear components, for the $\begin{bmatrix} x_i \\ v_i \end{bmatrix}$ pairs of branches:

$$Av = Bi$$

for any non-singular C $i = Yv$ if $Y = \text{admittance matrix}$

$$Y = B^{-1}A, \quad \text{for } C = B^{-1}$$

$$CAv = CBi \quad Z = Y^{-1} = A^{-1}B \quad \text{for } C = A^{-1}$$