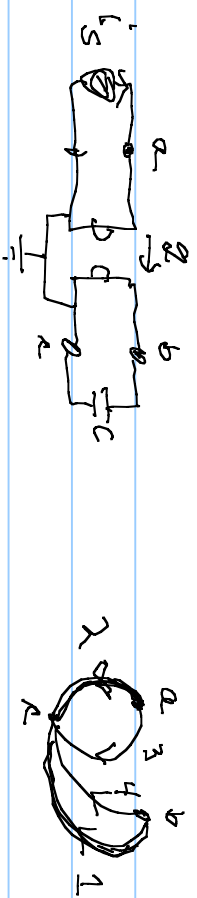


EE 610
09/08/16

$$\underbrace{\begin{Bmatrix} b \\ n \end{Bmatrix}}_{b \text{ columns}} \left[A \underbrace{e^T}_{i} - B \underbrace{q^T}_{r} \right] \begin{bmatrix} v_i \\ i_r \end{bmatrix} = A x - B q = M x, \quad x = \begin{bmatrix} v_i \\ i_r \end{bmatrix}, \text{ vector}$$

$A e^T$ is $b \times t$ columns, $-B q^T$ is b rows & columns
 gives b eqs in b unknowns

Example:



$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad g = \text{gyration conductance}$$

$$A v = B i, \quad i = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}, \quad v = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}$$

$$\begin{bmatrix} R & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -g & 0 \\ 0 & 0 & g & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} v = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} i$$

$$[0] = \left[\begin{array}{ccc|ccc} 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 1 & 0 & 0 \end{array} \right] \begin{matrix} u_4 \\ u_5 \\ u_6 \end{matrix} \Rightarrow 0 = e_{i_4} \quad [0] = \left[\begin{array}{ccc|ccc} 0 & -1 & 1 & 1 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 1 \end{array} \right] \begin{matrix} v_4 \\ v_5 \\ v_6 \end{matrix} \Rightarrow 0 = \sigma^T v_6$$

$$e^T = \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 1 \\ 1 & 0 \end{bmatrix}, \quad \sigma^T = \begin{bmatrix} 0 & -1 \\ -1 & 0 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} \quad \text{check } e \sigma^T = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$

$$A e^T = \begin{bmatrix} a & c & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -g & 0 & 0 \\ 0 & 0 & 0 & 0 & g & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 1 \\ 1 & 0 \end{bmatrix} = \begin{bmatrix} a & c & 0 \\ 0 & 0 & 0 \\ -g & 0 & 0 \\ 0 & g & 0 \end{bmatrix}; \quad B \sigma^T = \begin{bmatrix} 0 & -1 \\ -1 & 0 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & -1 \\ -1 & 0 \\ -1 & 0 \\ 1 & 0 \end{bmatrix}$$

$$[A e^T; -B \sigma^T] = \begin{bmatrix} a & c & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \\ -g & 0 & 0 & -1 & 0 \\ 0 & g & 0 & 0 & -1 \end{bmatrix}; \quad \begin{matrix} u_1 \\ u_2 \\ u_3 \\ u_4 \end{matrix}, \quad \mathcal{R} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}, \quad \begin{matrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{matrix} = \begin{bmatrix} 0 \\ 0 \\ -1 \\ 0 \end{bmatrix}$$

$$A \mathcal{R} = \underline{0}_4, \quad B \mathcal{V} = \underline{1}_4; \quad \mathcal{V} = [0 \ -1 \ 0 \ 0]^T \Rightarrow -B \mathcal{V} = [0 \ 1 \ 0 \ 0]^T$$

$$\begin{bmatrix} AC & 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 & 0 \\ -g & 0 & 0 & -1 & 0 \\ 0 & 0 & g & 0 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ +is \\ 0 \\ 0 \end{bmatrix}$$

divide the circuit

$$\begin{bmatrix} 1 \\ 2 \end{bmatrix} \begin{bmatrix} v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} -g & 0 \\ 0 & g \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow \begin{bmatrix} AC & 0 \\ 0 & 0 \end{bmatrix} v_1 + \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ +is \end{bmatrix}$$

$$\begin{bmatrix} AC & 0 \\ 0 & 0 \end{bmatrix} v_1 + \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} -g & 0 \\ 0 & g \end{bmatrix} v_1 = \begin{bmatrix} AC & g \\ -g & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 \\ +is \end{bmatrix}$$

$$AC v_1 + g v_2 = 0 \Rightarrow v_1 = -\frac{g}{AC} v_2$$

$$-g v_1 + 0 v_2 = -is \Rightarrow \frac{g^2}{AC} v_2 = +is \Rightarrow \begin{matrix} \xrightarrow{v_2 = is} \\ \left[\begin{matrix} 0 & 1 \\ 1 & 0 \end{matrix} \right] \end{matrix} v_2 \approx \frac{C}{gR}$$

$$g^2 v_1 = AC is \Rightarrow v_1 = A \left(\frac{C}{gR} \right) is$$

$$H = \frac{C}{s} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \frac{1}{s} = \frac{C}{s}$$

$$g = 1/n = 10^{-3}$$

$$C = 1 \mu\text{Sd} \Rightarrow k = \frac{C}{g} = \frac{10^{-6}}{10^{-6}} = 1 \text{ Hz}$$

$$\begin{bmatrix} a & c & 0 & 1 & 0 & 1 \\ 0 & 0 & 0 & 1 & 1 & 0 \\ -g & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & g & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \\ u_4 \end{bmatrix} = \begin{bmatrix} D \\ D \\ +1 \\ 0 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} a & c & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} x + \begin{bmatrix} 0 & 0 & 0 & -1 \\ 0 & 0 & -1 & 0 \\ g & 0 & 1 & 0 \\ 0 & -g & 0 & 1 \end{bmatrix} x + \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} z_s$$

$$E \frac{dx}{dt} = A x + B u, \quad n = \text{input}$$

$$E = \begin{bmatrix} c & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \text{ is singular} \quad \text{semi-state equations}$$

$$y = \text{output}, \quad u = \text{input}$$

$$x = \text{semi-state}$$

$$y = [e] x \quad \text{if } y \text{ is a linear combination of voltages \& currents in the circuit}$$

$$\begin{aligned} \text{E} \frac{dx}{dx} &= ax + b \\ y &= e^x \end{aligned} \quad \left. \vphantom{\begin{aligned} \text{E} \frac{dx}{dx} &= ax + b \\ y &= e^x \end{aligned}} \right\} \text{generics semi-otata eqs.} \\ & \text{differential-observa eqs.}$$