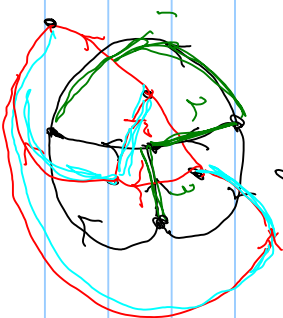


EE610
09/20/16

Dual $v \rightarrow i^d, i \rightarrow v^d$



$$i = C \frac{dv}{dt} \Rightarrow v = C \frac{di}{dt} \Rightarrow C \Rightarrow L \neq \text{inductor}$$

Dual graph \Rightarrow planar graphs
Technique



— = dual graph
— tree of dual
— tree of original

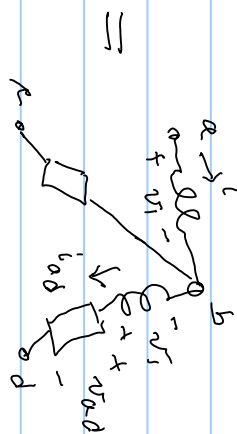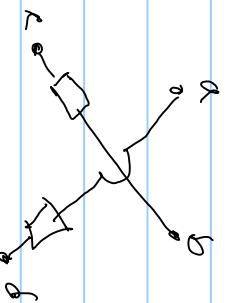if unavoidable crossing wires (branches) no graph dual



\Rightarrow allows for planar graphs with no change in equations

splitting matrix; $AV = B \begin{matrix} i \\ i \\ i \end{matrix}$; $av^i = v^i + i$; $av^i = v^i - i$

dual of system

$$\begin{bmatrix} v_1^i \\ \vdots \\ v_2^i \end{bmatrix} = \begin{bmatrix} 0 & -g^d \\ g^d & 0 \end{bmatrix} \begin{bmatrix} v_1^i \\ v_2^i \end{bmatrix} \Rightarrow v^i = Y v^i$$

$$\begin{bmatrix} v_1^d \\ v_2^d \end{bmatrix} = \begin{bmatrix} 0 & -g^d \\ g^d & 0 \end{bmatrix} \begin{bmatrix} v_1^d \\ v_2^d \end{bmatrix} \Rightarrow v^d = Z v^d \quad g^d = v^d$$

$$\begin{bmatrix} v_1^d \\ v_2^d \end{bmatrix} = Y^d \begin{bmatrix} v_1^d \\ v_2^d \end{bmatrix} \Rightarrow (Z^d)^{-1} = Y^d$$

$$Z^d = \begin{bmatrix} 0 & -g^d \\ g^d & 0 \end{bmatrix} = \begin{bmatrix} 0 & -v^d \\ v^d & 0 \end{bmatrix}, \quad (Z^d)^{-1} = \frac{1}{v^d} \begin{bmatrix} 0 & v^d \\ -v^d & 0 \end{bmatrix} = Y^d = \begin{bmatrix} 0 & 1/v^d \\ -1/v^d & 0 \end{bmatrix}$$



$$v^i = v^i + v^n, \quad i = v^i - v^n = A(v^i + v^n) = B(v^i - v^n)$$

$$(A+B)v^n = (B-A)v^i; \quad v^n = S v^i \Rightarrow S = (A+B)^{-1}(B-A)$$

$$g = Y v^i \Rightarrow A = Y, B = I_m; \quad S = (I_m + Y)^{-1}(I_m - Y)$$

$$(I_m + Y)S = (I_m - Y) \Rightarrow S + YS = I_m - Y \Rightarrow S - I_m = -Y - YS$$

$$= -(Y)(S + I_m)$$


$$S = (I_m - S)^{-1}(I_m + S)$$

$$(I_m + M)^{-1}(I_m - M) = (I_m - M)^{-1}(I_m + M)$$

$$(I_m - M)(I_m + M) = (I_m + M)(I_m - M)$$


$$(I_m + M - M - M^2) = (I_m + M - M - M^2)$$

Passivity:

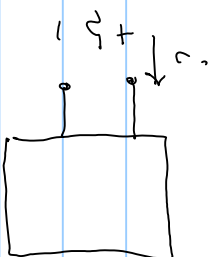

$$P(t) = v^T(t), i(t)$$
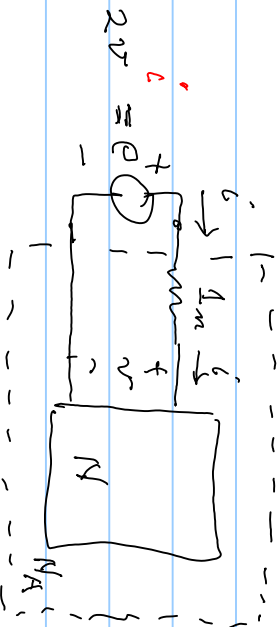
$$E(t) = \int_{-\infty}^t P(\tau) d\tau = \int_0^t v^T(\tau) i(\tau) d\tau + E(0) \geq 0 \text{ defines passive}$$



$$2v = v - i, \quad 2v = v + i$$

$$v = v' + v''$$

$$i = v' - v''$$

$$v^T i = (v' + v'')^T (v' - v'')$$

$$= (v'^T + v''^T) (v' - v'')$$

$$= v'^T v' - v'^T v'' + v''^T v' - v''^T v'' = 0$$

$$P(t) = \underbrace{v^T i}_{\text{instant}} - \underbrace{v^T v}_{\text{reflected}} + \underbrace{v''^T v''}_{\text{power}}$$

$$E_{CE1} = \int_{-\infty}^t [v^{i,T}(t), v^i - v^{(n)}v^{(n)}] dx \quad \text{if } \geq 0 \text{ then incident dominates reflected}$$

If $v^i = c/2$ is finite energy incident then for a passive network ($N = \text{network}$) then the reflected energy is finite

$$\text{def } \int_{-\infty}^t [v^{i,T}(t), v^i] dx = \int_{\text{network}} (up to time t) = \|v^i\|_{L_2}^2$$

$$\text{can drop } v^{i,T}(t) \text{ at } t_0 \quad \int_{-\infty}^{t_0} = \int_{-\infty}^{t_0} + 0 = \int_{-\infty}^{\infty}$$

$$\|v^i\|_{L_2}^2 \geq \|v^o\|_{L_2}^2 \geq 0 \quad \text{for a passive circuit}$$

If Separable, true if N is passive, then $v^i = Y_A \cdot E = Y_A (2v^i)$

$$v^i = 2v^o = (E - i) \cdot i = E - 2v^o \quad 2v^o = v^i \\ = E - 2Y_A E = (I_n - 2Y_A) E = 2v^o$$

$$Y^N = (I_m - 2\gamma A) Y^i \Rightarrow S = I_m - 2\gamma A \quad \left. \vphantom{S = I_m - 2\gamma A} \right\} \text{ explicit if } N \text{ is parabolic}$$

$$E_{X^i} \quad \begin{array}{c} \xrightarrow{1} \\ \xrightarrow{2} \end{array} \quad \begin{array}{c} \xrightarrow{1} \\ \xrightarrow{2} \end{array} \quad Y = \begin{bmatrix} aC & -aC \\ -aC & aC \end{bmatrix}; \quad S = (I_m + \gamma)^{-1} (I_m - \gamma)$$

$$I_2 + \gamma = \begin{bmatrix} 1+aC & -aC \\ -aC & 1+aC \end{bmatrix}, \quad (I_2 + \gamma)^{-1} = \frac{1}{\underbrace{(1+aC)^2 - (aC)^2}_{1+2aC}} \begin{bmatrix} 1+aC & aC \\ aC & 1+aC \end{bmatrix}$$

$$I_m - \gamma = \begin{bmatrix} 1-aC & aC \\ aC & 1-aC \end{bmatrix}$$

$$S(a) = \frac{1}{1+2aC} \begin{bmatrix} 1+aC & aC \\ aC & 1+aC \end{bmatrix} \begin{bmatrix} 1-aC & aC \\ aC & 1-aC \end{bmatrix} = \frac{1}{1+2aC} \begin{bmatrix} 1 & 2aC \\ 2aC & 1 \end{bmatrix}$$

$$S(-a) = \frac{1}{1-2aC} \begin{bmatrix} 1 & -2aC \\ -2aC & 1 \end{bmatrix}; \quad S(a)S(-a) = \frac{1}{1-4a^2C^2} \begin{bmatrix} 1-4a^2C^2 & 0 \\ 0 & 1-4a^2C^2 \end{bmatrix} = I_2$$

lowlat \Leftrightarrow $\mathcal{E}(\infty) = 0$ & passive