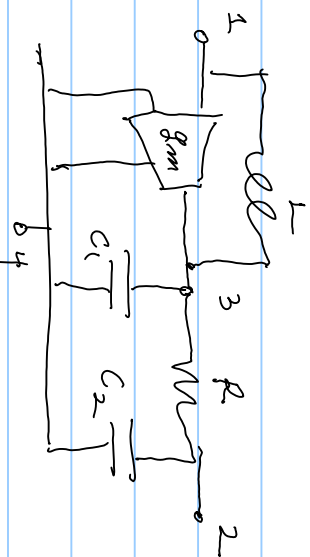


EE 610
09/22/16

Indefinite admittance




$$i_1 = \frac{1}{R_L} (v_1 - v_3), \quad i_2 = G(v_2 - v_3) + R C_2 (v_2 - v_4)$$

$$i_3 = \frac{1}{R_L} (v_3 - v_1) + g_m (v_1 - v_4) + R C_1 (v_3 - v_4) + G (v_3 - v_2)$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} \frac{1}{R_L} & 0 & -\frac{1}{R_L} & 0 \\ 0 & G + R C_2 & -G & -R C_2 \\ -\frac{1}{R_L} + g_m & -G & \frac{1}{R_L} + R C_1 + G & -g_m - R C_1 \\ -g_m & -R C_2 & -R C_1 & g_m + R (C_1 + C_2) \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$

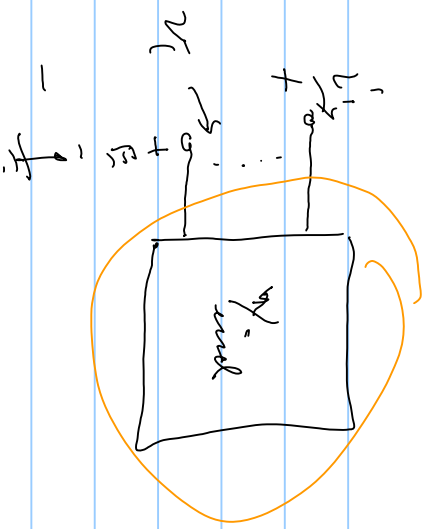\Rightarrow \sum of entries in a row = 0
 \Rightarrow \sum of entries in a column = 0



$$\sum i_i' = 0 \text{ by KCL}$$

$$i_i' = Y(v_1 + E_1)$$

vector

$$\begin{bmatrix} E_1 \\ E_2 \\ E_3 \\ E_4 \end{bmatrix}$$

If ground node 4 $\Rightarrow v_4 = 0$; $i_4 = i_1 + i_2 + i_3$ can ignore

$$Y_{\text{nodal}} = \begin{bmatrix} \frac{1}{R_L} & 0 & -\frac{1}{R_L} \\ 0 & G + R_2 & -G \\ -\frac{1}{R_L} + g_m & -G & \frac{1}{R_L} + G \end{bmatrix}$$

If eliminate internal node 3 $\Rightarrow i_3 = 0$, set find v_3 in terms of other voltages (v_1 & v_2) to $Y_{2 \times 2}$ matrix


$$v_3' = \left[-\frac{1}{R_L} + g_m \quad -G \right] \begin{bmatrix} v_1' \\ v_2' \end{bmatrix} + \left[G + R_C + \frac{1}{R_L} \right] v_3' = 0$$


$$-v_3' = \left[G + R_C + \frac{1}{R_L} \right]^{-1} \begin{bmatrix} -\frac{1}{R_C} + g_m & -G \end{bmatrix} \begin{bmatrix} v_1' \\ v_2' \end{bmatrix}$$

$$\begin{bmatrix} v_1' \\ v_2' \end{bmatrix} = \begin{bmatrix} \frac{1}{R_L} & 0 \\ 0 & G + R_C \end{bmatrix}^{-1} \begin{bmatrix} -\frac{1}{R_L} \\ -G \end{bmatrix} \begin{bmatrix} G + R_C + \frac{1}{R_L} \\ \frac{1}{R_C} + g_m - G \end{bmatrix} \begin{bmatrix} v_1' \\ v_2' \end{bmatrix}$$

$$v_{\text{approx}} = \begin{bmatrix} \frac{1}{R_L} & 0 \\ 0 & G + R_C \end{bmatrix}^{-1} \begin{bmatrix} -\frac{1}{G + R_C + \frac{1}{R_L}} \\ \frac{-\frac{1}{R_L} + g_m}{R_L} + g_m \end{bmatrix} \begin{bmatrix} -\frac{1}{R_L} (-G) \\ (-G) \left(\frac{1}{R_L} + g_m - G \right) \end{bmatrix}$$

Circuit diagram:

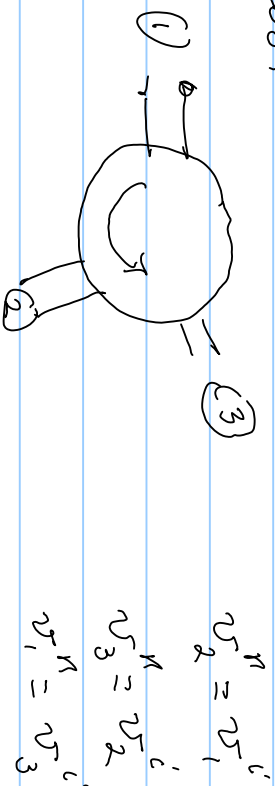

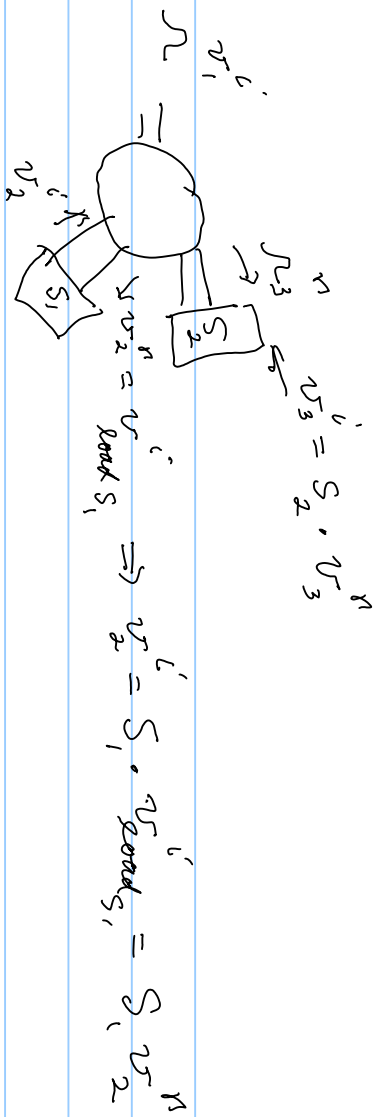

$$u_1^o = u_3^i = S_2 \cdot u_2^i = S_2 \cdot S_1 \cdot u_1^i = S_2 \cdot S_1 \cdot u_1^i$$

$$\Rightarrow S = S_2 \cdot S_1$$

→ parseval

$$\int_{-\infty}^{\infty} u^i(t) u^i(t) dt = \int_{-\infty}^{\infty} u^o(t) u^o(t) dt \geq 0 \text{ of parseval}$$

Parseval's theorem

$$\int_{-\infty}^{\infty} f(t) \star g(t) dt = \int_{-\infty}^{\infty} F(j\omega) \star G(j\omega) \frac{d\omega}{2\pi}$$

$F(j\omega) =$ Fourier Transform of $f(t)$

$$\int_{-\infty}^{\infty} V^{i'TX} V^{i'} dt = \int_{-\infty}^{\infty} V^{i'TX} V^{i'} \frac{d\omega}{2\pi}$$

$$- \int_{-\infty}^{\infty} V^{i'TX} V^{i'} \frac{d\omega}{2\pi} = - \int_{-\infty}^{\infty} V^{i'TX} V^{i'} \frac{d\omega}{2\pi} = - \int_{-\infty}^{\infty} V^{i'TX} V^{i'} \frac{d\omega}{2\pi}$$

≥ 0 if positive $\Rightarrow \geq 0$ if positive.

$$\int_{-\infty}^{\infty} V^{i'TX} [I_n - S^{TX}(j\omega) S(j\omega)] V^{i'} \frac{d\omega}{2\pi} \geq 0 \text{ if positive}$$

$\Rightarrow I_n - S^{TX}(j\omega) S(j\omega)$ is positive (semi)-definite
Hermitian form

\Rightarrow for real systems $S^{*}(j\omega) = S(-j\omega)$

no poles of $S(s)$ in $\sigma > 0$ where $R = \sigma + j\omega$, $\sigma > 0$ means the right half plane

The lossless $I_n - S(j\omega)S^T(j\omega) \equiv 0_n$ on all of $j\omega$ axis, $-\infty \leq \omega \leq \infty$
 can extend to whole s -plane \Rightarrow
 lossless $I_n = S(-s)S^T(s) \Leftrightarrow S^T(s) = S^{-1}(-s)$

Ex:
$$S = (1+y)(1-y)^{-1} = (1+ac)^{-1}(1-ac) = \frac{1-ac}{1+ac}$$

$$S^{-1} = \frac{1+ac}{1-ac} = S(-s)$$

Bounded-real

- 1) $S^*(s) = S^T(s^*)$ in $\sigma > 0$ (a real circuit)
- 2) No singularities in $\sigma > 0$ (stability)
(no poles on $j\omega$ axis)
- 3) $I_n - S^T(s)S(s)$ is positive (passive)
semi-definite

if $S(s)$ is rational & bounded-real \Rightarrow BR & we can design

$$\int_{-\infty}^{\infty} \frac{(V(j\omega) + I(j\omega))^T (V(j\omega) + I(j\omega)) - (V(j\omega) - I(j\omega))^T (V(j\omega) - I(j\omega))}{2} \frac{d\omega}{2\pi} > 0$$

a passive circuit

$$\int_{-\infty}^{\infty} [I^{T*} V + V^{T*} I] - [-I^{T*} V - V^{T*} I] d\omega \frac{1}{2\pi} > 0$$

$$\int (V^{T*} Y^{*T} \cdot V + V^{T*} Y V) \frac{d\omega}{4\pi} > 0$$

$$\int V^{T*} [Y^{T*} Y^{(j\omega)} + Y^{(j\omega)}] V \cdot \frac{d\omega}{4\pi} > 0 \text{ necessary}$$

$\Rightarrow Y^{(j\omega)} + Y^{(-j\omega)^T}$ is positive semidefinite for all ω
for which it exists

\Rightarrow extend to $a = i$

lowest $Y(a) + Y(-a)^T = 0_n$

Ex: $Y(a) = aC \quad aC + (-a)C = 0$