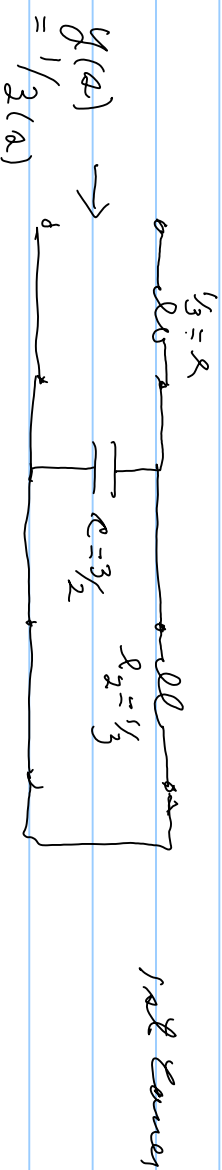


EE610  
10/05/16

$$y(s) = \frac{3(s^2+2)}{s(s^2+4)} = \frac{1}{s} + \frac{1}{\frac{3}{2}s + 1} + \frac{1}{\frac{1}{3}s + 0}$$

continued fraction expansion about  $s = \infty$



downward  $v \leftrightarrow i$   $z \leftrightarrow y$

$$y(s) = z(s) \quad \text{example: } z = y^D = \frac{3(s^2+2)}{s(s^2+4)} = \frac{1}{s} + \frac{1}{\frac{3}{2}s + 1} + \frac{1}{\frac{1}{3}s}$$

$$y = \frac{R(R^2 + 4)}{3(R^2 + 2)}$$

deal of the above

in terms of SCA:  $2v^i = v^i + i$ ,  $2v^N = v^i - i$

$$2v^i = 2v^i \text{ ID} = i + v^i, \quad 2v^N = i - v^i = -(v^i - i) = -2v^N$$

$$v^N \approx S v^i, \quad v^N \text{ ID} = S v^i \text{ ID} = S v^i = -v^N, \quad v^N = -S v^i$$

$$\Rightarrow S^D = -S$$

$$S = (I_m + Y)^{-1} (I_m - Y), \quad S^D = (I_m + Y^D)^{-1} (I_m - Y^D)$$

$$= (I_m + Z)^{-1} (I_m - Z)$$

$$= (I_m + Y^{-1})^{-1} (I_m - Y^{-1})$$



$$= (Y^{-1} (Y + I_m))^{-1} Y (Y - I_m)$$

$$\sim S = \sim (I_m + Y)^{-1} (I_m - Y) = (Y + I_m) (Y - I_m)$$

RC circuits :

convert LC to RC by  $L \Rightarrow R$
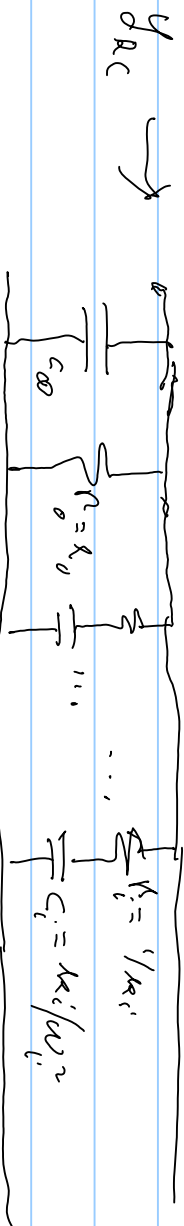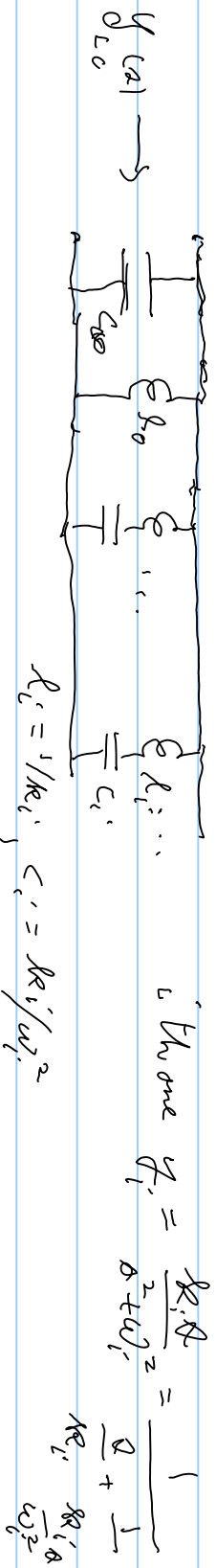
$$\text{for LC } y_{LC}(s) = R_{\infty} s + \frac{R_0}{s} + \sum \frac{R_i' s}{s^2 + \omega_i'^2}$$



$$y_i' = \frac{R_i' s}{s^2 + \omega_i'^2} = \frac{1}{\frac{s}{R_i'} + \frac{1}{\omega_i'^2}} = \frac{R_i' s}{s^2 + \omega_i'^2} \left[ \frac{R_i' s}{s^2 + \omega_i'^2} \right]$$

$$y_{RC} = K_{\infty} + K_0 + \sum \frac{K_i s^a}{s + \omega_i^2}$$

$\infty$   $\times$   $\frac{-\times}{-\omega_2^2}$   $\times$   $\frac{-\times}{-\omega_1^2}$

not in  
residue  $\Rightarrow$   $\frac{m_i}{s + \omega_i^2}$  not  $K_i s^a$   
form  $\underbrace{\hspace{1cm}}$  from  $\underbrace{\frac{R + \omega_i^2}{s}}$  comes from the current  
residual fraction expansion


$\therefore$  form  $\frac{y_{RC}}{s} = K_{\infty} + \frac{K_0}{s} + \sum \frac{m_i}{s + \omega_i^2}$  This is a partial fraction  
expansion with  
simple poles and  
positive residues

$$y_{RC}(s) = \frac{s(R+s+4)}{s^2 + 2s + 2} \quad ; \quad \frac{y_{RC}}{s} = \frac{s+4}{s+2} = 1 + \frac{m_1}{s+2}$$

$$s(R+s+4) \Big|_{s=-2} = (R+4) = (2+2) \cdot 1 + m_1 \quad \left| \text{set } s = -2 \right.$$


$$R = -2 \Rightarrow -2+4 = 2 = 0 + m_1 \Rightarrow m_1 = 2$$
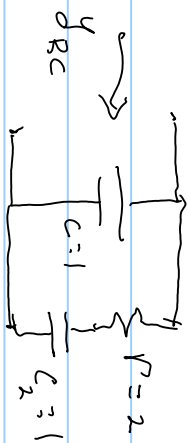
$$y_{RC} = a \left( \frac{a+4}{a+2} \right) = a \cdot 1 + \frac{2 \cdot a}{a+2}$$



and transfer

of matrix properties

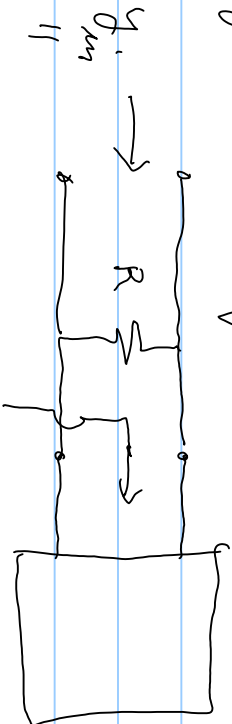

$$G + \frac{N(a^2)}{D(a^2)}$$

$$y_{RC} = \frac{a N(a^2)}{D(a^2)}$$

} assume PR  $\Rightarrow$   $z_{in}$  not poles in  $G > 0$

choose  $R=1 \Rightarrow G=1$

$$z = \frac{1}{z_{in}} = \frac{1}{G + \frac{a N(a^2)}{D(a^2)}}$$

$G=1$

$$\frac{D(a^2)}{D(a^2) + a N(a^2)} = \frac{D(a^2)}{P(a^2)}$$

Given  $a P(a^2) = E_1 P(a^2) + a P_2(a^2) \Rightarrow y = \frac{a P_2(a^2)}{P_1(a^2)}$

$$P(x) = 3x^5 + 2x^4 + 1x^3 + 3x^2 + 2x + 1 \quad ? \text{ is this Hurwitz}$$

$$= (2x^4 + 3x^2 + 1) + 3x^5 + 1x^3 + 2x$$

From  $q(x) = \frac{3x^5 + x^3 + 2x}{2x^4 + 3x^2 + 1}$  is this a local PR

$$\frac{2x^4 + 3x^2 + 1}{\frac{3}{2}x} \left[ \begin{array}{l} 3x^5 + x^3 + 2x \\ 3x^5 + \frac{3}{2}x^3 + \frac{3}{2}x \end{array} \right]$$

$$\frac{2-9x^3 + 4-3x}{2} \quad \frac{-4}{7}x$$


$$\frac{-7/2 x^3 + 1/2 x}{2x^4 + 3x^2 + 1}$$

$$\frac{2x^4 - 1/14 x^2}{2x^4 + 3x^2 + 1}$$

← gives a negative  
 ↳ in a 1st corner  
 Hurwitz's  
 ∴ P(x) is not Hurwitz

i.e., P(x) has a zero in the RHP

Case of 2 gyration

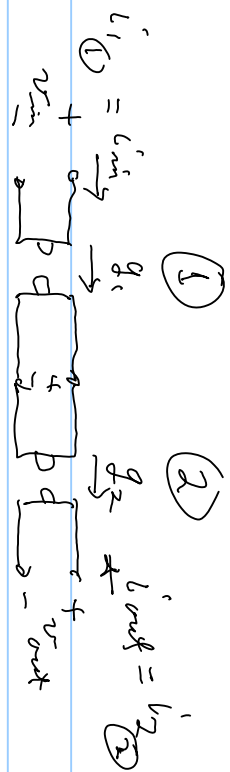

$$i_2 = -i_1 \quad (3)$$

$$v_{out} = -(-g_2) v_{out} \Rightarrow v_{out} = \frac{g_1 v_{in}}{g_2}$$

$$y_1 = \begin{bmatrix} 0 & -g_1 \\ g_1 & 0 \end{bmatrix} \quad y_2 = \begin{bmatrix} 0 & -g_2 \\ g_2 & 0 \end{bmatrix}$$


$$i_1 = -g_1 v_1 \quad (1), \quad v_2 = v_1 \quad (2)$$

$$= -g_1 v_1 \quad (1), \quad \frac{g_1}{g_2} = T_n$$

$$i_2 = g_2 v_2 \quad (2) \rightarrow = -g_1 v_1 \quad (1) = \frac{g_1 v_1 v_2}{g_2} \quad (2)$$

$$i_{in} = -\frac{g_1}{g_2} i_{out} = -T_n i_{out}$$

for a ideal transformer

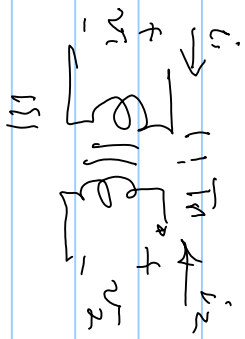


$$v_2 = T_n v_1$$

$$P_m = 0 = v_2 i_2 + v_1 i_1$$

$$= v_1 (T_n i_2 + i_1)$$

$$i_1 = -T_n i_2$$

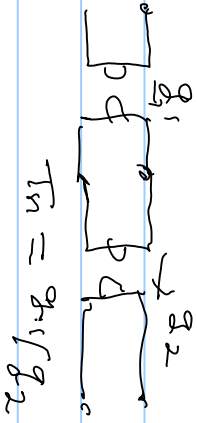

$$T_n = g_1 / g_2$$