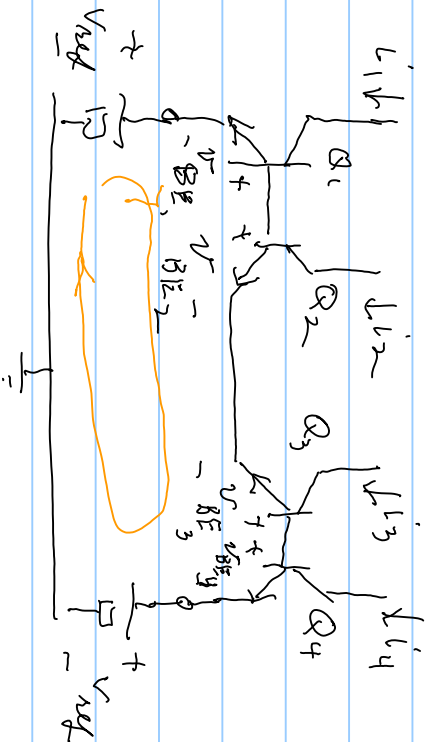


translinear circuits



$$I_c = A E \frac{V_{BE}}{V_T}$$

↑ material constant

$$\ln I_c = \frac{V_{BE}}{V_T}$$


Kirchhoff on voltages KVL

$$V_{BE1} - V_{BE2} + V_{BE3} + V_{BE4} = V_{BE1} + V_{BE3} - V_{BE2} - V_{BE4} \Rightarrow V_{BE1} + V_{BE3} = V_{BE2} + V_{BE4}$$

$$\ln I_1 + \ln I_3 = \ln I_2 + \ln I_4$$


$$\ln \frac{I_1 I_3}{I_2 I_4} = 0$$

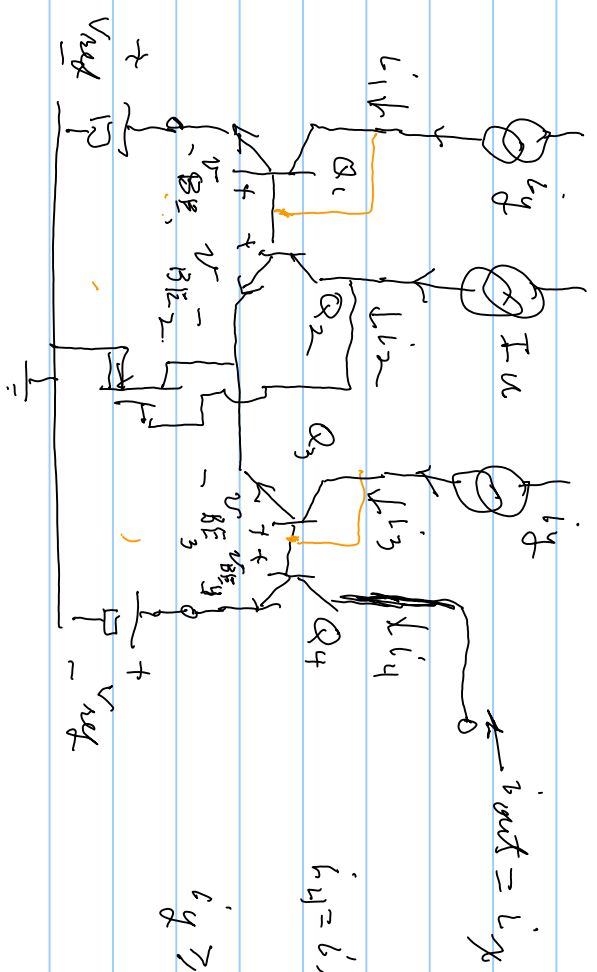Reason for diff:
$$\frac{v_{i3}}{A_2} = \frac{v_{o4}}{A_2} \Rightarrow v_o = v_{i3}/v_{i2}$$



$$v_{i4} = v_{i3} = \frac{v_{i1} v_{i3}}{v_{i2}} = \frac{v_{i4}}{I_{u2}}$$

$$v_{i4} > 0, I_{u2} > 0$$

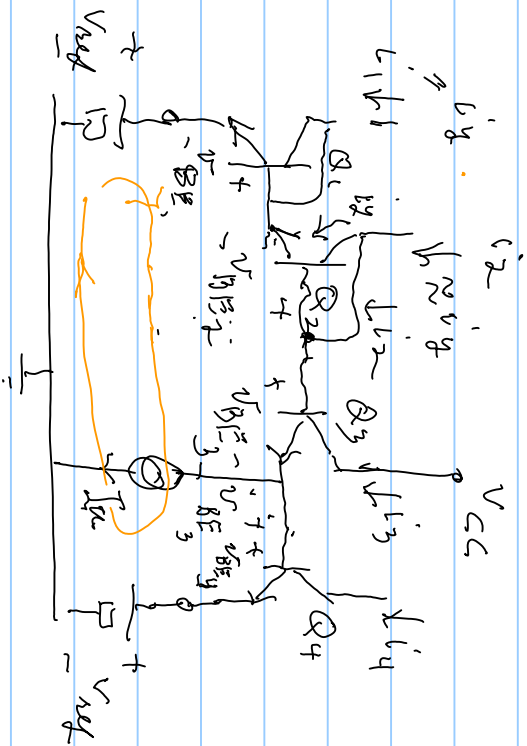


$$0 = -V_{sig} - V_{BE1} - V_{BE2} + V_{BE3} + V_{BE4} + V_{BE5} + V_{BE6}$$

$$V_{BE1} + 2V_{BE2} = V_{BE3} + V_{BE4}$$

$$\ln I_1, I_2 = \ln I_3, I_4$$

$$I_4 = I_1, I_2, I_3 \approx \left(\frac{I_2 (1 - \frac{1}{\alpha})}{\beta \mu} \right)^2$$

OP-amp via MOS Translinear loop

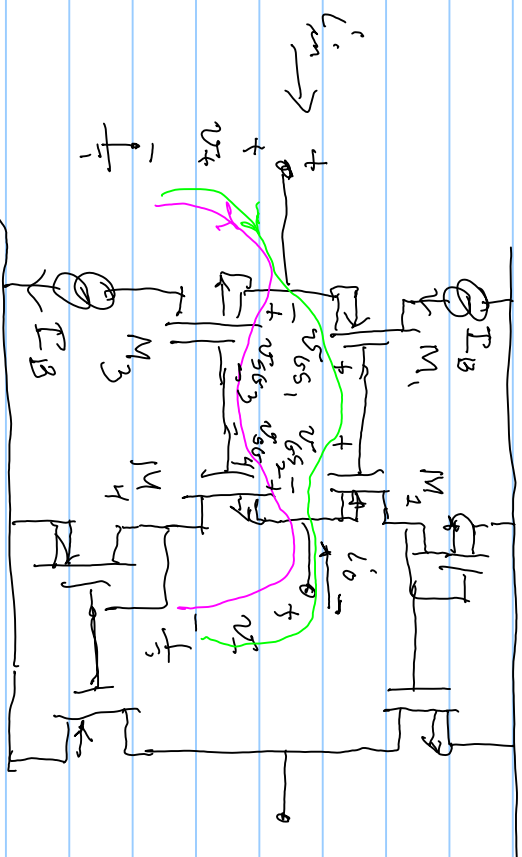

KVL gates/sources

$$0 = -V_{GS1} + V_{GS2} + V_{GS3} - V_{GS4} - V_{SG3}$$

$$V_{GS1} + V_{SG3} = V_{GS2} + V_{SG4}$$

or V_{D1} & cancel \Rightarrow

$$\sqrt{\frac{I_{B1}}{k_{M1}}} + \sqrt{\frac{I_{B3}}{k_{M3}}} = \sqrt{\frac{I_{D2}}{k_{M2}}} + \sqrt{\frac{I_{D4} + I_O}{k_{M4}}}$$

$$I_{B1} = k_{M1} (V_{GS1} - V_{TO_n})^2, \quad I_{S3} = k_{M3} (V_{SG3} - |V_{TO_p}|)^2$$

$$V_{SG3} = |V_{TO_p}| + \sqrt{\frac{I_{S3}}{k_{M3}}}$$

$$V_{SG4} = V_{TO_n} + \sqrt{\frac{I_{D4}}{k_{M4}}}$$

$$2\sqrt{I_B} = \sqrt{I_2} + \sqrt{I_2 + I_0}$$

green loop:

$$0 = -V_T - V_{GS1} + V_{GS2} + V_T \Rightarrow V_T - V_T = V_{GS2} - V_{GS1}$$

purple loop:

$$0 = -V_T + V_{SG3} - V_{SG4} + V_T \Rightarrow V_T - V_T = V_{SG3} - V_{SG4}$$

$$\text{add: } 2(V_T - V_T) = V_{GS2} + V_{SG3} - V_{GS1} - V_{SG4} \quad \text{but } V_{GS1} = V_{SG3} \text{ as } I_{B1} = I_{B2}$$

$$= V_{GS2} - V_{SG4} \quad \& \text{ in } \equiv 0$$

$$V_T = V_T + \frac{V_{SG4} - V_{GS2}}{2} \quad \text{if small signals then probably } V_T \gg (V_{SG4} - V_{GS2})/2 \text{ true if } |I_0| \ll I_2$$