

EE 610

12/08/16

Note Title

12/8/2016

connections use KCL & KVL

KCL:  $0 = \sum i_b$

T = tree or # of branches in a tree

$b = \text{branches or } \#$

KVL:  $0 = \sum v_b$

$l = \text{links or } \#$  in links

for separable part  $b = t + l$


$v_b = \sum v_t$ ,  $i_b = \sum i_l$





$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} \left| \begin{bmatrix} 0 & 0 & 1 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{bmatrix} \right. \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 & 0 & -1 & -1 & 0 & 0 & 0 \\ 0 & -1 & -1 & -1 & 0 & 1 & 0 \\ -1 & -1 & -1 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \end{bmatrix}$$
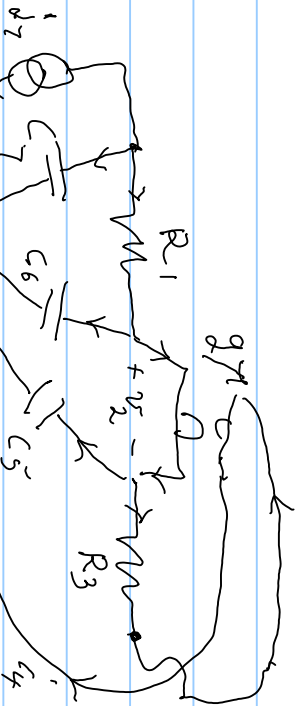
$$A(\omega) V(\omega) = B(\omega) I(\omega)$$


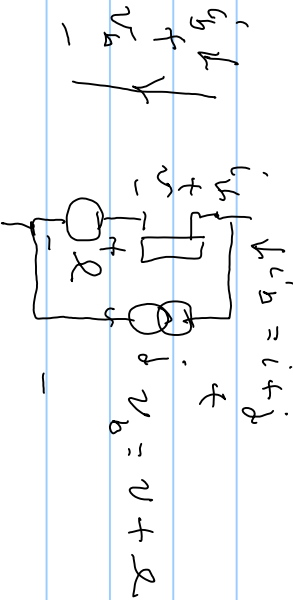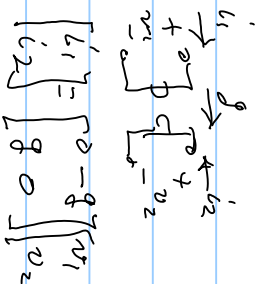
$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -g_m & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & g_m & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} V$$



$$= \begin{bmatrix} R_1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & R_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} I$$

$$e = 0, \quad j = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 1 \end{bmatrix}$$

$$v_b = e^T v_f = v, \quad i_b = g^T i = i + j$$

$$v_f = e^T v_f \quad i = g^T i_b - j$$

$$Av = Ae^T v_E = Bi = B \sigma^T i_a - B j_i$$

$$Ae^T v_E - B \sigma^T i_a = -B j_i$$

$$\underbrace{[Ae^T - B \sigma^T]}_{b \times b} \begin{bmatrix} v_E \\ i_a \end{bmatrix} = -B j_i \quad x = \begin{bmatrix} v_E \\ i_a \end{bmatrix}; \dim x = b \text{ \# of unknowns}$$

= semi-state (no T while state)  
no sig 3

semi-state  $EAx = Qx + Bu$   $u = j_T = \text{inputs}$   
eqs.

$(EA - Q)x = Bu \Rightarrow (EA - Q)^{-1}$  needed to solve

$$x = (EA - Q)^{-1} Bu = \begin{bmatrix} v_E \\ i_a \end{bmatrix}, \quad v_b = E^T v_E, \quad i_b = \sigma^T i_a$$

if  $y = \text{output}$   $= Cx$ ,  $C$  is an  $(\dim \text{output}) \times b$  matrix

Positive Real  $g(s)$  or  $z(s)$  if PR (=rational) can synthesize  
need use only 1 resistor

Sensitivity:  $S_{T(x)} = \frac{\partial T(x) / \partial x}{T(x) / x}$

can find  $\frac{\partial T(x)}{\partial x}$  via the adjoint

$$y^R = y^T$$

(turns gyration & amplifies around & keep others)