

Yu Peng Chen

114241092

ENEE 610 HW2

1.
(a)

$$\frac{dx_1}{dt} = 3x_1 - 5x_2 + 9u$$

$$\frac{dx_2}{dt} = 2 \tanh(3x_1 - 3x_2) + 12x_2$$

$$y = 2x_1 - 3x_2 + 8u$$

$$\dot{x} = Ax + Bu$$

$$y = Cx + Du$$

$$x_1 = x_2 = 0$$

Taylor series:

$$\begin{bmatrix} \frac{d(x_1-0)}{dt} \\ \frac{d(x_2-0)}{dt} \end{bmatrix} = \begin{bmatrix} \left. \frac{\partial f_1}{\partial x_1} \right|_{x_1=0, x_2=0} & \left. \frac{\partial f_1}{\partial x_2} \right|_{x_1=0, x_2=0} \\ \left. \frac{\partial f_2}{\partial x_1} \right|_{x_1=0, x_2=0} & \left. \frac{\partial f_2}{\partial x_2} \right|_{x_1=0, x_2=0} \end{bmatrix} \begin{bmatrix} x_1-0 \\ x_2-0 \end{bmatrix}$$

$$+ \begin{bmatrix} \left. \frac{\partial f_1}{\partial u} \right|_{x_1=0, x_2=0} \\ \left. \frac{\partial f_2}{\partial u} \right|_{x_1=0, x_2=0} \end{bmatrix} u$$

$$\begin{bmatrix} \frac{dx_1}{dt} \\ \frac{dx_2}{dt} \end{bmatrix} = \begin{bmatrix} 3 & -5 \\ 6 & 6 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 9 \\ 0 \end{bmatrix} u$$

$$y = \begin{bmatrix} 2 & -3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + 8u$$

b) Laplace Transform of the state equation

$$sX = AX + BU$$

$$Y = CX + DU$$

$$\Rightarrow (sI_n - A)X = BU, \quad X = (sI_n - A)^{-1}BU$$

$$Y = C(sI_n - A)^{-1}BU + DU = (C(sI_n - A)^{-1}B + D)U$$

Transfer function = $C(sI_n - A)^{-1}B + D$

$$A = \begin{bmatrix} 3 & -5 \\ 6 & 6 \end{bmatrix} \quad B = \begin{bmatrix} 9 \\ 0 \end{bmatrix} \quad C = [2 \quad -3] \quad D = 8$$

$$T(s) = \frac{1}{(s-3)(s-6)+30} \left\{ [2 \quad -3] \begin{bmatrix} s-6 & -5 \\ 6 & s-3 \end{bmatrix} \begin{bmatrix} 9 \\ 0 \end{bmatrix} \right\} + 8$$


$$= \frac{(2s-30)9 + 8(s^2-9s+48)}{s^2-9s+48} = \frac{8s^2 + (29-72)s + (384-309)}{s^2-9s+48}$$

(c) For the linearized system after expanded as Taylor series



$$\frac{dx_1}{dt} = 3x_1 - 5x_2 + g v_{in} \quad x_1 = v_1$$

$$\frac{dx_2}{dt} = 6x_1 + 6x_2 \quad x_2 = v_2$$


$$V_{out} = 2x_1 - 3x_2 + 8v_{in}$$

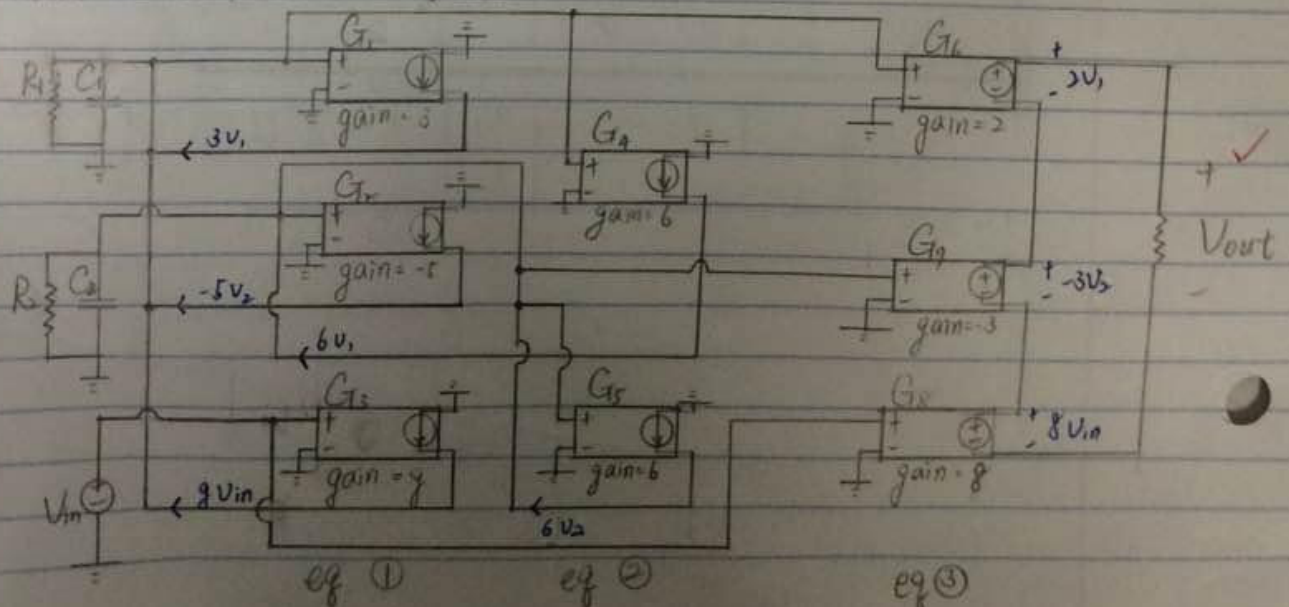

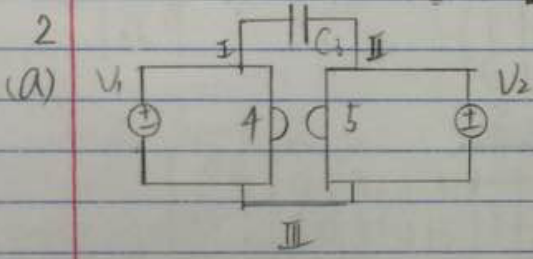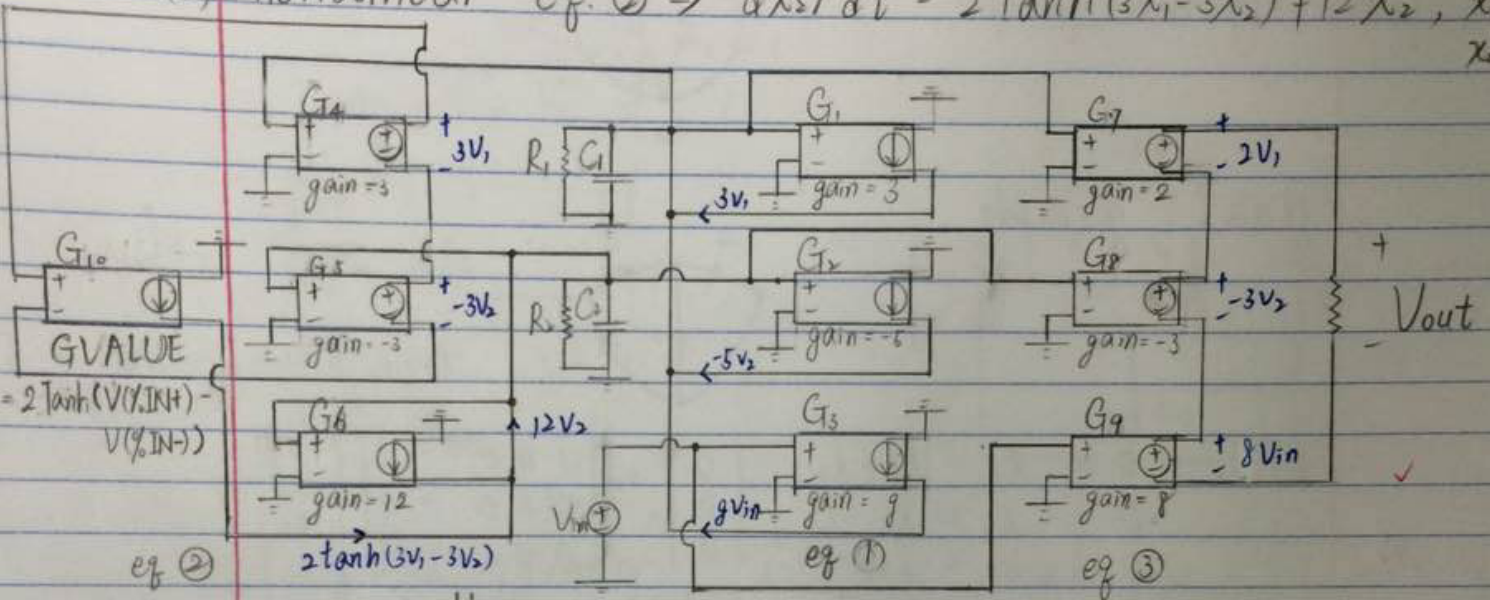(d) nonlinear eq. ② $\Rightarrow dx_2/dt = 2 \tanh(3x_1 - 3x_2) + 12x_2$, $x_1 = V_1$
 $x_2 = V_2$



directed graph

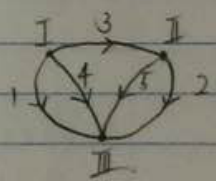

tree branches: 1, 2

KCL $0 = \lambda_1 + \lambda_3 + \lambda_4$
 $0 = \lambda_2 - \lambda_3 + \lambda_5$

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} \lambda_1 \\ \lambda_2 \\ \lambda_3 \\ \lambda_4 \\ \lambda_5 \end{bmatrix}$$

K

cut set matrix $e = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix}$


KVL: $0 = V_3 - V_1 + V_2$
 $0 = V_4 - V_1$
 $0 = V_5 - V_2$

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$


$-K^T$

tie set matrix $J = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix}$

(b) original graph

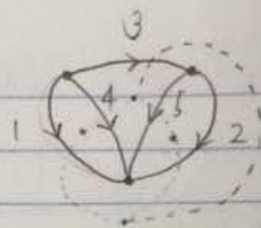

dual graph

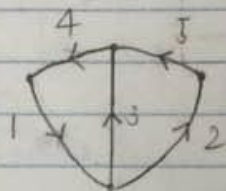

tree branches - 3, 4, 5

$$\text{KCL: } \begin{aligned} 0 &= \lambda_3 - \lambda_1 + \lambda_2 \\ 0 &= \lambda_4 - \lambda_1 \\ 0 &= \lambda_5 - \lambda_2 \end{aligned} \quad \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & -1 & 1 \\ 0 & 1 & 0 & -1 & 0 \\ 0 & 0 & 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} \lambda_3 \\ \lambda_4 \\ \lambda_5 \\ \lambda_1 \\ \lambda_2 \end{bmatrix}$$

$$\text{cut set matrix } e' = \begin{bmatrix} 1 & 0 & 0 & -1 & 1 \\ 0 & 1 & 0 & -1 & 0 \\ 0 & 0 & 1 & 0 & -1 \end{bmatrix}$$


$$\text{KVL: } \begin{aligned} 0 &= V_1 + V_3 + V_4 \\ 0 &= V_2 - V_3 + V_5 \end{aligned} \quad \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 1 & 0 & 1 & 0 \\ -1 & 0 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_3 \\ V_4 \\ V_5 \\ V_1 \\ V_2 \end{bmatrix}$$

$$\text{tie set matrix } J' = \begin{bmatrix} 1 & 1 & 0 & 1 & 0 \\ -1 & 0 & -1 & 0 & 1 \end{bmatrix}$$

compare e, J with e', J' ✓



$$e = [I_2 \mid K] \quad e' = [I_3 \mid -K^T]$$
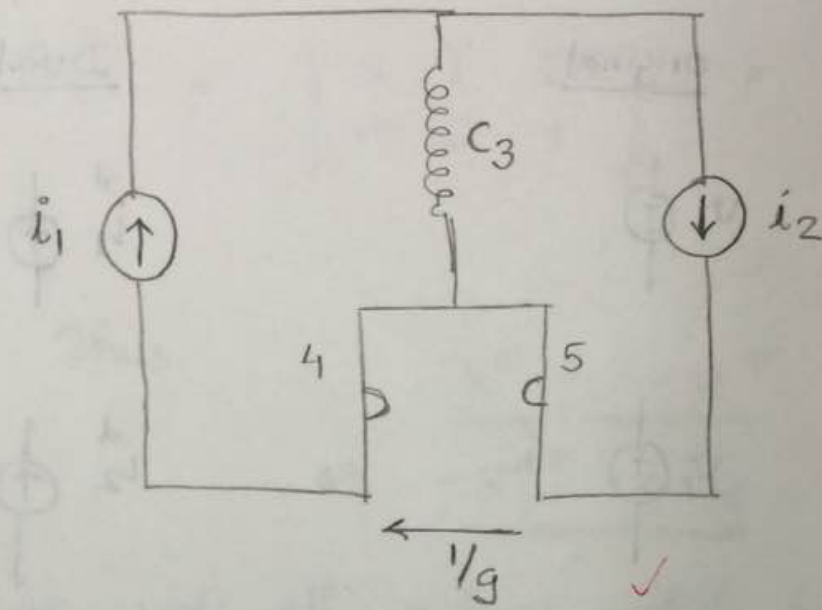
$$J = [-K^T \mid I_3] \quad J' = [K \mid I_2]$$



(d)

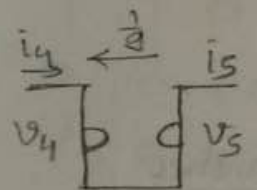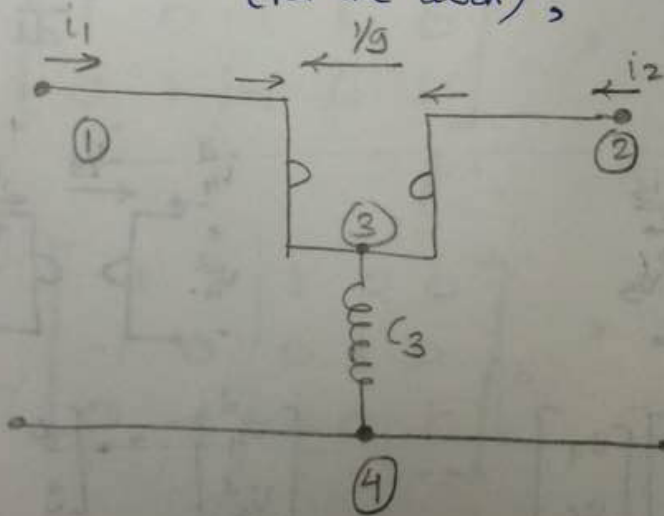Forming a two-port network,
(for the dual),



$$\begin{bmatrix} i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 0 & 1/g \\ 1/g & 0 \end{bmatrix} \begin{bmatrix} v_4 \\ v_5 \end{bmatrix}$$

$$i_1 = +\frac{1}{g}(v_2 - v_3) = +\frac{1}{g}v_2 - \frac{1}{g}v_3$$

$$i_2 = -\frac{1}{g}(v_1 - v_3) = -\frac{1}{g}v_1 + \frac{1}{g}v_3$$

$$\begin{aligned} i_3 &= -\frac{1}{g}(v_2 - v_3) + \frac{1}{g}(v_1 - v_3) - \frac{1}{sC_3}(v_4 - v_3) \\ &= +\frac{1}{g}v_1 - \frac{1}{g}v_2 + \frac{1}{sC_3}v_3 - \frac{1}{sC_3}v_4 \end{aligned}$$

$$i_4 = -\frac{1}{sC_3} (v_3 - v_4) = -\frac{1}{sC_3} v_3 + \frac{1}{sC_3} v_4$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{g} & -\frac{1}{g} & 0 \\ -\frac{1}{g} & 0 & \frac{1}{g} & 0 \\ -\frac{1}{g} & -\frac{1}{g} & \frac{1}{sC_3} & -\frac{1}{sC_3} \\ 0 & 0 & -\frac{1}{sC_3} & \frac{1}{sC_3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} \quad \left. \vphantom{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}} \right\} \begin{array}{l} \text{Indefinite} \\ \text{Admittance} \\ \text{matrix} \end{array}$$

Now setting

$$v_4 = 0$$

$$i_4 = i_1 + i_2 + i_3$$

↓ (Not asked for in the question)

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{g} & -\frac{1}{g} \\ -\frac{1}{g} & 0 & \frac{1}{g} \\ \frac{1}{g} & -\frac{1}{g} & \frac{1}{sC_3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

To eliminate i_3 , set $i_3 = 0$

$$i_3 = \frac{v_1}{g} - \frac{v_2}{g} + \frac{v_3}{sC_3} = 0$$

$$\Rightarrow v_3 = \frac{sC_3}{g} (v_1 - v_2)$$

$$\therefore \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -\frac{sC_3}{g^2} & \frac{sC_3}{g^2} + \frac{1}{g} \\ \frac{sC_3}{g^2} - \frac{1}{g} & -\frac{sC_3}{g^2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$