

ASSIGNMENT-4

SIDDHARTH TYAGI

ENEE-610: NETWORK THEORY

11

(a) Condition for Positive-Real:-

- No poles and zeroes in RHP:-

$$\therefore f_a(s) = \frac{s-a}{s+b} \Rightarrow \boxed{a \leq 0; b \geq 0.}$$

In general; if $s = \sigma + j\omega$; $f_a(s)$ is PR means that

$$\operatorname{Re}[f_a(s)] > 0 \text{ when } \sigma > 0.$$

$$\therefore f_a(\sigma + j\omega) = \frac{(\sigma - a) + j\omega}{(\sigma + b) + j\omega} = \frac{\{(\sigma - a) + j\omega\} \{(\sigma + b) - j\omega\}}{(\sigma + b)^2 + \omega^2}$$

$$\Rightarrow \operatorname{Re}[f_a(s)] = \frac{\{\sigma^2 + \omega^2 + \sigma(b - a) + ab\}}{(\sigma + b)^2 + \omega^2}$$

clearly; when $a \leq 0$ $b \geq 0$ is $\boxed{b \geq a}$; $\boxed{ab \leq 0.}$

\Rightarrow all terms of $\operatorname{Re}[f_a(s)] \geq 0.$

Only Condition:

$$\boxed{\begin{matrix} a \leq 0 \\ b \geq 0 \end{matrix}}$$

- Conditions for Bounded-Real:-

- $f_a^*(s) = f_a(s^*)$ is clearly true

- No singularities in RHP:-

$$\therefore \boxed{b \geq 0}$$

- $1 - f_a^*(s) f_a(s) > 0$ for all $\sigma > 0$ $\{s = \sigma + j\omega\}$.

$$\frac{(\cancel{\sigma-a})^* (\sigma-a+j\omega)^* (\sigma-a+j\omega)}{(\sigma+b+j\omega)^* (\sigma+b+j\omega)} = \frac{(\sigma-a)^2 + \omega^2}{(\sigma+b)^2 + \omega^2} < 1.$$

$$\therefore (\sigma-a)^2 < (\sigma+b)^2$$

$$\therefore \boxed{\{2\sigma + (b-a)\} \{b+a\} > 0} \quad \forall \sigma > 0$$

clearly; $\sigma > 0$.

$$\therefore \boxed{b+a > 0} \quad \checkmark$$

Positive-Real:-

$$f_b(s) = \left(\frac{s^2 + s + a}{s^2 + s + b} \right)$$

- Since, a, b are real $\Rightarrow Y^*(s) = Y(s)$

- No poles and zeroes in RHP:-

$$\left. \begin{aligned} Z_{1,2} &= -1 \pm \sqrt{1-4a} \\ p_{1,2} &= -1 \pm \sqrt{1-4b} \end{aligned} \right\} \begin{aligned} &\text{clearly; if } \underline{a > 0} \\ &\Rightarrow \sqrt{1-4a} \text{ can either be real} \\ &\quad \text{or imaginary} \end{aligned}$$

if imaginary $\Rightarrow \underline{\text{Re}(Z_{1,2}) = -1}$

if real $\Rightarrow \text{Re}(Z_{1,2}) = -1 + \sqrt{1-4a} \geq 0$
is ensured.

$\Rightarrow \boxed{a > 0 \text{ and } b > 0}$ will ensure no pole-zero in RHP.

- $\text{Re} \{ f_b(j\omega) \} > 0 ; \forall \omega$

$$f_b(j\omega) = \frac{(a - \omega^2) + j\omega}{(b - \omega^2) + j\omega} = \frac{\{(a - \omega^2) + j\omega\} \{(b - \omega^2) - j\omega\}}{(b - \omega^2)^2 + \omega^2}$$

$$\begin{aligned} \therefore \text{Re} \{ f_b(j\omega) \} &= \frac{(a - \omega^2)(b - \omega^2) + \omega^2}{(b - \omega^2)^2 + \omega^2} \\ &= \omega^4 + \{1 - 2a - 2b\}\omega^2 + ab > 0 \end{aligned}$$

~~$\Rightarrow (1 - 2a - 2b)^2 - 4ab > 0$ $\therefore 4a^2 + 4b^2 - 4a - 4b + 1 > 0$~~

~~$1 + 4a^2 + 4b^2 - 2a - 2b + 4ab - 4ab > 0$~~

This means:-

$$\boxed{(1-a-b)^2 - 4ab < 0} \text{ must be true.}$$

Bounded-Real:

- Since a, b are real $f_b^*(s) = f_b(s^*)$.

- For no singularities: in RHP

$$\circ \quad \boxed{b > 0}$$

- ~~$f_b^*(j\omega)$~~ $1 - f_b^*(j\omega) f_b(j\omega) \geq 0$.

$$\text{clearly: } f_b^*(j\omega) f_b(j\omega) = \frac{(a-\omega^2) + j\omega}{(b-\omega^2) + j\omega} \cdot \frac{(a-\omega^2) - j\omega}{(b-\omega^2) - j\omega}$$

$$= \frac{(a-\omega^2)^2 + \omega^2}{(b-\omega^2)^2 + \omega^2} = \frac{\omega^4 + (1-2a)\omega^2 + a^2}{\omega^4 + (1-2b)\omega^2 + b^2}$$

$$\therefore 1 - f_b^*(j\omega) f_b(j\omega) \geq 0$$

$$\Rightarrow (1-2b)\omega^2 + b^2 - (1-2a)\omega^2 - a^2 \geq 0$$

$$\therefore \Rightarrow (b+a+2\omega^2)(b-a) \geq 0.$$

clearly: $\boxed{b-a \geq 0}$ is a possible condition.

$$f_c(s) = \frac{(s^2 + as + 1)}{(s^2 + bs + 1)}$$

- No poles in RHP :-
zeros

$$-a \pm \sqrt{a^2 - 4} \geq 0$$

$$-b \pm \sqrt{b^2 - 4} \geq 0$$

clearly; if $a \geq 0$.

$$\Rightarrow \text{if } a^2 - 4 > 0 \Rightarrow -a + \sqrt{a^2 - 4} \leq 0$$

$$< 0 \Rightarrow -a \leq 0$$

\Rightarrow always Real (pole) ≤ 0

$$\therefore \boxed{a \geq 0; b \geq 0}$$

- $\text{Re}[f_c(j\omega)] > 0$;

$$f_c(j\omega) = \frac{(1 - \omega^2) + j a \omega}{(1 - \omega^2) + j b \omega} = \frac{\{(1 - \omega^2) + j a \omega\} \{(1 - \omega^2) - j b \omega\}}{(1 - \omega^2)^2 + (b \omega)^2}$$

$$\therefore \text{Re}[f_c(j\omega)] = (1 - \omega^2)^2 + ab \omega^2$$

clearly; $a \geq 0; b \geq 0$
ensures this.

\Rightarrow Only condition: $\boxed{a \geq 0; b \geq 0}$ for Positive-Real.



For Bounded-Real:-

again $b \geq 0$.

$$\text{also; } 1 - f_c^*(j\omega) f_c(j\omega)$$

$$= 1 - \left\{ \frac{(1-\omega^2) + ja\omega}{(1-\omega^2) + jb\omega} \right\} \cdot \left\{ \frac{(1-\omega^2) - ja\omega}{(1-\omega^2) - jb\omega} \right\}$$

$$= 1 - \frac{(1-\omega^2) + a^2\omega^2}{(1-\omega^2)^2 + b^2\omega^2}$$

$$= \frac{(b^2 - a^2)\omega^2}{(1-\omega^2)^2 + b^2\omega^2} > 0$$

$$\therefore \boxed{b^2 - a^2 > 0}$$

$$\text{or } \boxed{|b| > |a|}$$

Positive-Real:-

$$f_d(s) = \frac{as}{(s^2+b)^b}$$

clearly, for PR \Rightarrow relative degree ~~betⁿ~~ ~~is~~ numerator and denominator must be max. 1. $0 \leq b \leq 1$

$$\Rightarrow \boxed{b=0 \text{ or } 1}$$

(a) When $b=0$

$$\Rightarrow f_d(s) = as \text{ which will be } \boxed{\text{+ve real if } a > 0}$$

(b) When $b=1$.

$$f_d(s) = \frac{as}{(s^2+1)} ; \text{ ~~is~~ } s = \sigma + j\omega$$

$$= a \frac{(\sigma + j\omega)}{(\sigma^2 - \omega^2 + 1) + j2\sigma\omega}$$

$$= a \frac{(\sigma + j\omega)(\sigma^2 - \omega^2 + 1 - j2\sigma\omega)}{(\sigma^2 - \omega^2 + 1)^2 + 4\sigma^2\omega^2}$$

$$\Rightarrow \text{Re}[f_d(s)] = a[\sigma^3 + \sigma + \sigma\omega^2] \geq 0 \Rightarrow \boxed{a \geq 0}$$

\therefore Only condition of PR on a is $\boxed{a > 0}$.

Bounded-Real:-

$$f_d(s) = \frac{as}{(s^2+1)^b}$$

~~again if $b > 1 \Rightarrow$ the initial-state response will blow and~~

when $b=1$:-

$$f_d(j\omega) = \frac{a \times j\omega}{1 - \omega^2}$$

$$1 - f_d(j\omega) f_d^*(j\omega)$$

$$= 1 - \frac{a^2 \omega^2}{(1 - \omega^2)^2} \geq 0$$

$$\therefore (1 - \omega^2)^2 - a^2 \omega^2 \geq 0$$

$$\therefore \boxed{a^2 \omega^2 \leq (1 - \omega^2)^2} \text{ must be satisfied for B.R.}$$

$$\text{let } g(\omega) = (1 - \omega^2)^2 - a^2 \omega^2$$

$$\text{let } x = \omega^2 \geq 0 \Rightarrow g(x) = (1 - x)^2 - a^2 x = x^2 - (a^2 + 2)x + 1 \geq 0$$

$$\text{At } x = \frac{a^2 + 2}{2} \text{ } g(x) \text{ minimum. } g(x)_{\min} = \left(\frac{a^2 + 2}{2}\right)^2 - (a^2 + 2) \cdot \frac{a^2 + 2}{2} + 1$$

$$= 1 - \frac{(a^2 + 2)^2}{4} \geq 0$$

$$\Rightarrow (a^2 + 2)^2 \leq 4$$

$$\Rightarrow -4 \leq a^2 \leq 0$$

$$\Rightarrow a = 0$$

even:

$$(d) f_d = \frac{as}{(s^2+1)^b} = \frac{N(s)}{D(s)}$$

PR: ① $\operatorname{Re}[f_d(j\omega)] \geq 0$ for all $0 \leq \omega < \infty$
 ② The degrees of $N(s)$ and $D(s)$ differ at most by 1
 (from the textbook)

$\operatorname{Re}[f_d(j\omega)] = 0$, from ② \Rightarrow if $a \neq 0$, $0 \leq b < 1$
 $a = 0$, b arbitrary for PR

$$\text{BR: } |f_d(s)|^2 = \left(\frac{a\omega}{(1-\omega^2)^b}\right)^2 = \frac{a^2\omega^2}{(1-\omega^2)^{2b}} \leq 1 \quad \checkmark$$

$$\Rightarrow (1-\omega^2)^{2b} - a^2\omega^2 \geq 0 \Rightarrow \begin{aligned} -a^2\omega^2 &\geq 0 \\ -a^2 &\geq 0 \Rightarrow \underline{a=0 \text{ for BR}} \end{aligned}$$

$$2 \quad f(s) = \frac{3s(s^2+5)(s^2+8)}{(s^2+1)(s^2+6)}, \quad f(j\omega) = j \frac{3\omega(5-\omega^2)(8-\omega^2)}{(1-\omega^2)(6-\omega^2)}$$

$$\Rightarrow \operatorname{Re}[f(j\omega)] = 0 \Rightarrow f(s) + f(-s) = 0 \text{ on } s = j\omega$$

\Rightarrow lossless positive-real

2nd Foster

$$y(s) = \frac{3s(s^2+5)(s^2+8)}{(s^2+1)(s^2+6)} = k_{\infty}s + \frac{k_0}{s} + \sum \frac{2k_2s}{s^2+\omega_i^2}$$

$$= k_{\infty}s + \frac{2k_2s}{s^2+1} + \frac{2k_4s}{s^2+6} = 3s + \frac{2k_2s}{s^2+1} + \frac{2k_4s}{s^2+6} \quad k_{\infty}=3$$

$$\left(\frac{s^2+1}{s}\right) y(s) = \frac{3(s^2+5)(s^2+8)}{s^2+6} = (s^2+1)k_{\infty} + 2k_2 + \frac{2k_4}{s^2+6}(s^2+1)$$

$$s^2 = -1 \Rightarrow \frac{3 \times 4 \times 7}{5} = 2k_2, \quad k_2 = \frac{42}{5}$$


$$\left(\frac{s^2+6}{s}\right) y(s) \Big|_{s^2=-6} = \frac{3(s^2+5)(s^2+8)}{s^2+1} \Big|_{s^2=-6} = \frac{3 \times 2}{-5} = (s^2+6)k_{\infty} + \frac{2k_2(s^2+6)}{s^2+1} + 2k_4 \Big|_{s^2=-6}$$

$$= 0 + 0 + 2k_4$$

$$\Rightarrow k_4 = \frac{3}{5}$$

$$y(s) = 3s + \frac{\frac{84}{5}s}{s^2+1} + \frac{\frac{6}{5}s}{s^2+6}$$
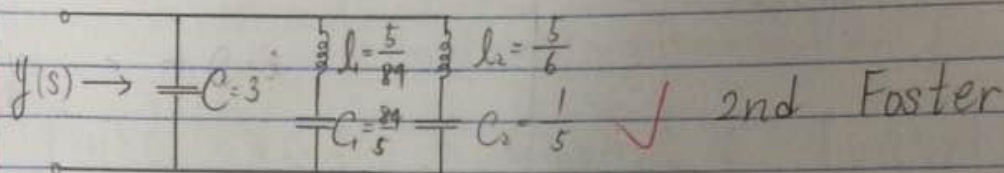
$$\bar{y}_1 = \frac{1}{y_1} = \frac{s^2+1}{\frac{84}{5}s} = \frac{5}{84}s + \frac{1}{\frac{84}{5}s}, \quad \bar{y}_2 = \frac{1}{y_2} = \frac{s^2+6}{\frac{6}{5}s} = \frac{5}{6}s + \frac{1}{\frac{6}{5}s}$$



$$\bar{z}(s) = \frac{1}{y(s)} = \frac{(s^2+1)(s^2+6)}{3s(s^2+5)(s^2+8)} = \frac{k_0}{s} + \frac{2k_2s}{s^2+5} + \frac{2k_4s}{s^2+8}$$


$$\frac{s^2+5}{s} \cdot \bar{z}(s) \Big|_{s^2=-5} = \frac{(s^2+1)(s^2+6)}{3s^2(s^2+8)} \Big|_{s^2=-5} = \frac{-4 \times 1}{3 \times (-5) \times 3} = 0 + 2k_2 + 0 \Rightarrow k_2 = \frac{2}{45}$$

$$\frac{s^2+8}{s} \cdot \bar{z}(s) \Big|_{s^2=-8} = \frac{(-7)(-2)}{3 \times (-8) \times (-3)} = 0 + 0 + 2k_4 \Rightarrow k_4 = \frac{7}{72}$$

$$3 \left[k_0 (s^2+5)(s^2+8) + \frac{4}{45} (s^4+8s^2) + \frac{14}{72} (s^4+5s^2) \right] = (s^2+1)(s^2+6)$$

$$120k_0 = 6 \Rightarrow k_0 = \frac{1}{20}$$
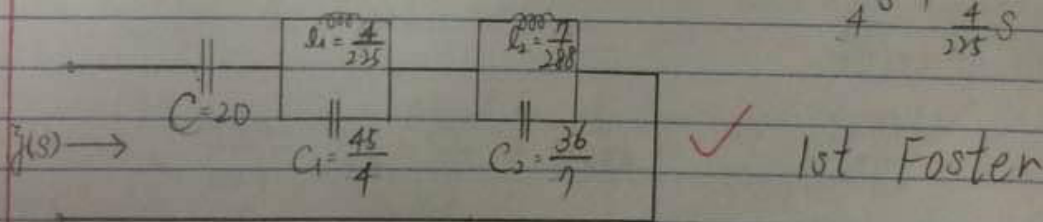
$$\bar{z}(s) = \frac{1}{20s} + \frac{\frac{4}{45}s}{s^2+5} + \frac{\frac{14}{72}s}{s^2+8} = \frac{1}{20s} + \frac{1}{\frac{45s}{4} + \frac{1}{225}s} + \frac{1}{\frac{36}{7}s + \frac{1}{288}s}$$



1st Foster: components are first connected in parallel then in series, using the input impedance to construct it.

2nd Foster: components are first connected in series then in parallel, using the input admittance to construct it.

1st Cauer

$$y(s) = \frac{3s^5 + 39s^3 + 120s}{s^4 + 9s^2 + 6} \quad \text{remove poles at } \infty$$

$$\begin{array}{r}
 3s \\
 s^4 + 9s^2 + 6 \overline{) 3s^5 + 39s^3 + 120s} \\
 \underline{3s^5 + 27s^3} \\
 18s^3 + 102s \\
 \underline{18s^3 + 18s} \\
 84s \\
 \underline{84s} \\
 0
 \end{array}$$

$$\Rightarrow y(s) = 3s + \frac{1}{\frac{1}{18}s + \frac{27}{2}s + \frac{1}{\frac{4}{63}s + \frac{1}{\frac{1}{2}s + \frac{1}{63}}}}}$$

$\frac{1}{18}$ $\frac{1}{2}$ $\frac{4}{63}$ $\frac{1}{2}$ $\frac{1}{63}$

$C_1 = 3$ $C_2 = \frac{27}{2}$ $C_3 = \frac{7}{2}$ 1st Cauer

2nd Cauer remove poles at 0

$$z(s) = \frac{6 + 9s^2 + s^4}{120s + 39s^3 + 3s^5}$$

$$\frac{1}{20s} \div (6 + 7s^2 + s^4)$$

$$\frac{6 + \frac{34}{20}s^2 + \frac{3}{20}s^4}{101} \quad \frac{2400}{101}$$

$$\frac{101s^2 + \frac{17}{20}s^4}{120s + 39s^3 + 3s^5}$$

$$\frac{10201}{37980s}$$

$$\frac{1899s^3 + 3s^5}{101s^2 + \frac{17}{20}s^4}$$

$$\frac{101s^2 + \frac{10 \times 101}{633 \times 20}s^4}{\frac{1202067}{2828s}}$$

$$\frac{28s^4}{633s^4} \quad \frac{1899s^3 + 3s^5}{101s^3}$$

$$\frac{28}{101s^3} \quad \frac{28}{1899s^3}$$

$$\frac{28}{633s^4} \quad \frac{28}{633s^4}$$

$$\Rightarrow \bar{y}(s) = \frac{1}{20s} + \frac{2400}{101s} + \frac{10201}{37980s} + \frac{1202067}{2828s} + \frac{28}{1899s^3}$$

$$C_1 = 20 \quad C_2 = \frac{37980}{10201} \quad C_3 = \frac{1899}{28}$$

$$L_1 = \frac{101}{2400} \quad L_2 = \frac{2828}{1202067}$$

✓ 2nd Cover


1st Cover the L's are horizontal while the C's are vertical. We choose the reaction function (could be y(s) or z(s)) that has the numerator with larger degree

2nd Cover the C's are horizontal while the L's are vertical. We choose the reaction function that has the numerator with the smallest degree, (e.g. constant)

$f(s)$ is an impedance \Rightarrow dual circuit


$$\bar{z}(s) = \frac{3s(s^2+5)(s^2+8)}{(s^2+1)(s^2+6)} = 3s + \frac{1}{\frac{5}{84}s + \frac{1}{84}} + \frac{1}{\frac{5}{6}s + \frac{1}{6}}$$

1st Foster

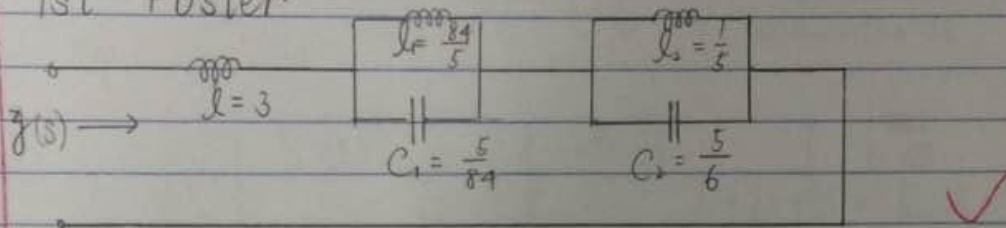

$$y(s) = \frac{(s^2+1)(s^2+6)}{3s(s^2+5)(s^2+8)} = \frac{1}{20s} + \frac{1}{\frac{45}{4}s + \frac{1}{4}} + \frac{1}{\frac{36}{7}s + \frac{1}{7}}$$

2nd Foster

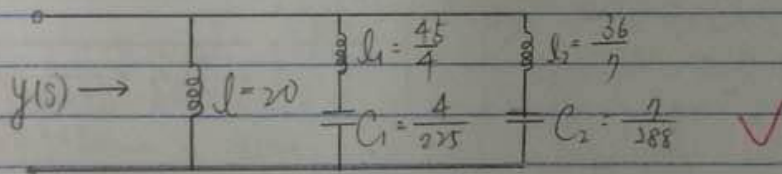


1st Foster of $f(s)$ as an impedance is the dual of
2nd Foster of $f(s)$ as an admittance.

2nd Foster of $f(s)$ as a $\bar{z}(s)$ is the dual of
1st Foster of $f(s)$ as a $y(s)$

As for the Cauer with $f(s)$ as an impedance


1st Cauer
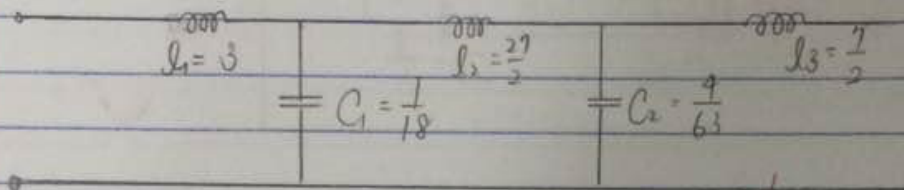
$$y(s) = \frac{s^4 + 9s^2 + 6}{3s^5 + 39s^3 + 120s}, \quad \bar{z}(s) = \frac{3s^5 + 39s^3 + 120s}{s^4 + 9s^2 + 6} = 3s + \frac{1}{\frac{1}{18}s + \frac{27}{2}s + \frac{\frac{4}{6}s + \frac{1}{2}s}{1}}$$



2nd Cauer
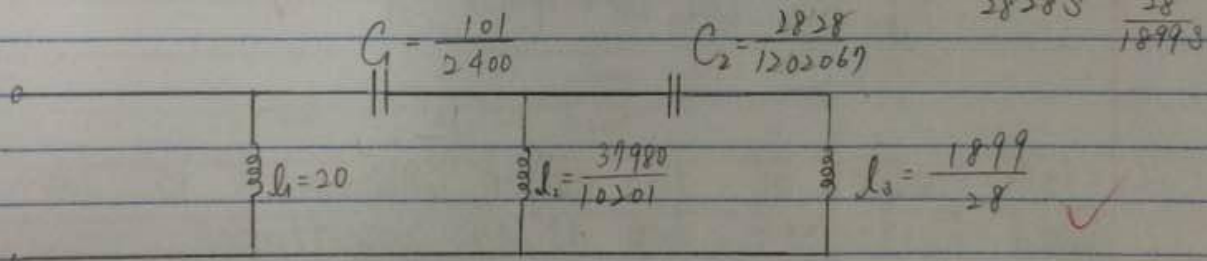
$$y(s) = \frac{6 + 9s^2 + s^4}{3s^5 + 39s^3 + 120s} = \frac{1}{20s} + \frac{1}{\frac{2400}{101s} + \frac{1}{\frac{10201}{37980s} + \frac{1}{\frac{1202069}{2828s} + \frac{1}{\frac{28}{18973}}}}}$$



1st Cauer with $f(s)$ as a $\bar{z}(s)$ is the dual of
1st Cauer with $f(s)$ as a $y(s)$


2nd Cauer with $f(s)$ as a $\bar{z}(s)$ is the dual of
2nd Cauer with $f(s)$ as a $y(s)$

3 admittance synthesis $y_{LC}(s) = \frac{3s(s^2+5)(s+8)}{(s^2+1)(s^2+6)}$

$$= 3s + \frac{\frac{84}{5}s}{s^2+1} + \frac{\frac{6}{5}s}{s^2+6}$$

LC \rightarrow RC

2nd Foster:

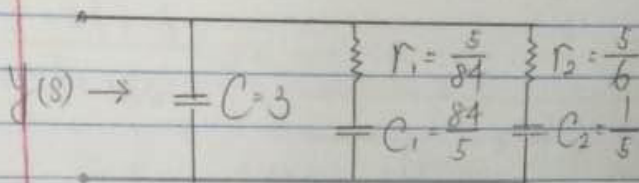


$$y_{RC}(s) = k_{\infty}s + k_0 + \sum \frac{k_i s}{s + w_i^2}$$

$$= 3s + \frac{\frac{84}{5}s}{s^2+1} + \frac{\frac{6}{5}s}{s^2+6}$$

$$= 3s + \frac{1}{\frac{5}{84} + \frac{1}{\frac{84}{5}s}} + \frac{1}{\frac{5}{6} + \frac{1}{\frac{1}{5}s}}$$

1st Foster

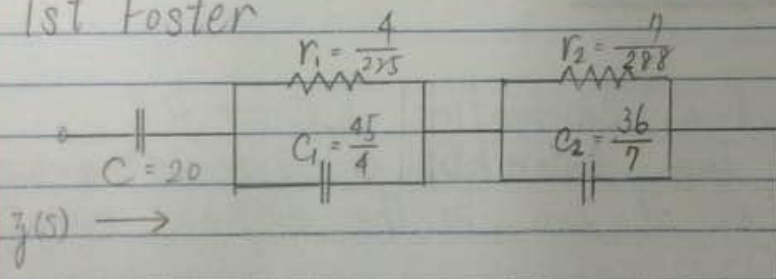


$$y_{RC}(s) = \frac{1}{20s} + \frac{\frac{4}{45}}{s+5} + \frac{\frac{7}{36}}{s+8} = \frac{1}{s} + \frac{1}{4 \cdot \frac{4}{225}} + \frac{1}{7 \cdot \frac{7}{288}}$$

$$\Rightarrow \underline{y_{RC}(s) = \frac{3s(s+5)(s+8)}{(s+1)(s+6)}} \quad \checkmark$$


$$= \frac{(s+1)(s+6)}{3s(s+5)(s+8)}$$

1st Cauer

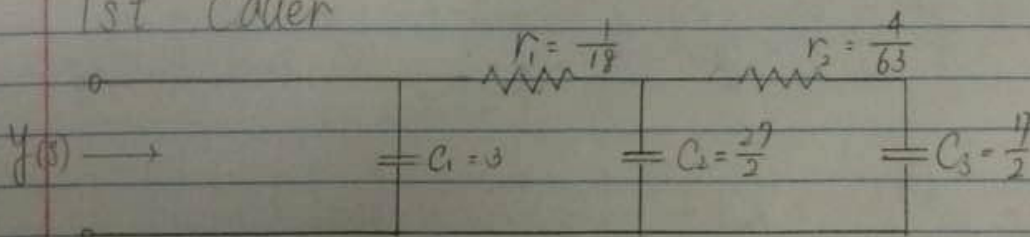

$$y_{RC}(s) = 3s + \frac{1}{\frac{1}{18} + \frac{1}{\frac{27}{2}s}} + \frac{1}{\frac{4}{63} + \frac{1}{\frac{17}{2}s}} = \underline{\underline{\frac{3s^3 + 39s^2 + 130s}{s^2 + 98s + 6}}} \quad \checkmark$$

2nd Cauer

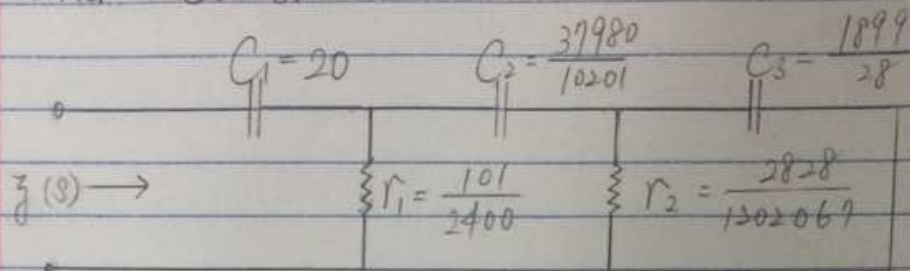

$$z_{RC}(s) = \frac{1}{20s} + \frac{1}{\frac{2400}{101} + \frac{1}{\frac{10201}{37980s} + \frac{1}{\frac{1202067}{2828} + \frac{1}{\frac{1899}{28}}}}} = \frac{6 + 78s + s^2}{120s + 39s^2 + 3s^3}$$

$$\Rightarrow \underline{y_{RC}(s) = \frac{3s^3 + 39s^2 + 120s}{s^2 + 78s + 6}} \quad \checkmark$$

Note that when converting LC \rightarrow RC we take off the variable s associated with the numerical values of L 's in the original equation

4.

$$S(s) = \frac{3s^2 - 6s + 3}{3s^2 + 6s + 3} = \frac{s^2 - 2s + 1}{s^2 + 2s + 1}$$

$$Y(s) = (1+s)^{-1} (1-s) = \frac{s^2 + 2s + 1}{2s^2 + 2} \cdot \frac{4s}{s^2 + 2s + 1} = \frac{2s}{s^2 + 1}$$

$$= \frac{1}{\frac{s}{2} + \frac{1}{2s}} \quad y(s) \rightarrow \begin{array}{c} \frac{1}{2} \\ \text{---} \\ l_1 = \frac{1}{2} \\ \text{---} \\ C_1 = 2 \end{array} \quad \checkmark \text{ 2nd Foster}$$

$$\bar{z}(s) = \frac{s^2 + 1}{2s} = k_{\infty}s + \frac{k_0}{s} \quad s \cdot \bar{z}(s) \Big|_{s=0} = \frac{1}{2} = 0 + k_0, \quad k_0 = \frac{1}{2}$$

$$\frac{s^2 + 1}{2s} = k_{\infty}s + \frac{1}{2s} \quad \begin{array}{c} \frac{1}{2} \\ \text{---} \\ l_1 = \frac{1}{2} \\ \text{---} \\ C_1 = 2 \end{array} \quad \checkmark$$

$$\Rightarrow k_{\infty} = \frac{1}{2}, \quad \bar{z}(s) = \frac{1}{2}s + \frac{1}{2s} \quad \bar{z}(s) \rightarrow \text{1st Foster}$$

In this case, the 1st Foster and the 2nd Foster are the same circuit

1st Cauer

$$Z(s) = \frac{s^2 + 1}{2s} = \frac{1}{2}s + \frac{1}{2s + 0}$$

$$\frac{\frac{1}{2}s}{2s} \left| \frac{1}{s^2 + 1} \right. \quad \frac{2s}{1} \left| \frac{2s}{2s} \right. \quad \frac{L_1 = \frac{1}{2}}{\text{---}} \quad \frac{C_1 = 2}{\text{---}} \quad \checkmark$$


2nd Cauer:

$$Z(s) = \frac{1 + s^2}{2s} = \frac{1}{2s} + \frac{1}{\frac{2}{s} + 0}$$

$$\frac{\frac{1}{2s}}{2s} \left| \frac{1}{1 + s^2} \right. \quad \frac{2}{1} \left| \frac{2s}{2s} \right. \quad \frac{C_1 = 2}{\text{---}} \quad \frac{L_1 = \frac{1}{2}}{\text{---}} \quad \checkmark$$

1st Cauer and 2nd Cauer are also the same


Circulator

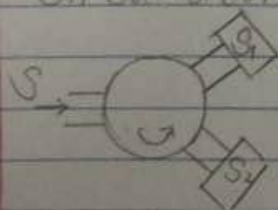

we know from the notes: $S = S_1 \cdot S_2$

$$S = \frac{s^2 - 2s + 1}{s^2 + 2s + 1} = \frac{(s-1)^2}{(s+1)^2} = S_1 \cdot S_2 = \frac{s-1}{s+1} \cdot \frac{s-1}{s+1}$$
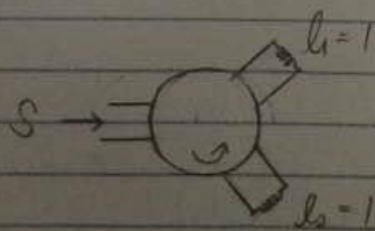
$$y_1 = y_2 = (1 + S_1)^{-1} (1 - S_1) = \frac{s+1}{2s} \cdot \frac{2}{s+1} = \frac{1}{s} \Rightarrow L = 1$$



✓