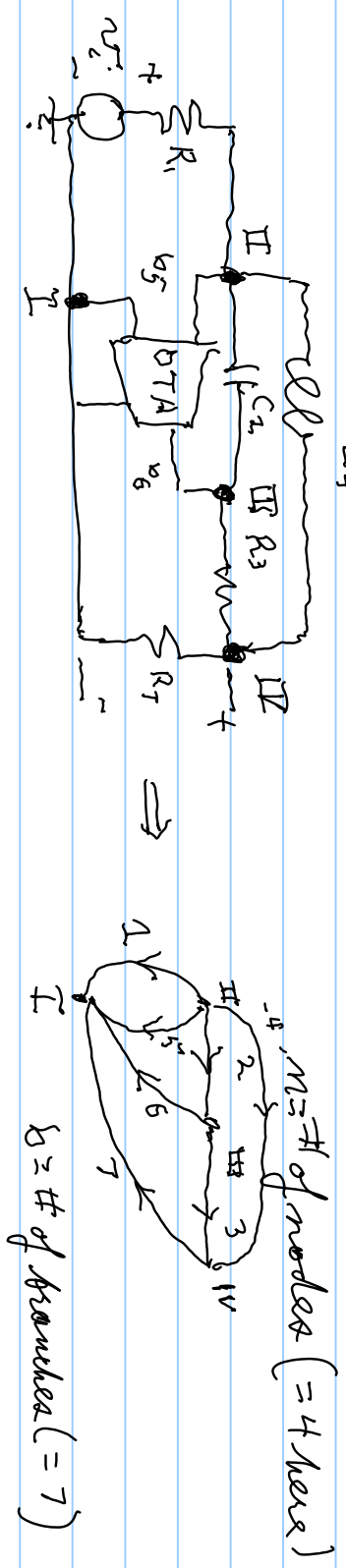



Graphs for circuits

$\sum$  of voltages around a closed path = 0  $\Rightarrow$  Kirchoff's voltage law

$\sum$  of currents into a closed surface = 0  $\Rightarrow$  Kirchoff's current law


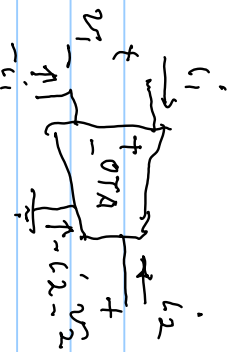
Graph = collection of points (= nodes = vertices) & collection of lines (= branches) connected to nodes






$$i_1 = 0$$

$$i_2 = g_m r_i$$

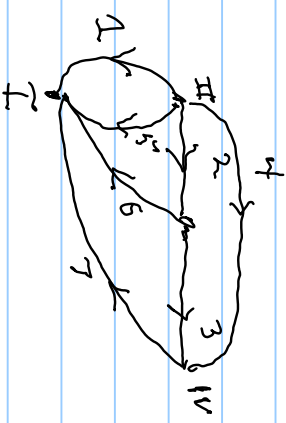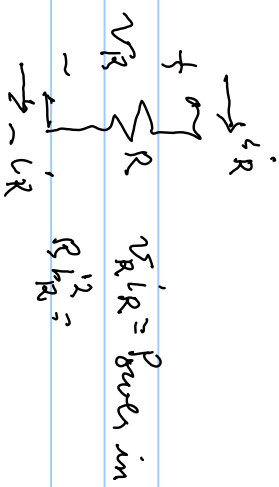

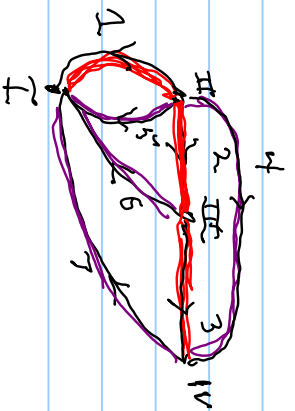Tree  $\Rightarrow$  branches connecting all nodes, no closed path  
 (# of Trees  $\Rightarrow$   $R_{short} \cdot 3 \cdot 12 \Rightarrow \det(AA^T)$ , incidence matrix



— Trees *branches*

— links = *cutset*


*branches*

$$v_T = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$v_B = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \end{bmatrix} = \begin{bmatrix} v_T \\ v_B \end{bmatrix}$$

$$v_B = \begin{bmatrix} v_4 \\ v_5 \\ v_6 \\ v_7 \end{bmatrix}$$
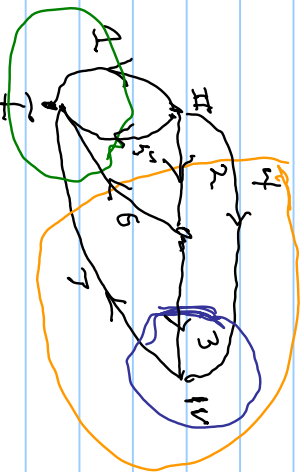
$$v_B = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \end{bmatrix}$$



— *cut 1*

— *cut 2*

— *cut 3*

$$l_4 = \begin{bmatrix} l_1 \\ l_2 \\ l_3 \end{bmatrix}$$

$$l_2 = \begin{bmatrix} l_4 \\ l_5 \\ l_6 \\ l_7 \end{bmatrix}$$

$$l_B = \begin{bmatrix} l_1 \\ l_2 \\ l_3 \end{bmatrix}$$


$$KCL: \quad 0 = i_1 + 0.5i_2 + 0.5i_3 + 0.5i_4 + i_5 + i_6 + i_7$$

$$0 = 0.5i_1 + 1.5i_2 + 0.5i_3 + 1.5i_4 + 0.5i_5 - i_6 - i_7$$

$$0 = 0.5i_1 + 0.5i_2 + 1.5i_3 + 1.5i_4 + 0.5i_5 + 0.5i_6 - i_7$$

$\Rightarrow \underline{Q}_3 = \underline{Q}_2 = \underline{Q}_1$
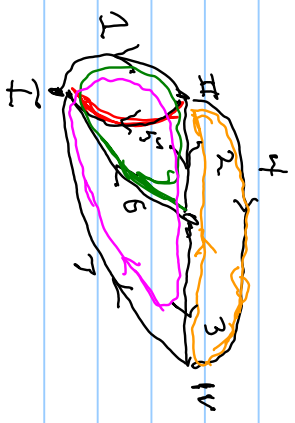
$$\underline{Q} = \text{cutset matrix} \quad \underline{Q}_3 = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 & 0 & -1 & -1 & -1 \\ 0 & 0 & 1 & 1 & 0 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \end{bmatrix}$$



KVL, tie set 1 = branches 1 & 5

$$\begin{aligned}
4 \quad 0 &= 0 \cdot v_1 - v_2 + 1 \cdot v_3 + 1 \cdot v_4 + 0 \cdot v_5 + 0 \cdot v_6 + 0 \cdot v_7 \\
5 \quad 0 &= -1 \cdot v_1 + 0 \cdot v_2 + 0 \cdot v_3 + 0 \cdot v_4 + 1 \cdot v_5 + 0 \cdot v_6 + 0 \cdot v_7 \\
6 \quad 0 &= -1 \cdot v_1 + 1 \cdot v_2 + 0 \cdot v_3 + 0 \cdot v_4 + 0 \cdot v_5 + 1 \cdot v_6 + 0 \cdot v_7 \\
7 \quad 0 &= 1 \cdot v_1 + 1 \cdot v_2 + 1 \cdot v_3 + 0 \cdot v_4 + 0 \cdot v_5 + 0 \cdot v_6 + 1 \cdot v_7
\end{aligned}
\Rightarrow \mathbf{0} = \mathbf{A} \cdot \mathbf{v}$$

$\mathbf{A} =$  tie set matrix

$$\Rightarrow \mathbf{0} = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 & 1 & 0 \\ -1 & 1 & 1 & 0 & 0 & 0 & 1 \end{bmatrix} \mathbf{v}$$

$t = \#$  of trees  $= m - 1$  (for 1 separate part)

$L = \#$  of links (= cables)  $= b - (t) = b - m + 1$

$$\mathbf{A} = \begin{bmatrix} -1 & 1 \\ 1 & 1 \end{bmatrix} \Rightarrow \mathbf{0} = -\mathbf{K}^T \mathbf{v}_t + \mathbf{1}_x \cdot \mathbf{v}_l \Rightarrow \mathbf{v}_l = -(-\mathbf{K}^T) \mathbf{v}_t$$