


$$v_b^T \begin{bmatrix} I_{L_t} \\ K^T \end{bmatrix} v_t = \begin{bmatrix} v_t^T \\ v_e^T \end{bmatrix} \Rightarrow v_b^T = C^T v_t$$

$$\Rightarrow i_b = \mathcal{O}^T i_q$$

as both known when known k

$$KVL \Leftrightarrow KCL$$
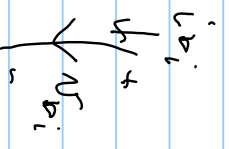
$$\begin{bmatrix} L_t \\ i_q \end{bmatrix} = i_b = \begin{bmatrix} -K \\ I_q \end{bmatrix} i_q$$



points into branch i =  $v_{b^i}^T i_b^i$

$\therefore$  points into the branches of a graph is  $v_b^T i_b(t) = 0$


$$v_b^T \cdot \mathcal{O}^T i_q = 0$$

but can put any voltages in tree branches & any resistances in links

$$\begin{matrix} \Rightarrow \\ \parallel \\ \parallel \end{matrix} \mathcal{O} \mathcal{O}^T = \mathcal{O}^{T \times R} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} -1 & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix}^T = \mathcal{O} = -K_1 + K_2$$

Essential equations


$$i_b \begin{matrix} + \\ | \\ + \\ | \\ - \end{matrix} v_b \Rightarrow$$

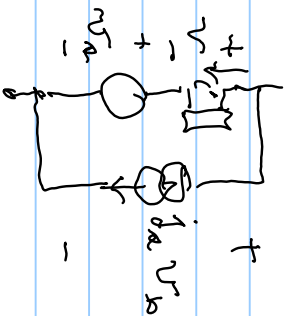

$$v_b = v_a + v_a$$

$$i_b = i_a + i_a$$

$AV = Bi$  for linear components

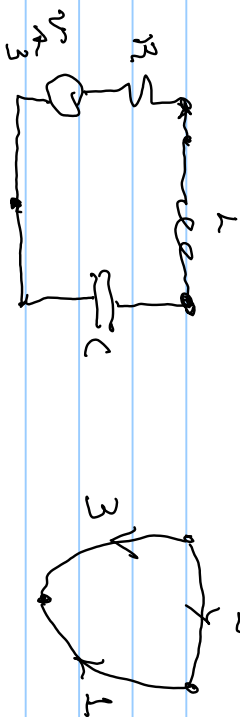

Branch 1:  $C \frac{dv_2}{dt} = i_3 = C \Delta v_1$

$\Delta = dv/dt$

Branch 2:  $L \frac{di_2}{dt} = v_2 = R_2 i_2 = v_2$


Branch 3:  $v_b = v_3 + v_a = R_3 i_3 + v_a$

$\Rightarrow v_3 = R_3 i_3 = v_b - v_a$

$$\begin{bmatrix} CA & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & R_2 & 0 \\ 0 & 0 & R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

$$\begin{matrix} v_b \\ v_a \end{matrix} = \begin{bmatrix} CA & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_b \\ v_a \\ v_a \end{bmatrix} \sim \begin{bmatrix} CA & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_b \\ v_a \\ v_a \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & R_2 & 0 \\ 0 & 0 & R_3 \end{bmatrix} i_b$$
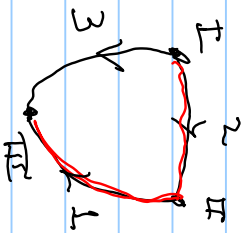
$$\begin{bmatrix} CA & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} e^{A^T t} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & R_2 & 0 \\ 0 & 0 & R_3 \end{bmatrix} \mathcal{V}^T \mathbf{i}_x = \begin{bmatrix} CA & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \mathcal{V}_{R_3} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \mathcal{V}_{R_3} \end{bmatrix}$$



Red:  $\Rightarrow 0 = 1 \cdot v_1 + 0 \cdot v_2 + 1 \cdot v_3 \Rightarrow e = \begin{bmatrix} 1 & 0 & 1 \\ 0 & 1 & 1 \end{bmatrix}$

KCL:  $\Rightarrow 0 = 0 \cdot i_1 + 1 \cdot i_2 + 1 \cdot i_3$

KVL:  $\Rightarrow 0 = -1 \cdot v_1 - 1 \cdot v_2 + 1 \cdot v_3 \Rightarrow e = \begin{bmatrix} -1 & -1 & 1 \\ 1 & 1 & 1 \end{bmatrix}$


$$\begin{bmatrix} CA & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & R_2 & 0 \\ 0 & 0 & R_3 \end{bmatrix} \begin{bmatrix} -1 \\ -1 \\ 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \mathcal{V}_{R_3} \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} CA & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \mathcal{V}_{R_3} \end{bmatrix} \Rightarrow \text{beqs. \& brunkenwerte, } x = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$\begin{bmatrix} C & 0 & 0 \\ 0 & 0 & -L \\ 0 & 0 & 0 \end{bmatrix} Ax = \begin{bmatrix} 0 & 0 & 1 \\ 0 & -1 & 0 \\ -1 & -1 & -R_3 \end{bmatrix} x + \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix} v_3 \Rightarrow \frac{d}{dt} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = Ax + Bu, \quad \begin{matrix} u = \text{input} = 1 \text{ volt} \\ y = \text{output} = 5 \text{ volts} \end{matrix}$$

If the output is the voltage on the capacitor then  $v_{out} = v_1$   $y = \text{output} = v_{out} = 1 \text{ volt}$   
 $= 1 \text{ volt}$   
 here

$$y = [1 \ 0 \ 0] x = Cx$$

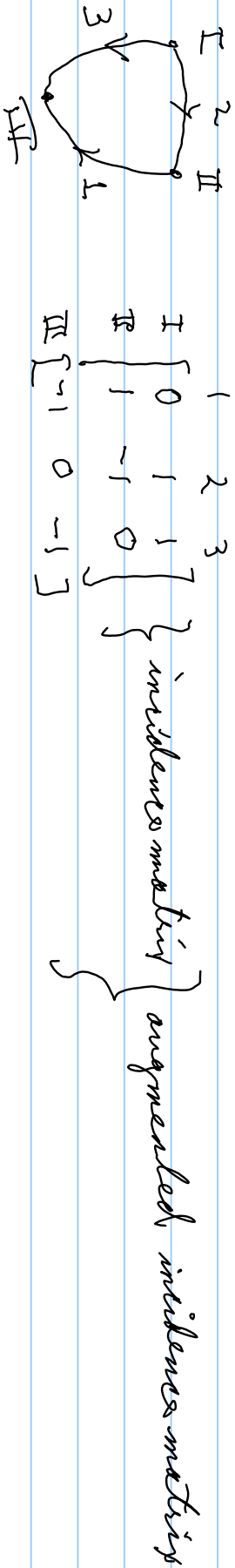

incidence incidence transpose

$$\begin{bmatrix} 0 & 1 & 1 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} 0 & 1 \\ 1 & -1 \\ 1 & 0 \end{bmatrix} = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix}$$

let  $\det \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix} = 4 - 1 = 3 = \# \text{ of trees for this graph}$

