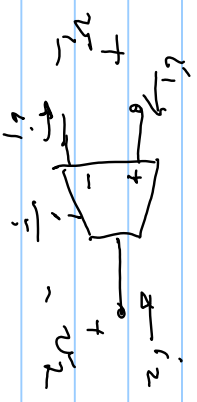


OTA



$$i_2 = g_m v_1$$

$$i_1 = 0$$

$$P(t) = v_1 i_1 + v_2 i_2 = v_2 i_2 = v_1 v_2 \cdot g_m$$

can be negative if $v_2 = -v_1 \neq 0$, $g_m > 0$

Passes into OTA

OR $P(t) < 0$ can occur then the energy in can be negative

\Rightarrow active device

$$E(t) = \int_{-\infty}^t P(x) dx \quad \text{passive if } > 0 \text{ for all } v \& i$$




$$i_1 = i_2 = g_m v_1$$

Equivalent to


$$\text{passive, } P = v_1 i_1 = v_1^2 g_m > 0 \quad R = \frac{1}{g_m} \quad G = \frac{1}{R} = g_m$$

also

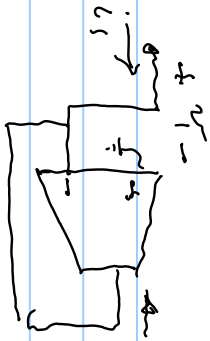

$$i_1 = i_2 = -g_m v_1 \Rightarrow$$
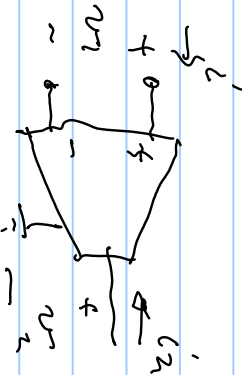
$$\left. \begin{matrix} R = -\frac{1}{g_m} \\ \Rightarrow G = -g_m < 0 \end{matrix} \right\}$$



$$\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\Rightarrow i_2 = g_m v_1 \quad Y \text{ is a } 2 \times 2$$


admittance matrix

in general if every branch has an admittance

$$A(A) \cdot v = I_b \quad ; \quad v = v_b - v_a$$

$$I = I_b - I_a$$

note

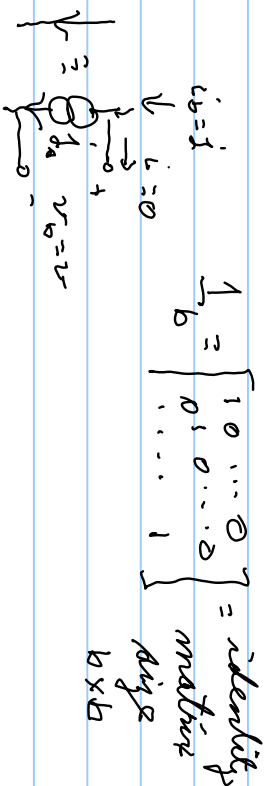

$$i_b = i$$

$$v_b = 0$$

$$I_b = \begin{bmatrix} 1 & 0 & \dots & 0 \\ 0 & 1 & 0 & \dots & 0 \\ \dots & \dots & \dots & \dots & \dots \\ 0 & \dots & \dots & \dots & 1 \end{bmatrix} = \text{identity matrix}$$

$b \times b$

$$A(n) v_b = 1_b i_b - 1_b i_a$$

$$v_b = E \cdot v_E, \quad 1_b = \sigma^T \cdot i_a \Rightarrow C \sigma^T = 0_{t,r}$$

$$A \cdot E^T v_E - 1_b \sigma^T i_a = -I_a$$

$$\underbrace{\begin{bmatrix} A E^T & -\sigma^T \end{bmatrix}}_{(b \times (t+r)) \text{ matrix}} \underbrace{\begin{bmatrix} v_E \\ i_a \end{bmatrix}}_{b \text{ vector}} = \underbrace{-I_a}_{b \text{ vector}}$$

x E = output matrix



$$\underbrace{\begin{bmatrix} C & A E^T \end{bmatrix}}_{t \times t} \underbrace{\begin{bmatrix} v_E \\ i_a \end{bmatrix}}_{t+r} = \underbrace{-E i_a}_{t \times r} \Rightarrow \underbrace{C A E^T}_{t \times r} v_E + 0_{t,r} i_a = \underbrace{-E i_a}_{t \times r}$$

t eq. in t unknowns

an admittance

n Norton type's current sources

Example

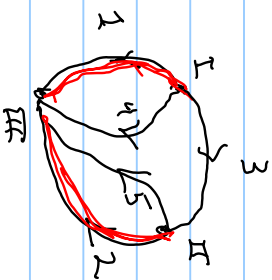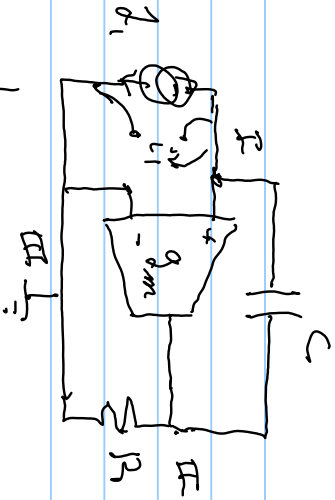

$b=5, t=2, R=3$

$$[0] = C i_b = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 1 & 1 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & 0 & 0 & 1 \end{bmatrix} v_b$$

$$i_a = \begin{bmatrix} i_1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}, -E i_a = - \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} -1 \\ 0 \end{bmatrix}$$

$A v = B i'$

$$= \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} -1 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$v_b = \begin{matrix} 1 \\ 1 \\ v \end{matrix} C v_f^T, \quad i_b = A v.$$

works well if have admittances for branches