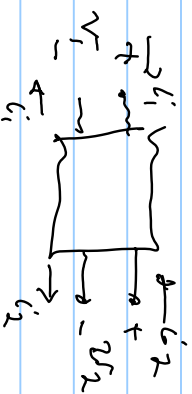


2-port



$$P_{in}(t) = v_1(t)i_1(t) + v_2(t)i_2(t)$$

$$v = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}, \quad i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

admittances  $i = Yv$   
impedances  $v = Zi$


$$\Rightarrow ZY = I_2 = YZ$$



$$v_A + i_B = Y_A v_A + Y_B v_B, \quad v_A = v_B = v$$

$$\text{if } i = (Y_A + Y_B)v \Rightarrow Y = Y_A + Y_B$$

Ex:

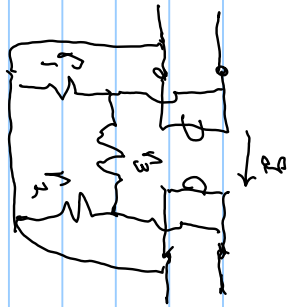

$$Y = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix}$$

$$Y_{in} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \times \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = y_{11}v_1 + y_{12}v_2$$

$$y_{11} = i_1 / v_1 \text{ if } v_2 = 0 = \text{short}$$




$$y_{11} = g_1 + g_2$$

$$g_1 = 1/R_1, g_2 = 1/R_2$$

$$y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0} = g_2 + g_3 \quad y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0}$$

$$= -g_3$$


$$y_{21} = -g_3 \text{ by symmetry}$$

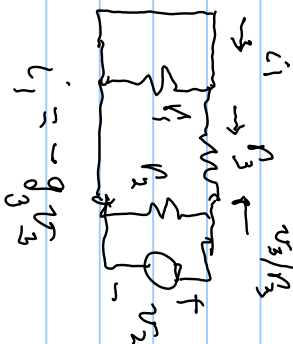

$$Y = \begin{bmatrix} g_1 + g_2 & -g_3 \\ -g_3 & g_2 + g_3 \end{bmatrix}$$



$$Y = Y_{ggs} + Y_{msk} = \begin{bmatrix} 0 & g_3 \\ -g_3 & 0 \end{bmatrix} + \begin{bmatrix} g_1+g_3 & -g_3 \\ -g_3 & g_2+g_3 \end{bmatrix} = \begin{bmatrix} g_1+g_3 & g-g_3 \\ -g-g_3 & g_2+g_3 \end{bmatrix}$$

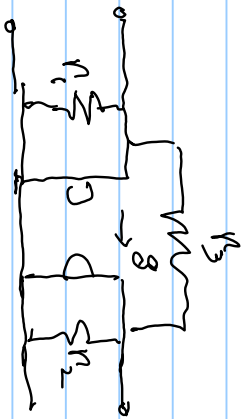if  $g = g_3$  then  $Y = \begin{bmatrix} g_1+g_3 & 0 \\ -2g_3 & g_2+g_3 \end{bmatrix} \Rightarrow$  unilateral "gain"  
i.e.  $v_1 = 0, v_2$




$$= Y = \begin{bmatrix} g_1 & 0 \\ 0 & 0 \end{bmatrix} + \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & g_2 \end{bmatrix} + \begin{bmatrix} g_3 & -g_3 \\ -g_3 & g_3 \end{bmatrix}$$

nodeal model  
 indefinite admittance:

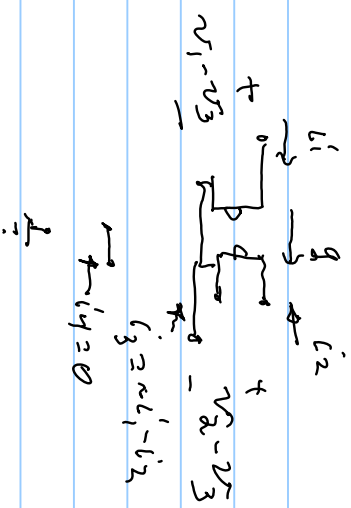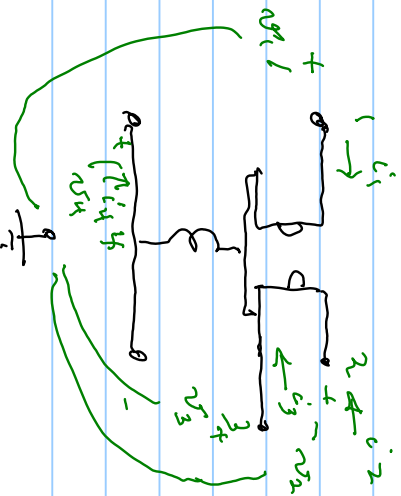
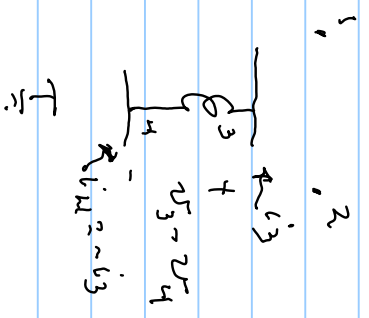
$$Y_{qys} = \begin{bmatrix} 0 & g & -g & 0 \\ -g & 0 & g & 0 \\ 0 & g & -g & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$



$$Y_{indus} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{AR} + \frac{1}{AR} & 0 \\ 0 & 0 & 0 & -\frac{1}{AR} + \frac{1}{AR} \end{bmatrix}$$

$$Y_{ind} = \begin{bmatrix} 0 & g & -g & 0 \\ -g & 0 & g & 0 \\ g & -g & \frac{1}{AR} + \frac{1}{AR} & -\frac{1}{AR} \\ 0 & 0 & -\frac{1}{AR} & \frac{1}{AR} \end{bmatrix} = \text{indefinite admittance}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = Y_{int} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$


more ground to node 4  $\Rightarrow v_4 = 0$  & ignores  $i_4$  (as  $i_4 = -i_1 - i_2 - i_3$ )

$$\begin{matrix} \text{port} \\ \left[ \begin{matrix} i_1 \\ i_2 \\ i_3 \end{matrix} \right] \end{matrix} = \begin{bmatrix} 0 & g & -g \\ -g & 0 & g \\ g & -g & 1/A_2 \end{bmatrix} \begin{matrix} \text{node} \\ \left[ \begin{matrix} v_1 \\ v_2 \\ v_3 \end{matrix} \right] \end{matrix}$$

Y<sub>ad</sub> nodal admittances

$$= \begin{bmatrix} 0 & g & -g \\ -g & 0 & g \\ g & -g & 1/A_2 \end{bmatrix}$$

But if want the 2-port Y for

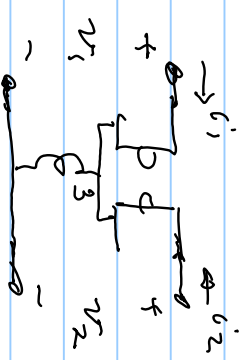

node 3 is internal  $\Rightarrow i_3 = 0$

$\therefore$  can solve for  $v_3$  (& eliminate it) in terms of  $v_1$  &  $v_2$

$$0 = \begin{bmatrix} \text{port} \\ \left[ \begin{matrix} i_1 \\ i_2 \end{matrix} \right] \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_{port} \\ v_{int} \end{bmatrix}$$

$$\Rightarrow 0 = Y_{11} v_{port} + Y_{21} v_{int}$$


$$v_{int} = -Y_{21}^{-1} Y_{11} v_{port}$$



$$v_{port} = Y_{11} v_{port} - Y_{12} Y_{22}^{-1} Y_{21} v_{port} = (Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}) v_{port}$$

$$(2-port) \quad Y = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21} \Rightarrow \text{Simplify } Y = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} - \frac{1}{Y_{22}} \begin{bmatrix} g & -g \end{bmatrix}$$
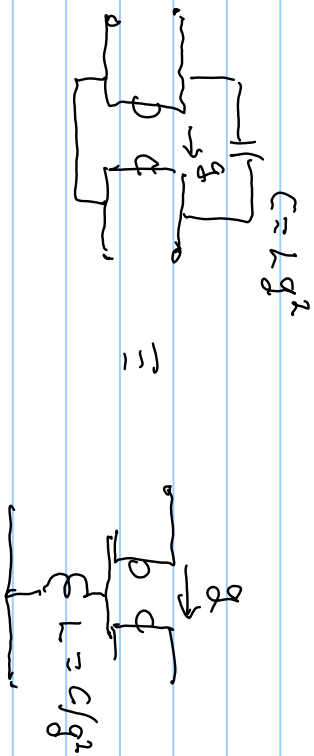
$$Y = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} - \frac{1}{g^2} \begin{bmatrix} -g^2 & g^2 \\ g^2 & -g^2 \end{bmatrix} = \begin{bmatrix} g & -g \\ -g & g \end{bmatrix}$$



$$g = 10^{-3}$$

$$L = 10^6 C$$

$$C = 1 \mu F, L = 1 H$$