

$$v = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}, \quad i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$e = \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} R_1 & 0 \\ 0 & R_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$i = Yv, \quad v = Zi$$

normalizing to $R_1 = R_2 = 1$

$$2v = v + i = v + Ri \Rightarrow v = \frac{1}{2} e$$

2 independent voltages

$$2v + 2v = v + i + (v - i) = 2v$$

$$2v - 2v = v + i - (v - i) = 2i$$



2 reflected voltages

$$\Rightarrow v = v^i + v^n$$

$$i = v^i - v^n$$

some lines with them $a = v^i$
 $b = v^n$

$S =$ weathering matrix $\Rightarrow v^n = S v^i$

$$2 v^n = v^i = 2 S \left(\frac{v^i}{2} \right) = S v^i + S v^i = v^n + v^i \Rightarrow S v^i + v^i = v^n + S v^n$$

$$\Rightarrow (S + I_2) v^i = (I_2 - S) v^n \Rightarrow v^i = (S + I_2)^{-1} (I_2 - S) v^n$$


also $(S + I_2) y = I_2 - S \Rightarrow y - I_2 = -S - S y = -S (I_2 + y)$

$$\Rightarrow (I_2 - y) (I_2 + y)^{-1} = S$$

also $S = (I_2 + y)^{-1} (I_2 - y)$ also $(I_2 + y) (I_2 - y) = (I_2 - y) (I_2 + y)^{-1}$


$$I_2 - y^2 = (I_2 - y) (I_2 + y) = (I_2 + y) (I_2 - y) = I_2 - y^2$$

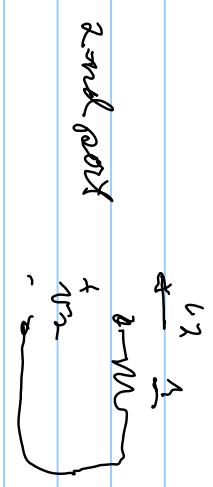other one 2-port, def $2V_2' = 0 = E_2 \Rightarrow V_1 + i_2 = 0 \Rightarrow i_2 = -V_2$



$$2V_2' = V_2 - i_2 = 2V_2 \Rightarrow V_2 = V_2'$$

let port

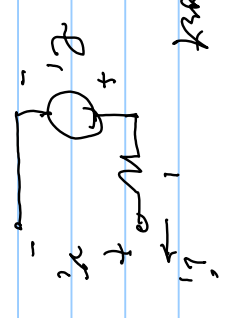

$$\Rightarrow E_1 = V_1 + i_1 = R V_1' \Rightarrow \frac{V_2'}{V_1'} \Big|_{V_2' = 0} = S_{21}$$

$$\frac{1}{2} S_{21} = \frac{V_2'}{E_1}$$

$$\begin{bmatrix} V_1' \\ V_2' \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1' \\ V_2' \end{bmatrix}$$

$$\Rightarrow V_2' = S_{21} V_1' \Rightarrow \frac{V_2'}{V_1'} = S_{21}$$

$$\frac{V_2'}{E_1} = S_{21} \Rightarrow \frac{V_2'}{E_1} = S_{21}$$

↑↑ Terminated voltage gain


$E_1: \begin{matrix} \text{---} & | & \text{---} \\ & \text{---} & \\ & & \text{---} \end{matrix} \quad C$
 $Y = \begin{bmatrix} RC & -RC \\ -RC & RC \end{bmatrix}$; $\det Y \neq 0$ nor Z exists
 as Y is singular

$$S = (I_2 + Y)(I_2 - Y)^{-1} = \begin{bmatrix} 1+RC & -RC \\ -RC & 1+RC \end{bmatrix}^{-1} \begin{bmatrix} 1-RC & RC \\ RC & 1-RC \end{bmatrix} = \begin{bmatrix} 1+RC & RC \\ RC & 1+RC \end{bmatrix} \begin{bmatrix} 1-RC & RC \\ RC & 1-RC \end{bmatrix}$$

$$\det(I_2 + Y) = (1+RC)^2 - (RC)^2 = 1+2RC$$

$$= \frac{1}{1+2RC} \begin{bmatrix} 1 & 2RC \\ 2RC & 1 \end{bmatrix} = S$$


$$S_{11} = \frac{2RC}{1+2RC}$$

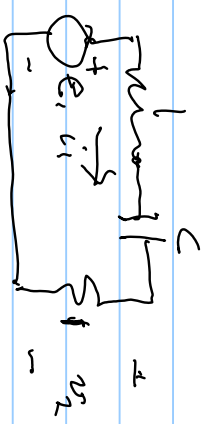

$$(2 + \frac{1}{RC})v_1 = e_1 \Rightarrow i_1 = \frac{e_1}{2 + \frac{1}{RC}} = v_2 \Rightarrow \frac{v_2}{e_1} = \frac{1}{2 + \frac{1}{RC}}$$

as i_1 flows in $R_2 = 1\Omega$

$$\frac{v_2}{e_1} = \frac{RC}{1+2RC}$$

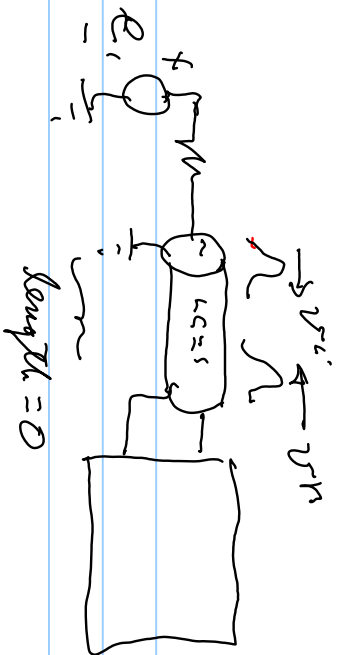

gives a physical meaning to S

$$\int_{-\infty}^T v^{i^T} v^i dx < \infty \text{ call } v^i \text{ an } L_2 \text{ function} \Rightarrow \text{square integrals}$$

$$= \int_{-\infty}^T (v+i)^T (v+i) dx = \int_{-\infty}^T (v^T v + v^T i + i^T v + i^T i) dx$$

$$= \int_{-\infty}^T v^T v dx + \int_{-\infty}^T i^T i dx + 2 \int_{-\infty}^T v^T i dx < \infty \text{ for all } t$$

(can let $t \rightarrow \infty$)

part 1:

= power into 2 parts

show that $E(t) = \int_{-\infty}^t p(\tau) d\tau > 0$ that τ & i are also L_2 functions