

$$i = y_a e, \quad e = v + i$$

$$v = e - y_a \cdot e = (I_m - y_a) e$$

$$e = v + i = 2v$$

$$2v^N = v \sim i = (I_m - y_a) e = (I_m - 2y_a) \cdot 2v^i$$

$$v^N = S \cdot v^i, \quad S = I_m - 2y_a$$

$$Av = B i$$

$$\Rightarrow y B \Rightarrow B A v = i \Leftrightarrow y = B A$$

$$\Rightarrow y A \Rightarrow v = A^{-1} B i \Rightarrow Z = A^{-1} B$$

$$Z^{-1} = (A^{-1} B)^{-1} = B^{-1} (A^{-1})^{-1} = B^{-1} A$$

for $v = v^i + v^N$

$$i = v^i - v^N$$

$$A \cdot v = A(v^i + v^r) = B i + B(v^i - v^r) \Rightarrow (A+B)v^i = (A+B)v^r$$

$$(B+A)^{-1} (B-A) \cdot v^i = v^r \Rightarrow S = (B+A)^{-1} (B-A)$$

$$\text{if } y \text{ exists} = B^{-1} A \Rightarrow S = (B(I_m + B^{-1}A))^{-1} (B(I_m - B^{-1}A)) = (I_m + Y)^{-1} B^{-1} B(I_m - Y)$$

$$= (I_m + Y)(I_m - Y)$$


Ex: $m=1$: one root, $Y = RC$ then $S = \left(\frac{1}{1+RC} \right) (1-RC) = \frac{1-RC}{1+RC}$

a real @ $R = -1/C$ & a zero $R = +1/C$


$R = \sigma + j\omega$ poles

$$\text{here } |S(\omega)| = \frac{|1-j\omega C|}{|1+j\omega C|} = \frac{\sqrt{1+(\omega C)^2}}{\sqrt{1+(\omega C)^2}} = 1$$

$R = j\omega$

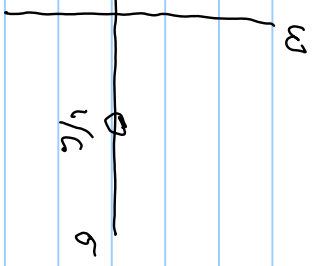

Look @ the negative impedance converter

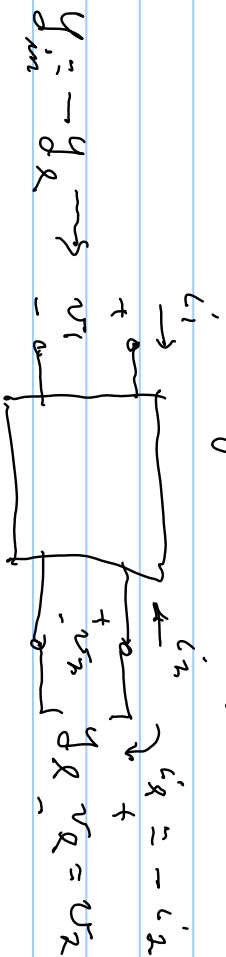

$$y_{in} = g_R v_2$$

$$\frac{i_1}{v_1} = g_{in} = \frac{-g_R v_2}{v_2} = -g_R$$

But hard to build in VLSI

Look @


$$\left. \begin{array}{l} i_1 = g_{m12} v_2 \\ \text{OTA} \end{array} \right\} \begin{array}{l} i_2 = g_{m21} v_1 \end{array}$$

$$\text{ref } i_2 = -g_R v_2$$

$$\Rightarrow -g_R v_2 = g_{m21} v_1$$

$$g_{m12} v_2 = i_1$$
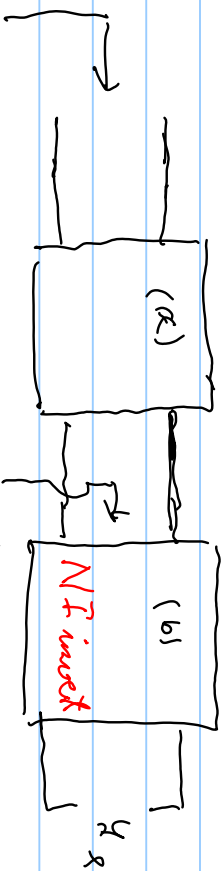
$$\Rightarrow \frac{-g_R v_2}{g_{m12} v_2} = \frac{g_{m21} v_1}{i_1} \Rightarrow \frac{i_1}{v_1} = g_{in} = \frac{g_{m12} g_{m21}}{g_R}$$



NIC = negative impedance converter

$$\begin{aligned} & -g_{m12}^{(a)}, g_{m11}^{(a)} \\ & \left(\frac{-g_{m12}^{(b)} g_{m21}^{(b)}}{g_R} \right) \end{aligned}$$

$$\begin{aligned} & -g_{m12}^{(b)}, g_{m21}^{(b)} \\ & \frac{g_R}{g_R} \end{aligned}$$

choose for (a) $g_{m12}^{(a)} = -g_{m21}^{(a)} = g_m^{(a)}$ \Rightarrow $g_{m12}^{(b)} = g_{m21}^{(b)} = g_m^{(b)}$ \Rightarrow NI invert

Then $y_{in} = -\frac{(g_m^{(a)})^2}{(g_m^{(b)})^2} i_{in} \Rightarrow$ can build with OTA's

If look @ S for $y = -y_R \Rightarrow S = (1 + (-y_R))^{-1} (1 - (-y_R))^{-1} = \frac{1}{S_R}$ where $S_R = (1 + y_R)(1 - y_R)$

∴ can divide S_a : $S \Rightarrow S = S_a^{-1}$
of more interest is getting $S = S_a \cdot S_b$ which retains generality

use the circulator



$$v^N = S v^i$$

$$v_1^N = v_3^i$$

$$v_2^N = v_1^i$$

$$v_3^N = v_2^i$$

$$v_2^N = v_1^i = \text{incident on Load } N_b$$

$$v_2^i = \text{reflected from Load } N_b \hat{=} S_b \cdot v_2^N$$

$$v_3^N = v_2^i \Rightarrow \text{into Load port } 3 = N_a$$

$$v_3^i = \text{reflected not things from } N_a = S_a v_3^N$$

