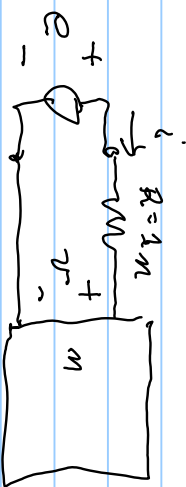


Homework 4 now due 10/09 = Tues.



$$P_o(t) = v^-(t) i(t) = \text{Re}(v^{T*}(t) i(t))$$

for real  $v(t), i(t)$

$$E(t) = \int_{-\infty}^t p_o(r) dr \geq 0 \text{ for passive}$$

$$E \leq L_2 \Rightarrow \int_{-\infty}^{\infty} e^{T*} e^{T} dx < \infty$$

$\Rightarrow v^-(t), v^+(t), v(t), i(t)$  are all in  $L_2$

$$\int_{-\infty}^{\infty} v^{T*}(t) i(t) dt = \int_{-\infty}^{\infty} V_j^{T*}(\omega) I_j(\omega) d\omega, \quad \omega = 2\pi f$$

$\therefore$  for passive circuits this gives constraints

$S(\lambda) \Rightarrow$  Bounded Real,  $n \times n$

$Y(\lambda) \Rightarrow$  Positive Real,  $n \times m$

$$A = \sigma + j\omega$$

a)  $S(\sigma)$  is real for  $\lambda = \sigma \geq 0$   
(real residues)

$Y(\lambda)$  is real for  $\lambda = \sigma > 0$

b)  $S(\lambda)$  is analytic in  $\sigma > 0$

$Y(\lambda)$  is analytic for  $\sigma > 0$

a)  $\frac{1}{s} - S^T(\lambda) S(\lambda)$  is positive  
semi-definite  
in  $\sigma \geq 0$

(positivity  $\Rightarrow$  bounded)

$Y^T(\lambda) + Y(\lambda)$  is positive  
semi-definite  
in  $\sigma > 0$

$$\Rightarrow V^T (Y(\lambda) + Y^T(\lambda)) V \geq 0 \text{ in } \sigma > 0$$

if rational (BR)

(PR)

a) coefficients real

coefficients real

b) no poles in  $\sigma \geq 0$

no poles in  $\sigma > 0$

a) as for Bounded Real

as for Positive Real

$$\frac{N(\lambda)}{D(\lambda)} \Rightarrow \text{Polynomial N/D}$$

for  $m \geq 1$  (b)  $PR$   
real coef.

a) only poles (zeros in  $S \geq 0$ )  
(more on  $j\omega$  axis)

a)  $|S(a)| \leq 1$  in  $S \geq 0$   
but can be only  
max  $|S(j\omega)| \leq 1$

zeros:  $\mathcal{E}(0) = 0$

max case

(p)  $PR$

real coef.

only poles (zeros in  $S \geq 0$ )  
(simple poles on  $j\omega$  axis)

$\Re(Y(j\omega) + Y^*(j\omega)) \geq 0$

note  $Y^*(s) = Y^*(j\omega)$  if  $PR$   
 $s = j\omega$

zeros  
not polynomials

poles are zeros of  
the denominator  
(or  $\infty$ )

$PR, PR \Rightarrow I_m - S^T(-\omega)S(j\omega) = 0_m$   
 $I_m - S^T(s)S(s) = 0_m$

Let  $\omega = a/j$  for an analytic continuation from  $a = j\omega$  for all  $a$  except poles

$\Rightarrow$  zeros:  $I_m - S^T(-a)S(a) = 0_m$   
 $\uparrow$   
 $\therefore S^T(-a) = S^{-1}(a)$

$\Re(Y^T(a) + Y(a)) = 0_m$  on  $j\omega$  axis  
 $\Re(Y^T(-j\omega) + Y(j\omega)) = 0_m$

$Y^T(-a) + Y(a) = 0_m$

$Y^T(-a) = -Y(a)$

Ex:  $F(a) = \frac{a+a}{a+b} \Rightarrow$  for  $b^R$ ,  $\left| \frac{a}{b} \right| \leq 1$  at  $a=0$ ; at  $a=\infty \Rightarrow \frac{a}{a} = 1$

for  $a \in \mathbb{R}$  @  $a = -b \Rightarrow b > 0$  if  $F(a)$  is  $b^R$ , if  $F(a)$  is  $p^R$  then  $b \geq 0$

check for  $b^R$ :  $\left| \frac{a+a}{a+b} \right| \leq 1 \Rightarrow \left| \frac{2a+a}{2a+b} \right|^2 = \frac{a^2 + \omega^2}{b^2 + \omega^2} \leq 1 \Rightarrow a^2 + \omega^2 \leq b^2 + \omega^2$  if  $b^R$   
 $a^2 \leq b^2$  but  $b > 0$

$A = \frac{a}{b}$




check for  $p^R$ : (if  $p^R$ , then  $Z = 1/y$  is  $p^R$ )  $\Rightarrow a \geq 0, b \geq 0$

synthesis:  $Y(a) = \frac{a+a}{a+b} = \frac{a}{a+b} + \frac{a}{a+b} = \frac{1}{\frac{a+b}{a}} + \frac{1}{\frac{a+b}{a}} = \frac{1}{Z_1} + \frac{1}{Z_2} \Rightarrow$

$Z_1 = \frac{a+b}{a} = 1 + \frac{1}{a/b} \Rightarrow$   $\underbrace{\frac{1}{a/b}}_{\text{residue}}$   $\underbrace{\frac{1}{a/b}}_{\text{residue}}$   $Z_2 = \frac{a+b}{a} \Rightarrow$

residue

residue

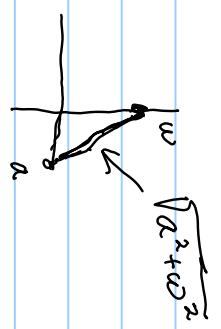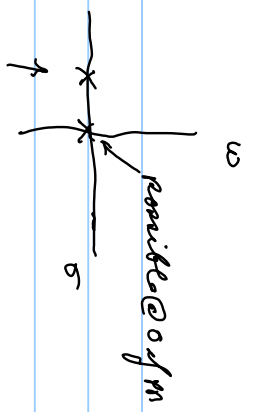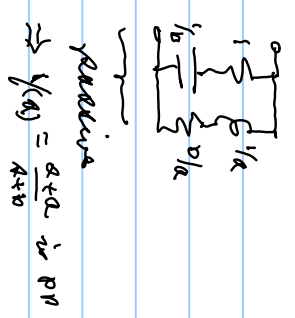

for open terminals

$$S(a) = \frac{a+a}{a+b}$$

$$Y(a) = \frac{1-S}{1+S}$$

$$= \frac{1 - \frac{a+a}{a+b}}{1 + \frac{a+a}{a+b}}$$

$$= \frac{a+b-a-a}{a+b+a+a}$$

$$= \frac{(1-1) + b-a}{2a + (b+a)}$$

positive

$$Y(a) = \frac{1}{\frac{2a}{b-a} + \frac{b+a}{b-a}}$$

→

$$L = 2/b-a$$

$$R = \frac{b+a}{b-a}$$

if  $a=b$ ,  $S=1 \Rightarrow$  open circuit ( $i=0$ )