

$$y(s) = \frac{5s^2 + 4s + 8}{s^2 + s + 2}$$

if PR desired to synthesize by Bode-Bangfu scheme

To find max. & min on $j\omega$ axis of $\text{Re } y(s)$, $\sigma \geq 0$

$$\text{take } e^{y(s)} \text{ \& } e^{-y(s)}$$

$$e^{y(s)} = e^{\text{Re } y + j \text{Im } y} = e^{\text{Re } y} \cdot e^{j \text{Im } y} \Rightarrow |e^{y(s)}| = e^{\text{Re } y}$$

$$|e^{-y(s)}| = e^{-\text{Re } y}$$

\Rightarrow min of $\text{Re } y(j\omega)$ occurs on $j\omega$ axis if $y(s)$ is analytic in $\sigma \geq 0$

\Rightarrow use max modulus theorem

Find $\text{Re } y(j\omega)$ in minimum; $\omega_0^2 = 2$; then $y(j\omega_0) = 2 + jB(\omega_0)$

$$\omega_0 = \sqrt{2}$$

\uparrow \uparrow
max. admittance

$$y_m(s) = y(s) - 2, \quad \text{Re } y_m(j\omega_0) = 0, \quad \& \text{Re } y_m(j\omega) \geq 0 \text{ for } y_m \text{ in PR}$$

$$y_m(a) = \frac{a^2 + 2a + 4}{2a^2 + a + 2} ; y_m(j\omega_0) = 0 - 1.414j \quad i = \sqrt{-1}$$

Obtain this transfer by using the Richards' function

$$y_n(s) = y_m(k_2) \left[\frac{k_2 y_m(k_2) - j\omega_0 y_m(a)}{k_2 y_m(a) - j\omega_0 y_m(k_2)} \right]$$

$$y_n(j\omega_0) \Rightarrow \text{numerator is } k_2 y_m(k_2) - j\omega_0 \cdot (-1.414j) = k_2 y_m(k_2) - \omega_0 (1.414)$$

$$\frac{y_n}{y_m} =$$

$$= k_2 y_m(k_2) - 2 \quad \text{denote } a > 0 \text{ to make this } 0$$

$$\therefore \text{ find } k_2 \text{ for } k_2 y_m(k_2) = 2 \Rightarrow k_2 = k_3 = 0 \Rightarrow |y_n(a)| = 0 ; y_n(a) \text{ is rational, not } = 0$$

$\therefore y_n(a) \Rightarrow (a^2 + \omega_0^2)$ factors as we proceed $y_n(j\omega_0) = 0$ by $k_2 = k_3$
a = j\omega_0 & a = -j\omega_0 are rational with real coefficients

also $a = k_3$ factor $y_n(a) = \frac{k_2 (a^2 + \omega_0^2) (a - 2)}{(a - 2) (2a^2 + a + 2)}$
 $\therefore y_m(k_3) = \frac{4 + 2 \cdot 2 + 4}{2 \cdot 2^2 + 2 + 2} = \frac{12}{12} = 1$

$$y_n(s) = 1 \cdot \left(\frac{(s-2)(s^2+2)}{(s-2)(2s^2+3s+4)} \right) = \frac{s^2+2}{2s^2+3s+4} \Rightarrow \frac{1}{y_n(s)} = 2 + \frac{3s}{s^2+2} = 2 + \frac{1}{\frac{1}{s} + \frac{1}{3s}} \leftarrow a_2$$

If y_n is an admittance then $y_n \Rightarrow$



If y_n is an impedance $Z_n = \frac{s^2+2}{(2s^2+3s+4)}$ then



$$\Rightarrow \frac{y_n(s)}{y_m(s)} = \frac{1 - \frac{A \cdot y_m(s)}{y_n(s)}}{\frac{y_m(s)}{y_n(s)} - \frac{A}{R}}$$


$$\Rightarrow \hat{y}_{ca} = \frac{y_n(s)}{y_m(s)}, \quad \hat{y}_{cm} = \frac{y_m(s)}{y_n(s)}$$

$$\hat{y}_n = \frac{1 - \frac{A}{R} \hat{y}_m}{\hat{y}_m - \frac{A}{R}} \Rightarrow \hat{y}_n \left(\hat{y}_m - \frac{A}{R} \right) = 1 - \frac{A}{R} \hat{y}_m$$

$$\hat{y}_{cm} \left(\hat{y}_n + \frac{A}{R} \right) = 1 + \frac{A}{R} \hat{y}_n \Rightarrow \hat{y}_{cm}(s) = \frac{1 + \frac{A}{R} \hat{y}_n}{\frac{A}{R} + \hat{y}_n} = \frac{1}{1 + \frac{A/R}{\hat{y}_n} + \frac{\hat{y}_n}{1 + A/R \hat{y}_n}}$$


end circuit
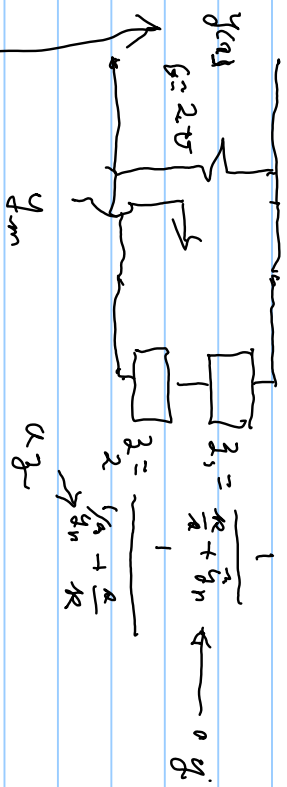
$$y_{dm}(s) = \frac{1}{\frac{1}{R} + g_n} + \frac{1}{\frac{1}{\frac{1}{R} + g_n} + \frac{1}{R}}$$



$$z_1 = \frac{1}{\frac{1}{R} + g_n}$$
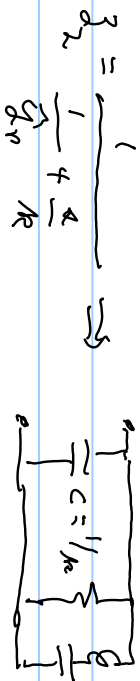
$$y_{dm}(s) = \frac{5s^2 + 4s + 8}{2s^2 + s + 2}$$



use 6 reactive elements
