

$i_1 = 0$   
mean input = no load

$v_1 = \frac{1}{g}$  linker Y device  
output  $v_0$


$$\frac{v_0}{v_1} = \frac{N(z)}{D(z)} \Rightarrow D = \frac{N(z)}{D(z)} \text{ assume no poles at } z = \infty$$

making D in state equation = constant  $v_1$  &  $v_0$  assumed (K)

$$= \frac{b_0 s^{-1} + \dots + b_{r-1} s^{-r} + b_r + b_0}{a^s + a s^{-1} + \dots + a_{r-1} s^{-r} + a_0}$$

;  $a$  &  $b$  constant  
single output & input
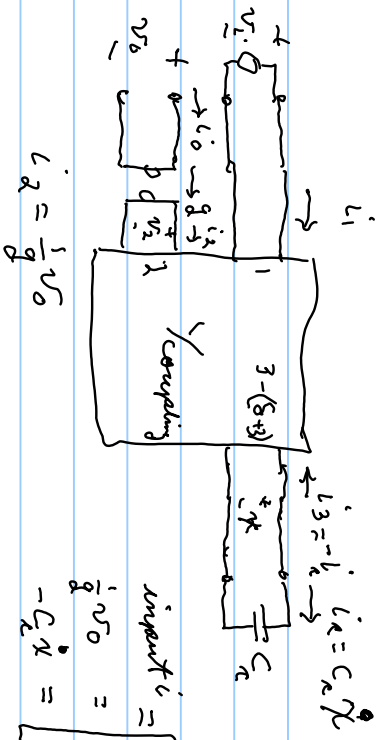
$$\Rightarrow X = Ax + Bv_1, v_0 = Cx + Dv_1$$



$$i_2 = \frac{1}{g} v_0$$

$$\text{input } i = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} l_1 \\ l_2 \\ l_3 \end{bmatrix}$$

$x =$  voltage  $S$ -vector

$$v_i = \text{input} \begin{bmatrix} v_1 = \text{input} \\ v_2 = 0 \\ v_3 = x \end{bmatrix} \quad \text{as } v_0 = 0 \text{ for no load}$$

$$\begin{bmatrix} i_1 \\ \frac{1}{g} v_0 \\ -C_2 x \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} & g_{13} \\ \frac{1}{g} D & y_{22} & \frac{1}{g} C \\ -C_2 B & y_{32} & -C_2 A \end{bmatrix} \begin{bmatrix} v_1 \\ 0 \\ x \end{bmatrix}$$

$$i = Ax + Bv_i$$

$$v_0 = Cx + Dv_i$$

these  $y_{11}, y_{12}, y_{13}, y_{22}, y_{32}$  are don't care matrices  
these can be real & arbitrary

can make a lot of this above

& passive in 1, 1 & 2, 2 reactions,  $G_{11} > 0, G_{22} > 0$

$$Y_{\text{coupling}} = \begin{bmatrix} G_{11} & -\frac{1}{g} D^T & & \\ \frac{1}{g} D & G_{22} & & \\ -C_2 B & -\frac{1}{g} C^T & & \\ & & +B^T C_2^T & \\ & & & \frac{1}{g} C & \\ & & & & -C_2 A \end{bmatrix}$$

$$E_{X_1}: \frac{V_o}{V_i} = \frac{2a^2 + 3a + 4}{a^3 + 5a^2 + 6a + 7} + 8$$

is P(a) = a<sup>3</sup> + 5a<sup>2</sup> + 6a + 7 *primality*



$$= (5a^2 + 7) \left[ 1 + \frac{a^3 + 6a}{5a^2 + 7} \right]$$

is LPR?

$$y(a) = \frac{a(a^2 + 6)}{5(a^2 + 7/5)}$$

$\frac{1}{2} = y(1) > 0$ , & poles & zeros

on complex & alternate

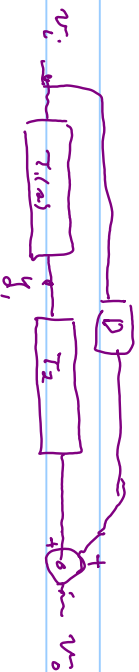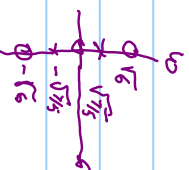

$$T_1 = \frac{1}{a^3 + 5a^2 + 6a + 7}, \quad T_2 = 2a^2 + 3a + 4$$

$$y_1 = T_1 v_i, \quad v_o = T_2 y_1 + D v_i$$

$$\text{for } T_1: (a^3 + 5a^2 + 6a + 7) y_1 = v_i \Rightarrow \begin{matrix} x_1 = y_1, & x_2 = \dot{x}_1 = \dot{y}_1 = ay_1, & x_3 = \ddot{x}_1 = \ddot{y}_1 = a^2 y_1 \end{matrix}$$

$$ax_3 + 5x_2 + 6x_1 + 7x_1 = v_i \Rightarrow \dot{x}_3 = v_i - 7x_1 - 6x_2 - 5x_3$$

$$\begin{bmatrix} a & 0 & 0 \\ 0 & a & 0 \\ 0 & 0 & a \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -7 & -6 & -5 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix} v_i$$

$$Cv = \begin{bmatrix} 2 & 3 & 4 \\ 2 & 3 & 4 \end{bmatrix} v = 2x_1^2 + 3x_2 + 4x_1$$

$$v_0 = Cx + Dv_c$$

$$= \begin{bmatrix} 4 & 3 & 2 \\ 4 & 3 & 2 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

$$\begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

$$Y_c = \begin{bmatrix} G_{11} & -8 & +[0 \ 0 \ 1] \\ 8 & G_{22} & [4 \ 3 \ 2] \end{bmatrix} \quad 5 \times 5$$

coupling

$$\text{choose } C_c = I_3 = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$g = 1$$

$$\text{choose } G_{11} = G_{22} = 0$$

$$Y_c = \begin{bmatrix} 0 & -8 & 0 & 0 & 1 \\ 8 & 0 & 4 & 3 & 2 \\ 0 & -4 & 0 & -1 & 0 \\ 0 & -3 & 0 & 0 & -1 \\ -1 & -2 & 7 & 6 & 5 \end{bmatrix}$$

5x5 coupling admittance  
constant, make with OTA's

we can transform the state by  $\tilde{x} = Px$ ;  $(Pv) = PAP^{-1}(Px) + PBv_c \Rightarrow \tilde{x} = Px$  in a new state

$$v_0 = CP^{-1}(Px) + Dv_c$$

state

i: local ports 3 through 5 in unit capacitors & port 2 in a unit gyrator, feed port 1 with input voltage

---

good for VLSI