

sensitivity example

$$v_o \rightarrow i_2 = 0$$

$$v_i$$

open circuit load, $i_2 = 0$

$$Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$Y_a = \frac{1}{g_2} \begin{bmatrix} 0 & g_2 \\ -g_2 & 0 \end{bmatrix}$$

$$\begin{aligned} r_i &= v_{ia} + v_{ib} \\ &= \underbrace{v_{ia}}_{\frac{v_i}{g_1}} + \underbrace{\frac{1}{g_1} \cdot \frac{v_i}{g_2}}_{v_{ib}} \end{aligned} \Rightarrow Z = Z_a + Z_b$$

$$Y_a = \frac{1}{g_2} \begin{bmatrix} 0 & g_2 \\ -g_2 & 0 \end{bmatrix}, Z_a = Y_a^{-1} = \frac{1}{g_2} \begin{bmatrix} 0 & -g_2 \\ g_2 & 0 \end{bmatrix} = \begin{bmatrix} 0 & -1/g_2 \\ 1/g_2 & 0 \end{bmatrix}$$

$$Z_b = \begin{bmatrix} 1 & 0 \\ 0 & 1/g_2 \end{bmatrix}$$

$$Z = \begin{bmatrix} \frac{1}{g_1} + 0 & \frac{1}{g_1} \cdot \frac{1}{g_2} \\ \frac{1}{g_1} \cdot \frac{1}{g_2} & \frac{1}{g_2} \end{bmatrix}; \quad \Delta Z: \det Z = \left(\frac{1}{g_1}\right)^2 \left(\frac{1}{g_1} \cdot \frac{1}{g_2} - \frac{1}{g_2}\right) = \frac{1}{g_1^2 g_2}$$

$$Y = \frac{1}{V_A C} \begin{bmatrix} -1 & 1 \\ 1 & 0 \end{bmatrix}$$

$$i_2 = y_{21}v_1 + y_{22}v_2 \approx 0 \text{ in original, } \frac{v_2}{v_1} \approx -\frac{y_{21}}{y_{22}} \approx -\left(\frac{-1}{g_1} - \frac{1}{g_2}\right) = 1 + \frac{g_1}{g_2}$$

$$\text{sensitivity } S_x^T = \frac{1}{T} \frac{dT}{dx} \Rightarrow S_c = \frac{\frac{d\omega}{dx}}{(1 + \frac{\omega c}{g})} = \frac{\frac{d(\omega + \frac{\omega c}{g})}{dx}}{1 + \frac{\omega c}{g}} = \frac{\frac{d\omega}{dx}}{g + \omega c} =$$

$$\text{if } a = i\omega \Rightarrow S_T^{(j\omega)} = \frac{1}{|T| e^{i\omega T}} \cdot \frac{d|T| e^{i\omega T}}{dx} = \frac{d|T|}{dx} \cdot \frac{e^{i\omega T}}{|T| e^{i\omega T}} + \frac{|T| \cdot \frac{dC}{dx}}{|T| e^{i\omega T}} = \frac{1}{|T|} \frac{d|T|}{dx} + \frac{e^{i\omega T}}{|T|} \frac{dC}{dx}$$

$$= S_x^T + j \frac{dC}{dx}$$

~~~~~

RC synthesis

$$\text{at } \omega = 0, L_C \Im(a) = k_{00} \cdot a + \frac{k_0}{a} + \sum_{i=1}^{i=m} \frac{k_i a}{a^2 + \omega_i^2}$$

$$L_C \Im(k_{00}) C = \frac{R}{k_0} \quad \omega = 0 \quad C = \frac{1}{k_0}$$

$$\text{or } \left[ \begin{array}{c} \text{---} \\ \text{---} \end{array} \right] \left[ \begin{array}{c} \text{---} \\ \text{---} \end{array} \right] \dots \left[ \begin{array}{c} \text{---} \\ \text{---} \end{array} \right]$$

$$c_i = \frac{1}{k_i}$$

$$R_i = k_i / \omega_i$$

Replace each L by an R to get an RC circuit


$$C_i = 1/R_i$$

$$R_o = k_{\infty} \quad C = 1/k_o \quad \left[ \frac{1}{k_o} \right] \rightarrow \left[ \frac{1}{k_1} \right] \cdots \left[ \frac{1}{k_n} \right] \Rightarrow Z_{RC} = R_o + \frac{k_o}{\omega} + \sum_{i=1}^n \frac{k_i}{\omega + \omega_i^2}, \quad \text{all } k_i > 0$$

$$R = k/(w_i^2)$$

$$Z_i = \frac{1}{R_i + \omega_i^2} = \frac{k_i}{\omega + \omega_i^2}$$

$$Z_{RC} \text{ poles move @ infinity}$$

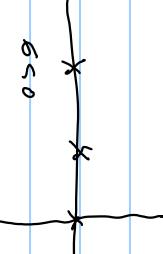


$$Z_{RC}(\omega)$$


derivative is always < 0

$$\text{Look @ } \frac{dZ_{RC}}{d\omega} = -\frac{k_o}{\omega^2} + \sum_{i=1}^n \frac{-k_i \omega}{(\omega + \omega_i^2)^2}$$

$\omega = 0$  derivative is always < 0

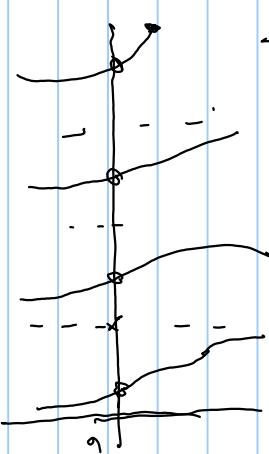
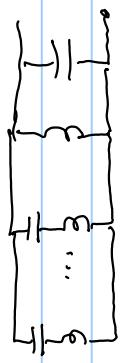
$$Y_{RC} = \frac{1}{Z_{RC}} = \text{harmonic 2nd Order, } Y_{RC} = \frac{1}{R_o k_o} + \frac{1}{\omega^2} + \sum_{i=1}^n \frac{k_i \omega}{(\omega + \omega_i^2)^2}$$



$$\frac{1}{Z_{RC}} = R_o + \frac{1}{\omega^2} \Rightarrow \frac{1}{Z_{RC}} = R_o + \frac{1}{\omega_c^2} = \frac{\omega_c^2 R_o}{\omega_c^2 + \omega_c^2} = \frac{\omega_c^2 + G_C}{\omega_c^2 + \omega_c^2 + G_C} = \frac{\omega_c^2 + G_C}{\omega_c^2 + \omega_G}$$

$$y = \frac{1}{R\alpha} + \frac{1}{R_0} + \sum_{i=1}^n \frac{\alpha c_i}{R_i k_i^{k+1}}$$

is not a partial fraction

$$\text{form } \frac{y_{rc}}{\alpha} = \frac{1}{R\alpha} + \frac{1}{R_0} + \sum_{i=1}^n \frac{G_i}{\alpha + G_i/c_i} \text{ This is a partial fraction expansion of } \frac{y_{rc}}{\alpha}$$

$\therefore$  for 2nd Order make a partial fraction expansion of  $y/R$  & then synthesize each term in  $y$  after multiplying back the  $R$ .

for 1st Order we expand about  $\alpha = 0$ ; remove poles of  $y$  & constants of  $\bar{z}$

for 2nd Order we expand about  $\alpha = 0$ ; remove constants @  $\alpha = 0$  of  $y$ , for  $\bar{z}$ , poles @ 0

$$\text{Ex: } y(\alpha) = \frac{\alpha(\alpha+2)}{(\alpha+1)^2} \Rightarrow y/\alpha = \frac{\alpha+2}{\alpha+1} = 1 + \frac{\alpha}{\alpha+1} \quad \text{pk: } \alpha+2 = \alpha+1+k_1 \Rightarrow k_1 = 1$$

$$\begin{aligned} y &= \alpha + \frac{\alpha}{\alpha+1} \Rightarrow \frac{1}{\alpha+1}, \frac{\alpha}{\alpha+1} \\ &\quad \end{aligned}$$