

$$\dot{x} = Ax + Bu, \quad y = Cx + Du, \quad x = k\text{-vector}$$

Linear time-invariant

Solution


$$x^{At} = \sum_{k=0}^{\infty} \frac{(At)^k}{k!} = I_k + At + \frac{1}{2} A^2 t^2 + \dots, \quad \frac{d}{dt} e^{At} = A e^{At}$$


$\therefore$  if  $u=0$   $\dot{x} = Ax$  is solved,  $x(t) = e^{At} x(0), t > 0$

if  $u \neq 0$  then  $x(t) = e^{At} x(0) + \int_0^t e^{A(t-\tau)} B u(\tau) d\tau, t \geq 0$

OTO solve  $\dot{x} = Ax + Bu$ , need the Diagonal matrix

Transformers


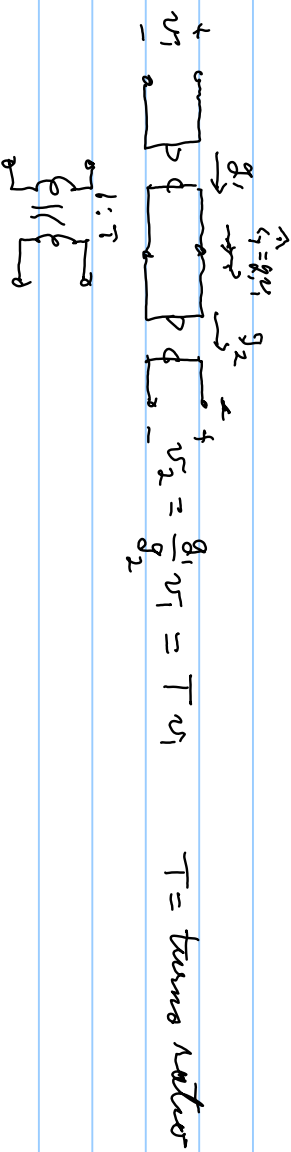


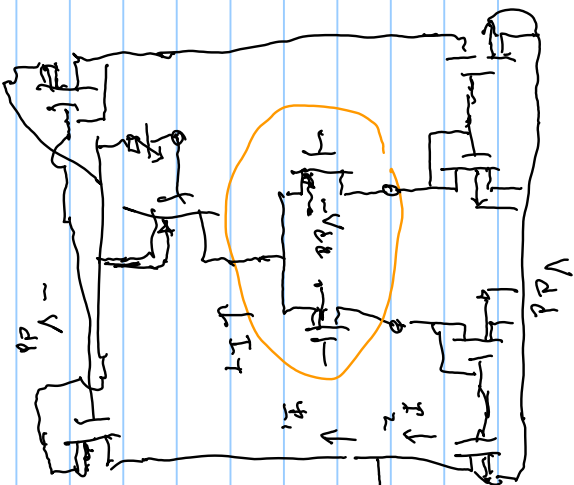

$V_T =$  thermal voltage  
 $= \frac{kT}{q} \approx 26 \text{ mV} @ \text{room Temp}$

$\square =$  differential gain

of 135T

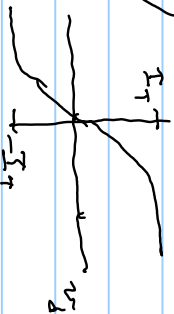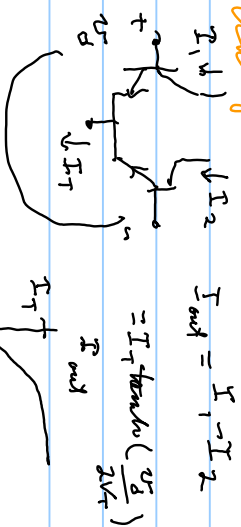


small signal gain is

$$\frac{dI_{out}}{dv_d} \Big|_{v_d=0} \approx \frac{d I_T \tanh(\frac{v_d}{2V_T})}{dv_d} \Big|_{v_d=0} = I_T \left( 1 - \tanh^2\left(\frac{v_d}{2V_T}\right) \right) \cdot \frac{1}{2V_T} \Big|_{v_d=0} = \frac{I_T}{2V_T}$$

$v_d$  small signal gain

Initial conditions:

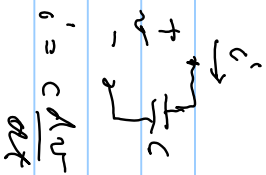

$v(0^-) = v(0^+)$  if we the capacitor & no  $\infty$  current is allowed

switch

$$i = C \frac{dv}{dt}$$

if  $C$  is time varying:  $i = \frac{dq}{dt} \approx \frac{d(C \cdot v)}{dt} = C \cdot \frac{dv}{dt} + \frac{dC}{dt} \cdot v$

$q = \text{charge on capacitor} = C \cdot v$

if  $C$  is voltage dependent & time dependent  $\frac{d(C(v,t) \cdot v)}{dt} = \frac{\partial(C(v,t) \cdot v)}{\partial v} \cdot \dot{v} + \frac{\partial(C(v,t) \cdot v)}{\partial t} + C \cdot \frac{dv}{dt}$