
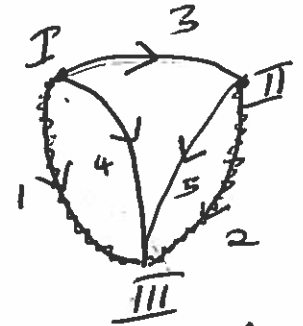


Homework 2.

Q(a)

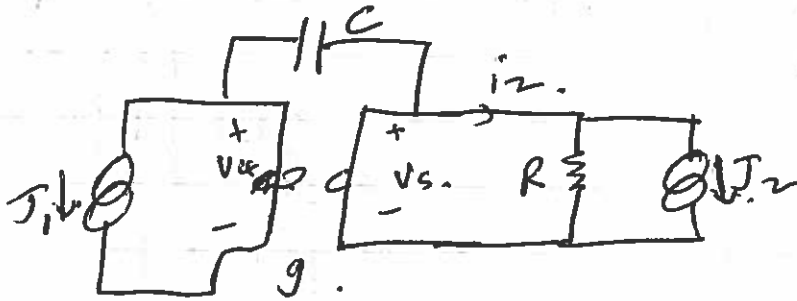

graph

(b)

$$AV = Bi$$

$$i = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} v.$$

$$\begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & g_R & 0 & 0 & 0 \\ 0 & 0 & sC & 0 & 0 \\ 0 & 0 & 0 & 0 & g \\ 0 & 0 & 0 & -g & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

$$C = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix}$$

$$J_s = \begin{bmatrix} J_1 \\ J_2 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$-CJ_s = - \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} -J_1 \\ -J_2 \end{bmatrix}$$

$$CACT = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & G_R & 0 & 0 & 0 \\ 0 & 0 & sC & 0 & 0 \\ 0 & 0 & 0 & 0 & G \\ 0 & 0 & 0 & -G & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 1 & -1 \\ 1 & 0 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 0 & 0 & sC & 0 & G \\ 0 & G_R & -sC & -G & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 1 & -1 \\ 1 & 0 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} sC & -sC + G \\ -sC - G & G_R + sC \end{bmatrix}$$

$$CACTV_t = CT_s$$

$$\begin{bmatrix} sC & -sC + G \\ -sC - G & G_R + sC \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -I_1 \\ -I_2 \end{bmatrix}$$

$$\det(CACT) = sC(G_R + sC) + (G - sC)(G + sC)$$

$$= sC(G_R + sC) + G(G - sC) + G(sC - G)$$

$$= sC(G_R + sC) + G^2 - G^2$$

$$= G_R sC + G^2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{-1}{sC(G_R + G) + G^2} \begin{bmatrix} G_R + sC & sC - G \\ sC + G & sC \end{bmatrix} \begin{bmatrix} + J_1 \\ + J_2 \end{bmatrix}$$

==

(c)

Impedance matrix

$$Z = \frac{-1}{sC(G_R + G) + G^2} \begin{bmatrix} G_R + sC & sC - G \\ sC + G & sC \end{bmatrix}$$

Admittance

$$Y = Z^{-1}$$

$$= - \begin{bmatrix} sC & -sC + G \\ -sC - G & G_R + sC \end{bmatrix}$$

$$\textcircled{2} \quad z(s) = \frac{2s+6}{(s+2)(s+6)} = \frac{2s+6}{s^2+8s+12}.$$

$$T(s) = \frac{2s}{s^2} \rightarrow 0. \quad \therefore D=0.$$

$$A = \begin{bmatrix} 0 & 1 \\ -12 & -8 \end{bmatrix} \quad B = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \quad C = \begin{bmatrix} 6 & 2 \end{bmatrix} \\ D=0.$$

$$y = [C(sI_2 - A)^{-1}B + D]u.$$

$$z = \begin{bmatrix} 6 & 2 \end{bmatrix} \begin{bmatrix} s & -1 \\ 12 & s+8 \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$z(s) = \frac{2s+6}{s^2+8s+12}.$$

$$\therefore A = \begin{bmatrix} 0 & 1 \\ -12 & -8 \end{bmatrix}$$

$$B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$C = \begin{bmatrix} 6 & 2 \end{bmatrix}$$

$$D = 0.$$

$$(b) \quad A = \begin{bmatrix} -6 & 0 \\ 0 & -2 \end{bmatrix} \quad A = \begin{bmatrix} -2 & 0 \\ 0 & -6 \end{bmatrix}$$

$$B = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \quad C = \frac{1}{2} \begin{bmatrix} 1 & 3 \end{bmatrix}$$

$$\lim_{s \rightarrow \infty} \frac{2s}{s^2} = 0. \quad D = 0.$$

$$Z(s) = \frac{1}{2} \begin{bmatrix} 1 & 3 \end{bmatrix} \begin{bmatrix} s+2 & 0 \\ 0 & s+6 \end{bmatrix}^{-1} \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$= \frac{1}{2} \begin{bmatrix} 1 & 3 \end{bmatrix} \begin{bmatrix} s+6 & 0 \\ 0 & s+2 \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$= \frac{2s+6}{(s+6)(s+2)} = \frac{2s+6}{s^2+8s+12}$$

$$(c) \quad y(s) = \frac{1}{z(s)} = \frac{s^2+8s+12}{2s+6}$$

$$y = \int C (sI_2 - A)^{-1} B + D.$$

$$s \rightarrow \infty. \quad \frac{s^2}{2s} \rightarrow \infty. \quad D \rightarrow \infty.$$

It cannot be realized.