

ENEE 610
Electrical Network Theory

HomeWork # 07

Ihteyaz Aqeed 'Arash'

115505704


Problem 01

a) Here, $\frac{V_2}{V_1} = \frac{K}{\lambda^4 + 3\lambda^3 + 8\lambda^2 + 9\lambda + 12} = \frac{\frac{K}{3\lambda^3 + 9\lambda}}{1 + \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda}}$


So, $Y_{22} = \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda}$

Now,
$$\begin{array}{r} 3\lambda^3 + 9\lambda \overline{) \lambda^4 + 8\lambda^2 + 12} \left(\frac{1}{3}\lambda \right. \\ \underline{\lambda^4 + 3\lambda^2} \\ 5\lambda^2 + 12 \overline{) 3\lambda^3 + 9\lambda} \left(\frac{3}{5}\lambda \right. \\ \underline{3\lambda^3 + 36\lambda} \\ \frac{9}{5}\lambda \overline{) 5\lambda^2 + 12} \left(\frac{25}{9}\lambda \right. \\ \underline{5\lambda^2} \\ 12 \overline{) \frac{9}{5}\lambda} \left(\frac{3}{20}\lambda \right. \\ \underline{\frac{9}{5}\lambda} \\ \phantom{\frac{9}{5}\lambda +} 0 \end{array}$$

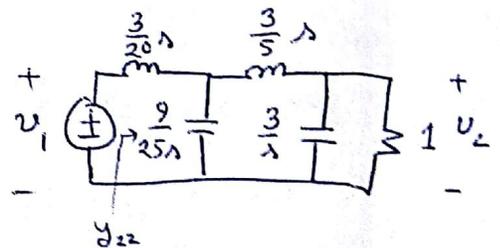So,
$$Y_{22}(\lambda) = \frac{1}{3}\lambda + \frac{1}{\frac{3}{5}\lambda + \frac{1}{\frac{25}{9}\lambda + \frac{1}{\frac{3}{20}\lambda}}}$$



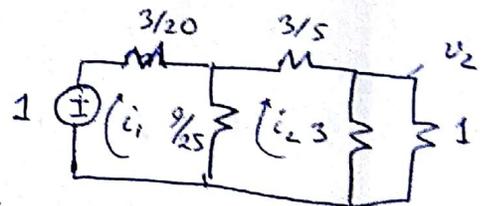Now, to evaluate K , let $\lambda = 1$
& $V_1 = 1$.



Solving using KVL, $i_1 = \frac{76}{33}$, $i_2 = \frac{16}{33}$

So, $V_2 = \frac{3}{4} i_2 = \frac{4}{11}$

again, $\frac{V_2}{V_1} = \frac{K}{1 + 3 + 8 + 9 + 12} \Rightarrow V_2 = \frac{K}{33}$


Equating, $\boxed{K = 12}$

$$(b) \text{ Here, } \frac{V_2}{V_1} = \frac{K\lambda^4}{\lambda^4 + 3\lambda^3 + 8\lambda^2 + 9\lambda + 12} = \frac{\frac{K\lambda^4}{3\lambda^3 + 9\lambda}}{1 + \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda}}$$

$$\text{So, } y_{22} = \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda}$$

$$\text{Now, } \frac{9\lambda + 3\lambda^3}{12 + 8\lambda^2 + \lambda^4} \left(\frac{4}{3\lambda} \right) \cdot \frac{9\lambda + 3\lambda^3}{9\lambda + \frac{9}{4}\lambda^3} \left(\frac{9}{4\lambda} \right) \cdot \frac{9\lambda + \frac{9}{4}\lambda^3}{\frac{3}{4}\lambda^3} \left(\frac{16}{3\lambda} \right) \cdot \frac{4\lambda^2 + \lambda^4}{4\lambda^2} \left(\frac{3}{4\lambda} \right) \cdot \frac{\frac{3}{4}\lambda^3}{\frac{3}{4}\lambda} \left(\frac{3}{4\lambda} \right)$$
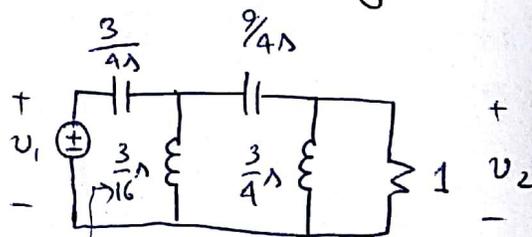
$$\text{So, } y_{22}(\lambda) = \frac{4}{3\lambda} + \frac{1}{\frac{9}{4\lambda} + \frac{1}{\frac{16}{3\lambda} + \frac{1}{\frac{3}{4\lambda}}}}$$




$$\text{Now, let, } V_1 = 1, \lambda = 1$$

Solving using KVL,

$$i_1 = \frac{107}{99}, \quad i_2 = \frac{7}{99}$$

$$\text{So, } V_2 = \frac{3}{7} \cdot \frac{7}{99} = \frac{1}{33}$$
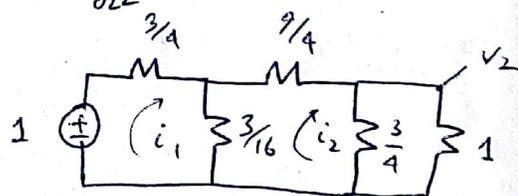
$$\text{Again, } V_2 = \frac{K}{33} \Rightarrow \boxed{K = 1}$$



$$(c) \text{ Here, } \frac{v_2}{v_1} = \frac{k\lambda^2}{\lambda^4 + 3\lambda^3 + 8\lambda^2 + 9\lambda + 12} = \frac{\frac{k\lambda^2}{3\lambda^3 + 9\lambda}}{1 + \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda}}$$

$$\text{So, } y_{22} = \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda}$$

$$\begin{aligned} \text{Now, } & \frac{9\lambda + 9\lambda^3}{12 + 8\lambda^2 + \lambda^4} \left(\frac{4}{3\lambda} \right) \\ & \frac{12 + 4\lambda^2}{4\lambda^2 + \lambda^4} \left(\frac{9\lambda + 3\lambda^3}{9\lambda + \frac{9}{4}\lambda^3} \right) \\ & \frac{\frac{3}{4}\lambda^3}{\lambda^4} \left(\frac{\lambda^4 + 4\lambda^2}{4\lambda^2} \right) \left(\frac{4}{3\lambda} \right) \\ & \frac{\frac{3}{4}\lambda^3}{4\lambda^2} \left(\frac{3}{4}\lambda^3 \right) \left(\frac{3}{16}\lambda \right) \\ & \frac{\frac{3}{4}\lambda^3}{4} \end{aligned}$$

$$\text{So, } y_{22}(\lambda) = \frac{4}{3\lambda} + \frac{1}{\frac{9}{4\lambda} + \frac{1}{\frac{4}{3}\lambda} + \frac{1}{\frac{3}{16}\lambda}}$$



Now, let, $v_1 = 1, \lambda = 1$

Solving, we get,

$$i_1 = \frac{128}{99}, i_2 = \frac{28}{99}$$

$$\text{So, } v_2 = \frac{3}{7} \times \frac{28}{99} = \frac{4}{33}$$
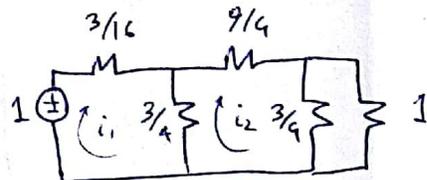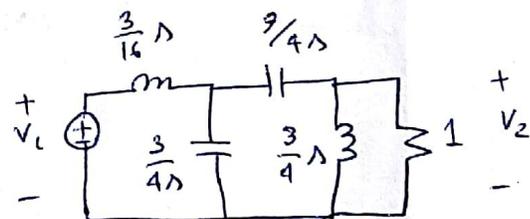
$$\text{But, } v_2 = \frac{k}{33} \Rightarrow \boxed{k = 4}$$




(d) For part (a), $\frac{V_2}{V_1} = \frac{12}{s^4 + 3s^3 + 8s^2 + 9s + 12} = \frac{\frac{12}{3s^3 + 9s}}{1 + \frac{s^4 + 9s^2 + 12}{3s^3 + 9s}} = \frac{y_{21}}{1 + y_{22}}$

So, we get, $y_{21} = -\frac{12}{3s^3 + 9s}$, $y_{22} = \frac{s^4 + 9s^2 + 12}{3s^3 + 9s}$

From the symmetry condition, $y_{12} = y_{21} = -\frac{12}{3s^3 + 9s}$

Now, $y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$

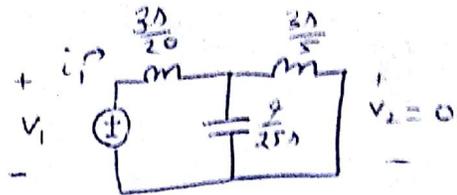

$$\begin{aligned} \text{Here, } Z_{11} &= \frac{3s}{20} + \left(\frac{9}{25s} \parallel \frac{3s}{5} \right) \\ &= \frac{3s}{20} + \frac{\frac{9}{25s} \times \frac{3s}{5}}{\frac{9}{25s} + \frac{3s}{5}} \\ &= \frac{3s}{20} + \frac{27s}{5(15s^2 + 9)} \end{aligned}$$

$$= \frac{3s^3 + 9s}{20s^2 + 12}$$

So, $y_{11} = \frac{20s^2 + 12}{3s^3 + 9s}$

So,
$$Y(s) = \begin{bmatrix} \frac{20s^2 + 12}{3s^3 + 9s} & -\frac{12}{3s^3 + 9s} \\ -\frac{12}{3s^3 + 9s} & \frac{s^4 + 9s^2 + 12}{3s^3 + 9s} \end{bmatrix}$$

Here, $Y(s) + Y^T(-s) = 0$


So, $Y(s)$ is a lossless positive real system.

For part (b), $\frac{v_2}{v_1} = \frac{\lambda^4}{\lambda^4 + 3\lambda^3 + 8\lambda^2 + 9\lambda + 12} = \frac{\frac{\lambda^4}{3\lambda^3 + 9\lambda}}{1 + \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda}} = \frac{-y_{21}}{1 + y_{22}}$

So, $y_{21} = -\frac{\lambda^4}{3\lambda^3 + 9\lambda}$, $y_{22} = \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda}$

From symmetry condition, $y_{12} = y_{21} = -\frac{\lambda^4}{3\lambda^3 + 9\lambda}$

Now, $y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$

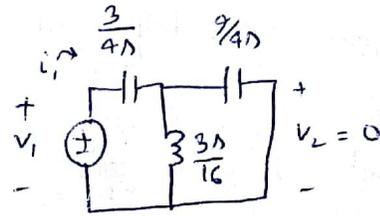

Now, $z_{11} = \frac{3}{4\lambda} + \left(\frac{3\lambda}{16} \parallel \frac{9}{4\lambda} \right)$

$$= \frac{3}{4\lambda} + \frac{\frac{3}{16} \times \frac{9}{4}}{\frac{3\lambda}{16} + \frac{9}{4\lambda}} = \frac{3}{4\lambda} + \frac{27\lambda}{12\lambda^2 + 144}$$

$$= \frac{3\lambda^2 + 9}{\lambda^3 + 12\lambda}$$

So, $y_{11} = \frac{\lambda^4 + 12\lambda^2}{3\lambda^3 + 9\lambda}$

So, $Y(\lambda) = \begin{bmatrix} \frac{\lambda^4 + 12\lambda^2}{3\lambda^3 + 9\lambda} & -\frac{\lambda^4}{3\lambda^3 + 9\lambda} \\ -\frac{\lambda^4}{3\lambda^3 + 9\lambda} & \frac{\lambda^4 + 8\lambda^2 + 12}{3\lambda^3 + 9\lambda} \end{bmatrix}$

Here, $Y(\lambda) + Y^T(-\lambda) = 0$, so it is a lossless positive real system.


Finally, for part (c),

$$\frac{v_2}{v_1} = \frac{4s^2}{s^4 + 3s^3 + 8s^2 + 9s + 12} = \frac{\frac{4s^2}{3s^3 + 9s}}{1 + \frac{s^4 + 8s^2 + 12}{3s^3 + 9s}} = \frac{-y_{21}}{1 + y_{22}}$$

$$\text{So, } y_{21} = -\frac{4s^2}{3s^3 + 9s}, \quad y_{22} = \frac{s^4 + 8s^2 + 12}{3s^3 + 9s}$$

$$\text{From symmetry condition, } y_{12} = y_{21} = -\frac{4s^2}{3s^3 + 9s}$$

$$\text{Now, } y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$$

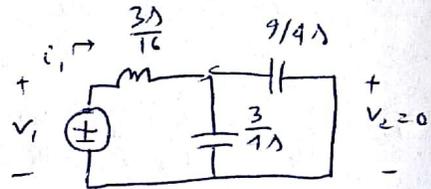

$$\text{where, } Z_{11} = \frac{3s}{16} + \left(\frac{3}{4s} \parallel \frac{9}{4s} \right)$$

$$= \frac{3s}{16} + \frac{\frac{3 \times 9}{16s^2}}{\frac{3}{4s} + \frac{9}{4s}}$$

$$= \frac{3s}{16} + \frac{9}{16s}$$

$$= \frac{3s^2 + 9}{16s}$$

$$\text{So, } y_{11} = \frac{16s^2}{3s^3 + 9s}$$

$$\text{So, } Y(s) = \begin{bmatrix} \frac{16s^2}{3s^3 + 9s} & -\frac{4s^2}{3s^3 + 9s} \\ -\frac{4s^2}{3s^3 + 9s} & \frac{s^4 + 8s^2 + 12}{3s^3 + 9s} \end{bmatrix}$$

Here, $Y(s) + Y^T(-s) = 0$, So, the system is a lossless positive real one.

Problem 02

(a) Here, $Z(s) = \frac{3s(s^2+4)}{s^2+2} \Rightarrow Y(s) = \frac{s^2+2}{3s(s^2+4)} = \frac{i(s)}{v(s)}$

∴ Here, let, $x_1 = \frac{1}{3s(s^2+4)} v(s)$

$$\Rightarrow v(s) = 3s^3 x_1(s) + 12s x_1(s)$$

Now, let, $x_2 = s x_1 = \dot{x}_1$

& $x_3 = s x_2 = s^2 x_1 = \ddot{x}_1$

then, $v = 3 \dot{x}_3 + 12 x_2 \Rightarrow \dot{x}_3 = \frac{1}{3} v - 4 x_2$

So, we can write,

$$\dot{x}_1 = x_2$$

$$\dot{x}_2 = x_3$$

$$\dot{x}_3 = -4x_2 + \frac{1}{3}v$$

$$\dot{i} = 2x_1 + x_3$$

So, we can write state-space realization as:-


$$\dot{x} = Ax + Bv \Rightarrow \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & -4 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 1/3 \end{bmatrix} v$$

$$\& \dot{i} = Cx + Dv \Rightarrow i = [2 \ 0 \ 1] \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} + [0]v$$

Now, let, $-C_{int} \dot{x} = - \begin{bmatrix} c_1 & 0 & 0 \\ 0 & c_2 & 0 \\ 0 & 0 & c_3 \end{bmatrix} \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \end{bmatrix} = - \begin{bmatrix} c_1 \dot{x}_1 \\ c_2 \dot{x}_2 \\ c_3 \dot{x}_3 \end{bmatrix}$ is the current, through capacitors of value c_1, c_2 & c_3 , \dot{i}_{int} .

Then, we can synthesize the network as:-

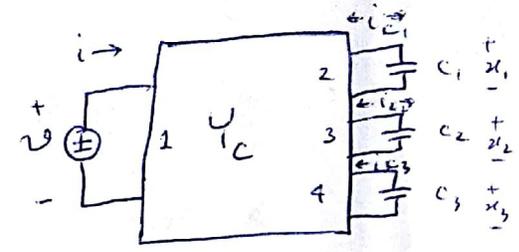Here, x is the potential drop across the capacitors. Then, the system can be written as,



$$\begin{bmatrix} i \\ i_{c1} \\ i_{c2} \\ i_{c3} \end{bmatrix} = Y_c \begin{bmatrix} v \\ x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} D & C \\ -C_{int}^B & -C_{int}^A \end{bmatrix} \begin{bmatrix} v \\ x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

Here, Y_c is the coupling admittance network. Choosing, $C_{int} = 1_s = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$, $Y_c = \begin{bmatrix} D & C \\ -B & -A \end{bmatrix}$

$$\text{So, } \begin{bmatrix} i \\ i_{c1} \\ i_{c2} \\ i_{c3} \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 2 & 0 & 1 \\ 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & -1 \\ -1/3 & 0 & 4 & 0 \end{bmatrix}}_{Y_c} \begin{bmatrix} v \\ x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

So, we can synthesize the coupling network using parallel combinations of OTA's, & set all capacitors as unity to get the output current at the input terminal.

Here, $y(s)$ has a pole at infinity, which means the system is an LPR & can be synthesized.

$$(b) \text{ Here } \frac{V_2}{V_1} = \frac{\lambda^2 - a\lambda + b}{\lambda^2 + a\lambda + b}$$

$$\text{Let, } x_1 = \frac{1}{\lambda^2 + a\lambda + b} V_1$$

$$\Rightarrow V_1 = (\lambda^2 + a\lambda + b) x_1 = \ddot{x}_1 + a\dot{x}_1 + bx_1$$

$$\text{again, let, } x_2 = \dot{x}_1 \Rightarrow V_1 = \dot{x}_2 + ax_2 + bx_1$$

$$\text{also, } V_2 = (\lambda^2 - a\lambda + b) x_1 = \dot{x}_1 - a\dot{x}_1 + bx_1$$

$$= \dot{x}_2 - ax_2 + bx_1 = V_1 - 2ax_2$$

So, we can write,

$$V_2 = -2ax_2 + V_1$$

$$\dot{x}_1 = x_2$$

$$\dot{x}_2 = -bx_1 - ax_2 + V_1$$


So, state space realization,

$$\dot{x} = Ax + BV_1 \Rightarrow \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -b & -a \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} V_1$$

$$\& V_2 = Cx + DV_1 \Rightarrow V_2 = \begin{bmatrix} 0 & -2a \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 1 \end{bmatrix} V_1$$

Now, to synthesize the circuit, we can use a gyrator of gain g to get the output, & we can use intermediate capacitor terminals such that $-C_{int} \dot{x} = i_{int}$; where x is the voltage across capacitors C_1 & C_2 .

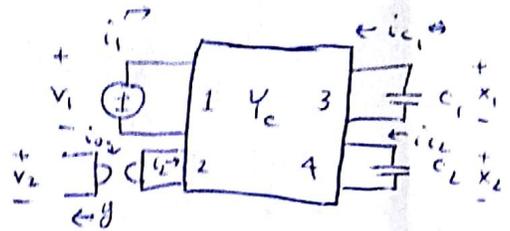It can be visualized as the figure that follows:



$$\text{Then, } \begin{bmatrix} i_1 \\ i_2 \\ i_{c1} \\ i_{c2} \end{bmatrix} = Y_c \begin{bmatrix} v_1 \\ v_2 \\ x_1 \\ x_2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_{in1} \end{bmatrix} = \begin{bmatrix} g_{11} & -\frac{1}{g} D^T & B^T C_{int}^T \\ \frac{1}{g} D & g_{22} & \frac{1}{g} C \\ -C_{int} B & -\frac{1}{g} C^T & -C_{int} A \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ x_1 \\ x_2 \end{bmatrix}$$

For simplicity, choosing $g=1$, $C_{int} = I_2 = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$,
& $g_{11} = g_{22} = 0$, we get, the coupling admittance,

$$Y_c = \begin{bmatrix} 0 & -D & B^T \\ D & 0 & C \\ -B & -C^T & -A \end{bmatrix}$$

$$\text{So, } \begin{bmatrix} i_1 \\ i_2 \\ i_{c1} \\ i_{c2} \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & -1 & 0 & 1 \\ 1 & 0 & 0 & -2a \\ 0 & 0 & 0 & -1 \\ -1 & 2a & b & a \end{bmatrix}}_{Y_c} \begin{bmatrix} v_1 \\ v_2 \\ x_1 \\ x_2 \end{bmatrix}$$

So, we can synthesize this all-pass circuit using parallel combinations of OTA's & gyrators, & set the capacitor & output gyrator as unity to design the required network.

Problem 03

a) we know, in Richards' section,

$$Y_R = \begin{bmatrix} nC & -nC+g \\ -nC-g & nC \end{bmatrix}$$

Now, replacing nC with $y(n)$, we get,

$$Y_R = \begin{bmatrix} y & -y+g \\ -y-g & y \end{bmatrix}$$



$$\text{So, } \Delta Y_R = y^2 - (y^2 - g^2) = g^2$$

$$\begin{aligned} \text{Now, } y_{in} &= y_{11} - \frac{y_{12}y_{21}}{y_{22} + y_L} = \frac{\Delta Y_R + y_{11}y_L}{y_{22} + y_L} \\ &= \frac{g^2 + yG}{y + G} \end{aligned}$$

But, for Richards' section, $G = |g| \Rightarrow g^2 = G^2$

$$\text{So, } y_{in} = \frac{G^2 + yG}{y + G} = G = y_L$$

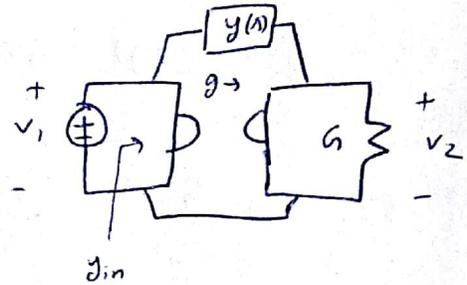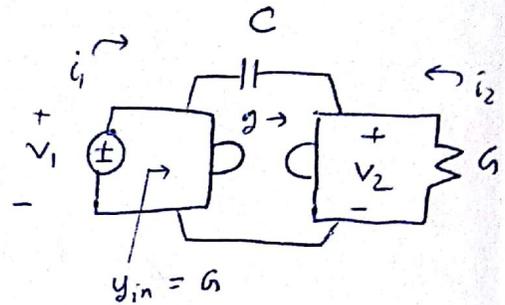So, this circuit is still an all-pass constant- R network.



Now, we need to determine the $y(s)$ required such that,

$$\frac{V_2}{V_1} = \frac{s^2 - a s + b}{s^2 + a s + b}$$

We know, for Richards' section, $\frac{V_2}{V_1} = \frac{sC + G}{sC + G}$

choosing, $y(s) = sC \Rightarrow \frac{V_2}{V_1} = \frac{y(s) - G}{y(s) + G}$


$$\text{So, } \frac{y - G}{y + G} = \frac{s^2 - a s + b}{s^2 + a s + b} = \frac{\left(s + \frac{b}{s}\right) - a}{\left(s + \frac{b}{s}\right) + a}$$

equating, $y(s) = s + \frac{b}{s}$

$$G = a$$


$$g = -a$$

So, we can synthesize the circuit as:-

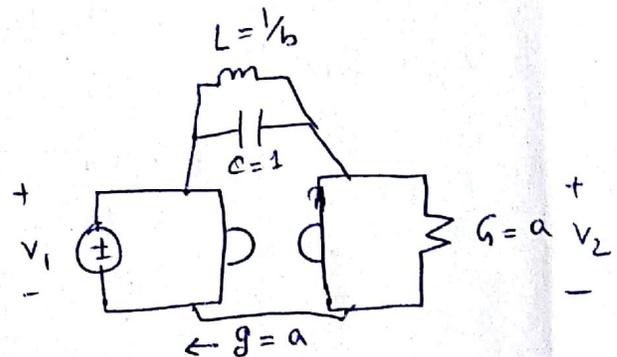

this is an all-pass constant-R circuit utilized via modified Richards' section.


(b) Any rational all-pass $\frac{V_2}{V_1}$ will have the property such that their poles & zeros are equal & opposite from the origin, i.e. they are equidistant from the origin, such that their amplitude, $|\frac{V_2}{V_1}|$ is always unity, & thus they can be used as filters for phase angle correction.

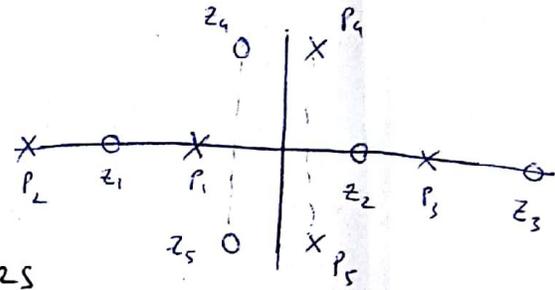

i.e., the general form of all all-pass filter is,

$$\frac{V_2}{V_1} = \frac{(s-\alpha_1)(s-\alpha_2)(s-\alpha_3)\dots(s-\alpha_n)}{(s+\alpha_1)(s+\alpha_2)(s+\alpha_3)\dots(s+\alpha_n)}$$

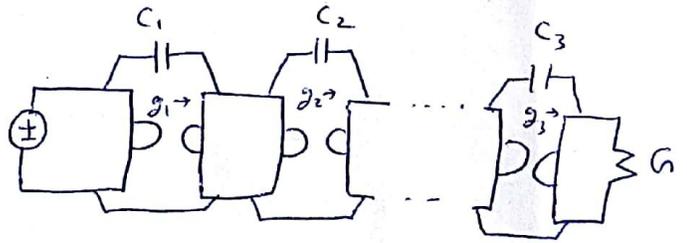We can design this system as a cascade of n -number of Richards' section circuits to get the overall constant- R circuit as:-



where, $G_1 = 1$, & for convenience, choose, $g_1 = g_2 = \dots = g_n = 1$, & $c_1 = \alpha_1$, $c_2 = \alpha_2$, \dots , $c_n = \alpha_n$. Thus, any rational all-pass circuit can be easily synthesized via Richards' sections.

→ —