
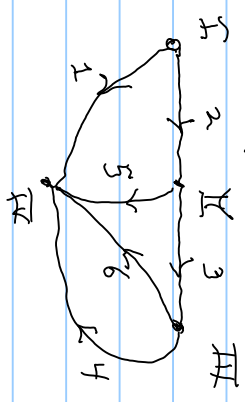


graph

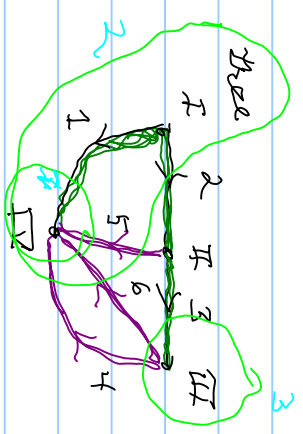

incidence graph



tree
 branches
 links
 ~ cutsets

KCL equations
 node 1: $0 = i_1 + 0.1i_2 + 0.1i_3 + i_4 + i_5 + i_6 \Rightarrow 0 = \sum i_b$
 node 2: $0 = 0.1i_1 + i_2 + 0.1i_3 - i_4 - i_5 - i_6$
 node 3: $0 = 0.1i_1 + 0.1i_2 + i_3 - i_4 + 0.1i_5 - i_6$

$i_b = \begin{cases} i_1 \\ i_2 \\ i_3 \end{cases}$ tree links

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 & -1 \\ 0 & 0 & 1 & -1 & 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

↑
t-variables

$t = 3$
 $\# t = t = 3$
 $\# \text{ links } = L = 3$
 $\# \text{ nodes } = N = 4$
 $\# \text{ branches } = b = 6$

KVL

the rest equations

$$\begin{cases} 4 \\ 5 \\ 6 \end{cases} \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{cases} -v_1 + v_2 + v_3 \\ -v_1 + v_2 + 0.1v_3 \\ v_1 + v_2 + v_3 \end{cases} + \begin{cases} v_4 + 0.1v_5 + 0.1v_6 \\ 0.1v_4 + v_5 + 0.1v_6 \\ 0.1v_4 + 0.1v_5 + v_6 \end{cases}$$

$$\begin{bmatrix} -1 & 1 & 1 & 1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 1 & 0 \\ -1 & 1 & 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

↑
1

$$0 = \mathcal{G} \cdot v_b ; \quad \mathcal{G} = \text{tie set matrix} = \begin{bmatrix} -1 & 1 & 1 & 1 & 1 \\ -1 & 1 & 0 & 1 & 1 \\ -1 & 1 & 1 & 1 & 1 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 1 & 1 & 1 \\ 0 & k & 1 & 1 & 1 \\ 0 & k & 1 & 1 & 1 \end{bmatrix}$$




$$0 = E \cdot v_b ; \quad E = \text{cut set matrix} = \begin{bmatrix} 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 \end{bmatrix}$$

0 = rows in from outside

$$= v_1 i_1 + v_2 i_2 \dots + v_6 i_6 = [v_1, v_2, \dots, v_6] \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_6 \end{bmatrix} \approx v_b^T i_b = 0$$

$$v_b = E^T \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_6 \end{bmatrix} ; \quad i_b = \mathcal{G}^T \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_6 \end{bmatrix}$$
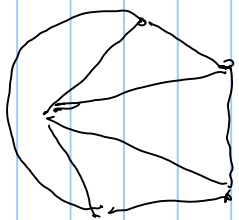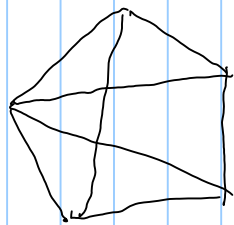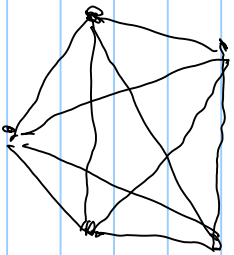
$$v_b^T i_b = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_6 \end{bmatrix}^T \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_6 \end{bmatrix} = 0 \quad \text{cancel } i_2 \& v_2 \text{ or can independently choose every entry for this proper analysis}$$



no crossing wires
planar graph


becomes

$$\sum_{i=1}^N v_i = 2$$

Power in = $v_1 i_1 + v_2 i_2$; $v_2 = N v_1$

$$0 = v_1 i_1 + N v_1 i_2 \Rightarrow 0 = i_1 + N i_2 \Rightarrow i_1 = -N i_2$$

if $N=1$

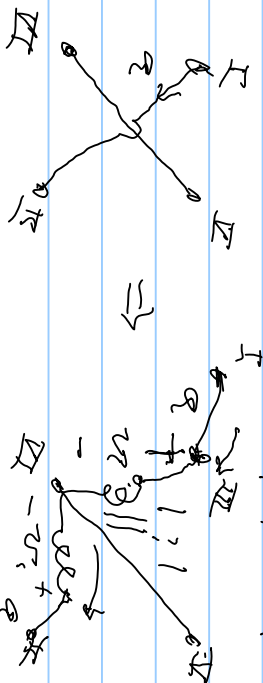

has unchanged equations
allows nonplanar graphs
To become planar
(add 2 of nodes & branches)

